

---

UNIVERSITI SAINS MALAYSIA

Semester I Examination  
Academic Session 2008/2009

November 2008

**EEE 542 – INDUSTRIAL POWER ELECTRONICS**

Time : 3 hours

---

**INSTRUCTION TO CANDIDATE:**

Please ensure that this examination paper contains **FOUR (4)** printed pages and **SIX (6)** questions before answering.

Answer **FIVE (5)** questions.

Distribution of marks for each question is given accordingly.

All questions must be answered in English.

- S1. Design single-phase full rectifier 2 quadrant with R and L load. Determine:
- (i) Sketch the output voltage waveform for  $\alpha=90^\circ$
  - (ii) Determine the circuit's efficiency at  $\alpha=90^\circ$
  - (iii) Value of  $\alpha$  if  $V_{dc}/V_m = 0.6$
  - (iv) What is the maximum efficiency of the circuit?
- (100%)
- S2. Design three-phase full converter, with highly inductive load from three-phase supply,  $V_s=208V$  and  $f=50Hz$ .
- (i) Sketch the output voltage waveform for  $\alpha=60^\circ$
  - (ii) Determine the value of  $V_{dc}$  and  $V_{rms}$  at  $\alpha=60^\circ$
  - (iii) The maximum efficiency of the circuit
  - (iv) What is the advantage of this circuit compared to half wave rectifier?
- (100%)
- S3. (a) Explain in brief the principle operation of an ac controller transformer tap.
- (30%)
- (b) For three-phase full wave ac controller Y connected R load:
- (i) Draw the complete design of the system
  - (ii) Determine the output waveforms for  $\alpha=60^\circ$  at load C
  - (iii) The rms output voltage the controller in term of  $\alpha$ .
- (70%)

- S4. (a) What are the performance parameters of inverter circuit?  
(20%)
- (b) Explain in detail the operation of a single-phase bridge inverter with inductive load from a dc source:
- (i) Sketch the complete design
  - (ii) The output voltage and current waveforms
  - (iii) The rms output voltage
- (40%)
- (c) For question 3(b), if the circuit has an RLC with  $R=10\Omega$ ,  $L=30\text{mH}$ ,  $C=100\mu\text{F}$ ,  $f_o=50\text{ Hz}$  and dc input voltage  $V_s=240\text{ V}$ . Express the instantaneous load current in Fourier series.  
(40%)
- S5. Explain how a 3 phase inverter is constructed from a single dc supply. Describe in detail the concept apply in your design. Based on the  $180^\circ$  conduction, derive the expression for the instantaneous line to line voltage  $V_{ab}$  in a Fourier series.  
(100%)
- S6. (a) What are the advantages and disadvantages of a Boost regulator?  
(20%)

- (b) Referring to buck-boost regulators:
- (i) Draw the complete circuit diagram.
  - (ii) Explain in brief the circuit operation.
  - (iii) Sketch the waveform of the regulators.
  - (iv) Prove that this regulator can provides an voltage output that may be less than or greater than the input voltage.
  - (v) Derive the equations for  $I_{\min}$  and  $I_{\max}$ .
- (60%)
- (c) State the critical condition for continuous inductor current in this regulator.
- (20%)