

UNIVERSITI SAINS MALAYSIA

Peperiksaan Semester Pertama  
Sidang Akademik 1997/98

September 1997

EEE 237 - Pengantar Kejuruteraan Kuasa

Masa : [3 jam]

---

ARAHAN KEPADA CALON :

Sila pastikan bahawa kertas peperiksaan ini mengandungi **ENAM (6)** muka surat bercetak dan **ENAM (6)** soalan sebelum anda memulakan peperiksaan ini.

Jawab **LIMA (5)** soalan.

Agihan markah bagi soalan diberikan di sisi sebelah kanan soalan berkenaan.

Semua soalan hendaklah dijawab di dalam Bahasa Malaysia. Jika pelajar memilih menjawab di dalam Bahasa Inggeris sekurang-kurangnya satu soalan mesti dijawab di dalam Bahasa Malaysia.

1. Setiap cabang bagi suatu beban tiga fasa tersambung bintang terdiri daripada gegelung dengan rintangan  $4.2\Omega$  dan reaktans  $5.6\Omega$ . Beban tersebut dibekalkan pada voltan talian  $415V$ ,  $50Hz$ . Jumlah kuasa aktif yang dibekalkan kepada beban diukur menggunakan kaedah dua wattmeter. Lukis gambar rajah litar bagi sambungan-sambungan wattmeter tersebut dan kirakan bacaan-bacaan mereka secara berasingan. Terbitkan sebarang formula yang anda gunakan dalam pengiraan.

*Each branch of a three-phase star-connected load consists of a coil of resistance  $4.2\Omega$  and reactance  $5.6\Omega$ . The load is supplied at a line voltage of  $415V$ ,  $50Hz$ . The total active power supplied to the load is measured by the two-wattmeter method. Draw a circuit diagram of the wattmeter connections and calculate their separate readings. Derive any formula used in your calculations.*

(100%)

2. Keputusan-keputusan berikut didapati pada satu transformer  $50kVA$ : ujian litar buka: voltan utama,  $3300V$ ; voltan sekunder,  $415V$ ; kuasa utama,  $430W$ . Ujian litar pintas: voltan utama,  $124V$ ; arus utama,  $15.3A$ ; kuasa utama,  $525W$ ; arus sekunder, nilai beban penuh. Kirakan:

*The following results were obtained on a  $50kVA$  transformer: open-circuit test-primary voltage,  $3300V$ ; secondary voltage,  $415V$ ; primary power,  $430W$ . Short-circuit test - primary voltage,  $124V$ ; primary current,  $15.3A$ ; primary power,  $525W$ ; secondary current, full-load value. Calculate:*

- (a) kecekapan-kecekapan pada beban penuh dan separuh beban bagi faktor kuasa  $0.7$ .
- the efficiencies at full load and at half load for  $0.7$  power factor.*

- (b) pengaturan voltan bagi faktor kuasa 0.7,  
*the voltage regulations for power factor 0.7,*
- (i) mengekor,  
*lagging;*
- (ii) mendulu;  
*leading;*
- (c) voltan-voltan terminal sekunder yang sepadan dengan (i) dan (ii).  
*the secondary terminal voltages corresponding to (i) and (ii).*

(100%)

3. Suatu motor pirau 240-V bergerak selaju 850 r/min apabila arus angker ialah 70A. Rintangan litar angker ialah  $0.10\Omega$ . Kirakan rintangan yang diperlukan untuk diletakkan bersiri dengan angker bagi mengurangkan laju kepada 650 r/min apabila arus angker ialah 50A.

*A 240-V shunt motor runs at 850 r/min when the armature current is 70A. The armature circuit resistance is  $0.10\Omega$ . Calculate the required resistance to be placed in series with the armature to reduce the speed to 650 r/min when the armature current is then 50A.*

(100%)

4. Suatu motor aruhan tiga fasa 220-V 60-Hz enam-kutub 10hp mempunyai parameter-parameter litar berikut atas dasar per fasa merujuk kepada stator:

*A three-phase 220-V 60-Hz six-pole 10-hp induction motor has the following circuit parameters on a per phase basis referred to the stator:*

$$\begin{array}{ll} R_S = 0.344\Omega & R'_R = 0.147\Omega \\ X_S = 0.498\Omega & X'_R = 0.224\Omega \end{array} \quad X_m = 12.6\Omega$$

Jumlah kehilangan-kehilangan putaran dan kehilangan teras ialah 262W dan boleh dianggap malar. Bagi suatu gelincir 2.8%, tentukan:

*The rotational losses and core loss combined amount to 262W and may be assumed constant. For a slip of 2.8% determine:*

- (a) arus talian dan faktor kuasa  
*the line current and power factor*
- (b) tork aci dan kuasa kuda keluaran  
*the shaft torque and output horsepower*
- (c) kecekapan  
*the efficiency*

(100%)

...5/-

5. Suatu motor segerak 2200V tiga fasa tersambung Y mempunyai regangan segerak  $X_s = 2.6\Omega/\text{fasa}$ . Rintangan angker boleh diabaikan. Kuasa masukan ialah 820kW, sementara ujaan medan adalah supaya EMF pembilang bersamaan 2800V. Kirakan:

A 2200-V three-phase Y-connected synchronous motor has a synchronous reactance  $X_s = 2.6\Omega/\text{phase}$ . The armature resistance is assumed to be negligible. The input power is 820kW, while the field excitation is such that the counter EMF is 2800V. Calculate:

- (a) sudut tork  
*the torque angle*
- (b) arus talian  
*the line current*
- (c) faktor kuasa  
*the power factor*


(100%)

...6/-

6. Suatu litar tiristor ditunjukkan dalam Rajah 6. Jika tiristor  $T_1$  di 'ON'kan pada  $t=0$ , tentukan masa pengaliran tiristor  $T_1$  dan voltan kapasitor setelah  $T_1$  di 'OFF'kan. Parameter-parameter litar ialah  $L = 10\mu\text{H}$ ,  $C = 50\mu\text{F}$ , dan  $V_s = 200\text{V}$ . Pearuh membawa arus mula  $I_m = 250\text{A}$ .

A typical thyristor circuit is shown in Figure 6. If thyristor  $T_1$  is switched on at  $t=0$ , determine the conduction time of thyristor  $T_1$  and the capacitor voltage after it is turned off. The circuit parameters are  $L = 10\mu\text{H}$ ,  $C = 50\mu\text{F}$ , and  $V_s = 200\text{V}$ . The inductor carries an initial current of  $I_m = 250\text{A}$ .

(100%)

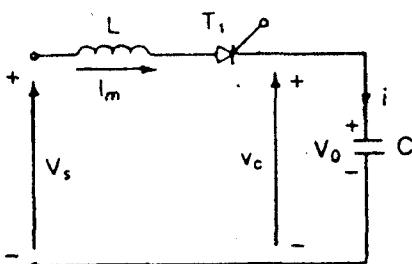

Rajah 6 - Litar Tiristor Tertukar Tertib-Diri

Figure 6 - Self-Commutated Thyristor Circuit

ooooooo