
UNIVERSITI SAINS MALAYSIA

Semester I Examination
Academic Session 2010/2011

November 2010

EEE 542 – INDUSTRIAL POWER ELECTRONICS

Time: 3 Hours

INSTRUCTION TO CANDIDATE:

Please ensure that this examination paper contains **SIX** printed pages and **SIX** questions before answering.

This question paper has four three sections, **Section A, Section B, Section C** and **Section D**.

Answer **ONE** question from each **Section A, Section B,** and **Section D**.
TWO question from **Section C**. Answer **FIVE** questions.

Distribution of marks for each question is stated accordingly.

All questions must be answered in English.

Section A: Answer question 1 or 2

1. A three phase semiconverter as shown in Figure 1 is operated from a three phase Y connected 208 V 60 Hz supply and the load resistance is $R=10\Omega$, and $L=10\text{mH}$. If it is required to obtain an average output voltage of 50% of the maximum possible output voltage, calculate
- a) The delay angle
 - b) The rms and average output current
 - c) The rectification efficiency

Maximum average output voltage occurs at delay angle of $\alpha=0$.
For $\alpha > \pi/3$ the output voltage is discontinuous. Assume $E=0$

(100 marks)

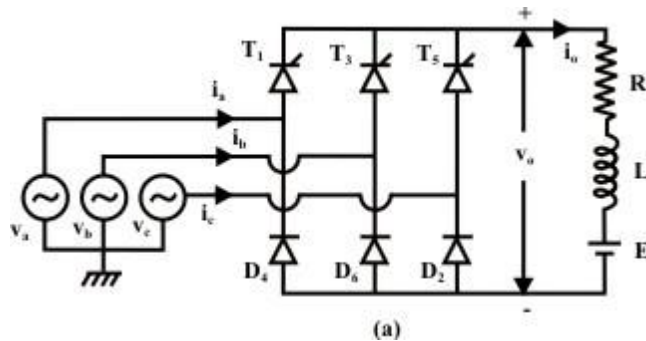


Figure 1: Semiconverter

2. A three phase full converter as shown in Figure 2 is also operated from a three phase Y connected 208 V 60 Hz supply and the load resistance is $R=10\Omega$ and $L=10\text{mH}$. If it is required to obtain an average output voltage of 50% of the maximum possible output voltage, calculate
- d) The delay angle
 - e) The rms and average output current
 - f) The rectification efficiency

Maximum average output voltage occurs at delay angle of $\alpha=0$. Assume $E=0$

(100 marks)

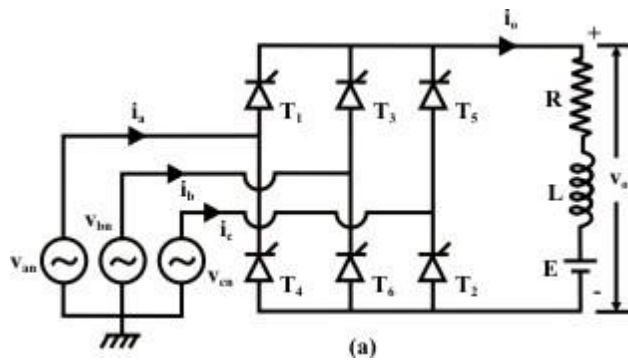


Figure 2: Full converter

Section B: Answer question 3 or 4

3. The three phase half wave ac controller is shown in Figure 3 supplies a wye-connected resistive load of $R=10\Omega$ and the line to line input voltage is 208 V (rms), 60 Hz. If the delay angle for the balance system is $\alpha=\pi/3$, determine:
- a) The rms output phase voltage for phase A
 - b) The input power factor PF

Draw the appropriate output voltage and highlight the technique used.

(100 marks)

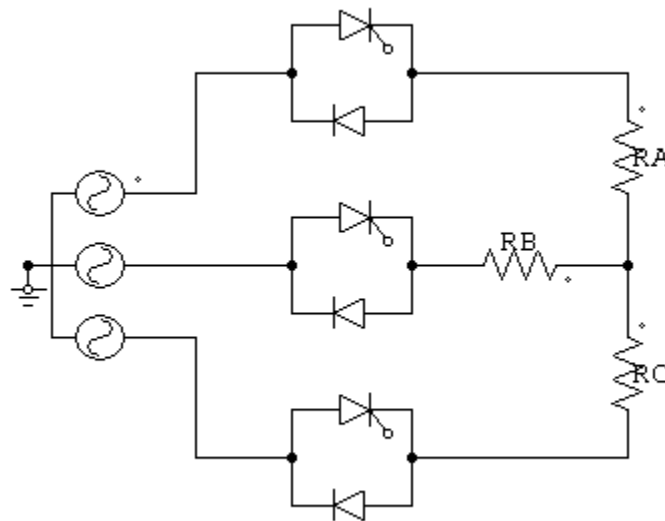


Figure 3: Half wave ac controller

4. The three phase full wave ac controller is shown in Figure 4 supplies a wye-connected resistive load of $R=10\Omega$ and the line to line input voltage is 208 V (rms), 60 Hz. If the delay angle for the balance system is $\alpha=\pi/3$, determine:
- a) The rms output phase voltage for phase B
 - b) The input power factor PF

Draw the appropriate output voltage and highlight the technique used.

(100 marks)

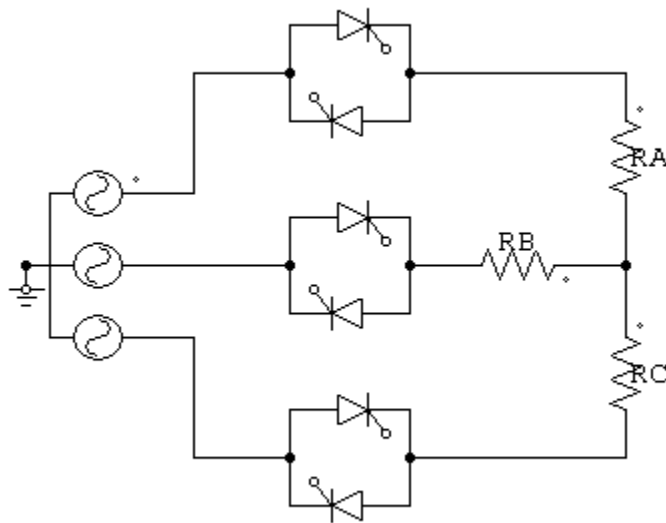


Figure 4: Full wave ac controller

Section C: Answer question 5, 6 or 7

5. The full bridge inverter in Figure 5 has an RLC load with $R=5\Omega$, $L=10\text{mH}$ and $C=20\mu\text{F}$. The inverter frequency $f_o=400\text{ Hz}$ and the dc input voltage $V_s=220\text{V}$

- a) Express the instantaneous load current in a Fourier series
- b) Calculate the THD of the load current

(100 marks)

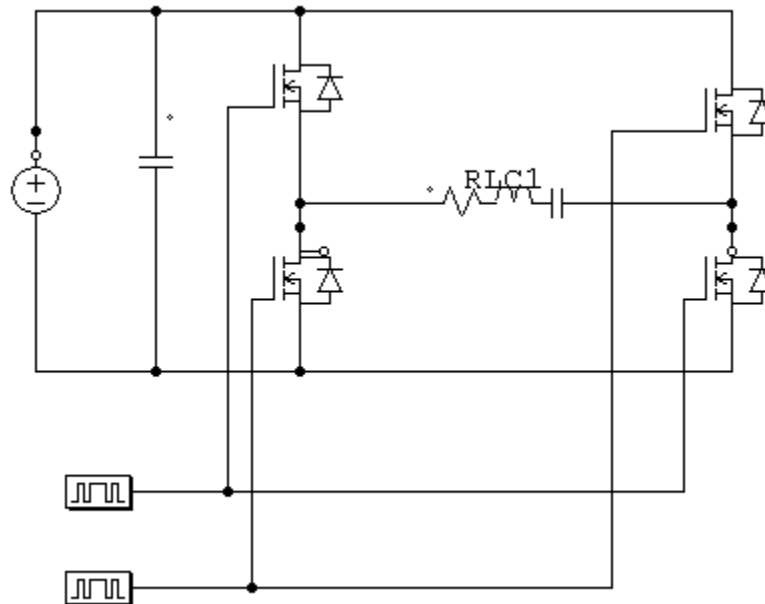


Figure 5: Inverter full bridge

6. Design a three phase inverter and show how a three phase output can be obtained from a configuration of six Mosfet. Applied appropriate control signal for the Mosfet.

Show the overall circuit diagram of the topology used. Assume Y to Y connection and show the derivation applied.

(100 marks)

7. Construct and design a 5 level multiple inverter. In this design:
- State clearly the topology used including the power devices
 - Draw the equivalent circuit for each of the output level and state the operation in a table.
 - Draw the switching waveforms and the final output voltage.
 - Explain how to calculate the inverter THD using PSIM and draw the appropriate harmonics waveforms
 - Suggest the improvement of your design in order to increase the inverter efficiency.

(100 marks)

Section D: Answer question 8 or 9

8. Design a buck converter such that the output voltage is 28V when the input is 48V. The load is 8 Ohm. Design the converter such that it will be in continuous current mode. The output voltage ripple must not be more than 0.5%. Specify the frequency and the values of each component. Suggest the power switch also.

(100 marks)

9. Design a boost converter to provide an output voltage of 36V from a 24V source. The load is 50Ω. The voltage ripple factor must be less than 0.5%. Specify the duty cycle ratio, switching frequency, inductor and capacitor size, and power device.

(100 marks)