

---

UNIVERSITI SAINS MALAYSIA

First Semester Examination  
Academic Session 2011/2012

January 2012

**EEE 510 – ADVANCED ANALOGUE CIRCUIT DESIGN**

Time : 3 hours

---

**INSTRUCTION TO CANDIDATE:**

Please ensure that this examination paper contains **SEVEN** printed pages and **SIX** questions before answering.

Answer **FIVE** questions.

Answer to any question must start on a new page.

Distribution of marks for each question is given accordingly.

All questions must be answered in English.

1. (a)

 


Figure 1: Switched Capacitor Resistor

- (i) Explain the function of MOSFET S1 and S2. (2 marks)
  - (ii) Derive the equivalent resistance of the circuit in Figure 1. (6 marks)
  - (iii) Explain the limitation of the circuit in Figure 1. (2 marks)
- (b)
- (i) What is the operation of MOSFET whereby the behaviour of VGS is similar as VBE of bandgap device? (2 marks)
  - (ii) Together with switched capacitor resistor, design a PTAT current generator. A final equation must be included together with the design. (8 marks)

2. (a) Given the simplified 3-bit DAC mathematical model is

$$V_{out} = (2^2 \overline{D[2]} + 2^1 \overline{D[1]} + 2^0 \overline{D[0]}) \times R$$

The model is based on current steering-resistor string approach. Draw the schematic of the DAC. Explain the functions of all the components in the schematic.

(12 marks)

- (b) Extend the model up to 8-bit. Explain your model.

(8 marks)

- 3.

 


Figure 2 : Biasing circuitries for a typical current steering DAC

- (a) Explain the function of the operational amplifier. (2 marks)
- (b) What is the value of current  $I$ , if  $R$  is  $3.7\text{ k}\Omega$  and  $V_{REF} = 1.2\text{V}$ ? (2 marks)
- (c) Assuming  $V_{DD} = 3\text{ V}$  and  $M1$  is in saturation,  $W/L = 10/2$ ,  $V_{tp} = -1$ ,  $K_p = 40\ \mu\text{A}/\text{V}^2$ , calculate the required  $V_{GS}$ . (6 marks)
- (d) Draw the basic 8-bit DAC which must include the biasing circuitries and the DAC resistor string. (10 marks)

4. Question 4 refer to Figure 1.

- (a) Draw small signal model of the circuit. (10 marks)
- (b) Derive the expression of  $R_{OUT}$ . (10 marks)

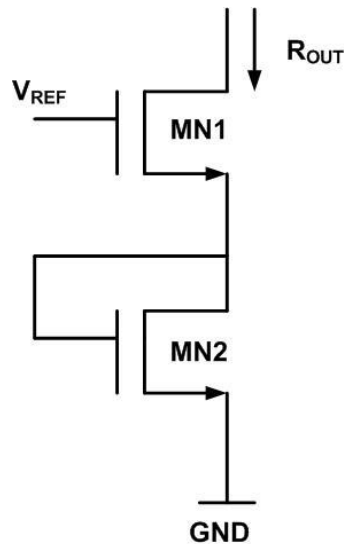


Figure 1

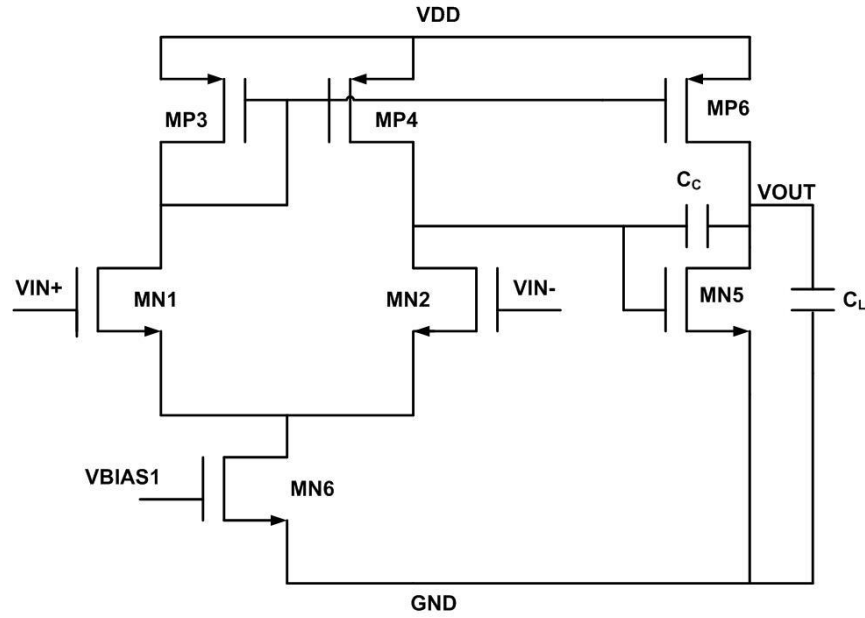


Figure 2

5. Figure 2 shows configuration of two stages CMOS OTA.

(a) Find total DC gain. (5 marks)

(b) The design is required to have 75 degree phase margin what is the ratio of  $gm1/gm5$ .

(5 marks)

(c) Calculate the settling time that gives error percentage  $\varepsilon$  (0.01%) of unity configuration.

(Neglect intrinsic capacitance ,  $V_{DD} = 1V$  ,  $GBW = 500MHz$  , assume value of  $C_L = 1pf$ )

(10 marks)

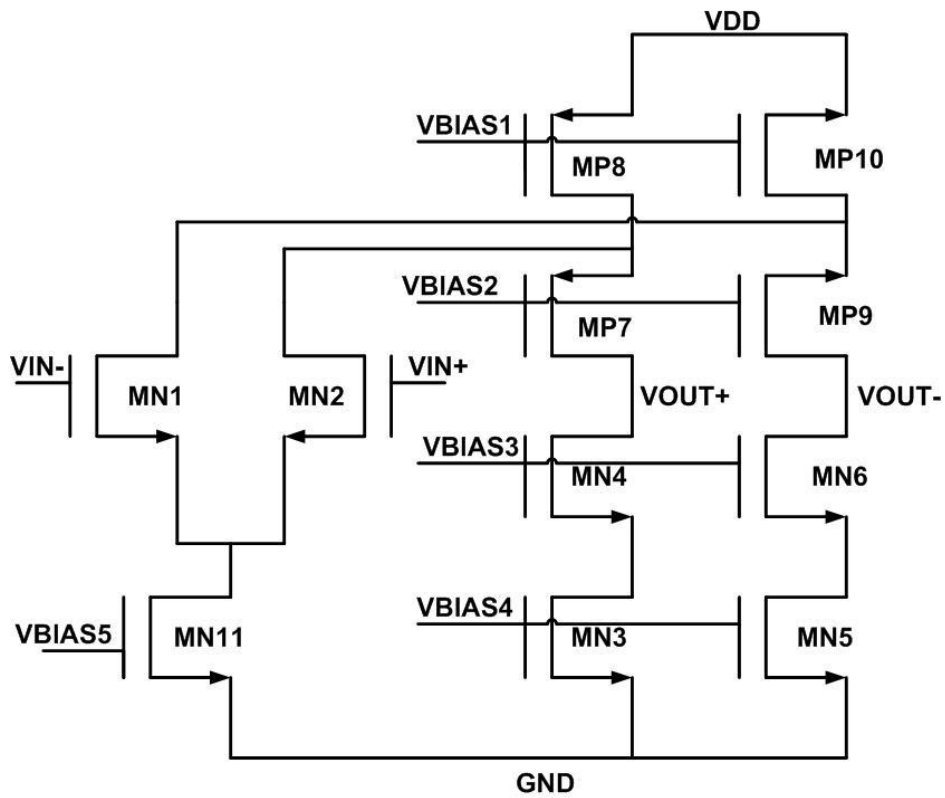


Figure 3

- 6 . Figure 3 shows the design of CMOS folded cascode configuration.
- (a) Design continuous CMFB circuit to get stable output voltage. (10 marks)
- (b) Explain how your CMFB circuit operations. (10 marks)