

UNIVERSITI SAINS MALAYSIA

Peperiksaan Semester Pertama
Sidang Akademik 1995/96

Oktober - November 1995

EEE 441 - Elektronik Kuasa

Masa : [3 jam]

ARAHAN KEPADA CALON :

Sila pastikan bahawa kertas peperiksaan ini mengandungi 12 muka surat bercetak dan **ENAM (6)** soalan sebelum anda memulakan peperiksaan ini.

Jawab **LIMA (5)** soalan.

Agihan markah bagi soalan diberikan di sut sebelah kanan soalan berkenaan.

Jawab semua soalan di dalam Bahasa Malaysia.

...2/-

1. (a) Apakah langkah-langkah yang terlibat di dalam rekabentuk peralatan elektronik kuasa?

What are the steps involved in designing power electronics equipment?

(15%)

- (b) Apakah kesan-kesan sampingan dari peralatan elektronik kuasa?

What are the peripheral effects of power electronics equipment?


(15%)

- (c) Bentuk gelombang pulihan TUTUP (turn off) suatu peranti ditunjukkan oleh Rajah 1-1. Jika Q_{rr} ialah cas pulihan seperti ditunjukkan oleh kawasan lorekan, I_{RM} ialah arus balikan puncak, t_{rr} ialah masa pulih balikan dan t_1, t_2 merupakan bahagian dari t_{rr} . Terbitkan ungkapan untuk t_{rr} dan I_{RM} dalam sebutan Q_{rr} dan di/dt untuk pulihan pentas dan pulihan lembut.

The waveforms for turnoff recovery of a device is shown in Figure 1-1. If Q_{rr} is the recovered charge shown in the shaded area, I_{RM} is the peak reverse current, t_{rr} is the reverse recovery time, and time t_1 and t_2 are subdivisions of t_{rr} . Derive the expressions for t_{rr} and I_{RM} in term of Q_{rr} and di/dt for abrupt recovery and a very soft recovery.

(40%)

...3/-

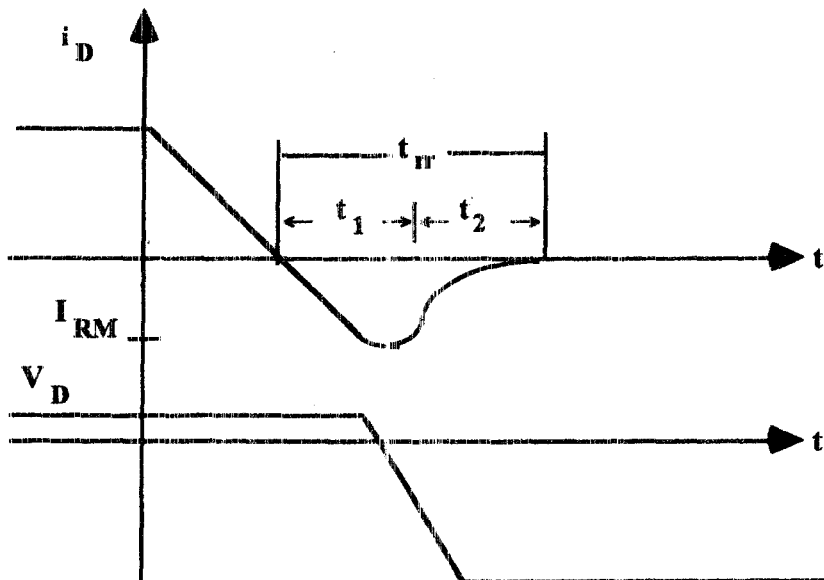

Rajah 1-1

Figure 1-1


- (d) Peranti BJT dikendalikan untuk suatu kala dan kehilangan pensuisannya ditunjukkan oleh Rajah 1-2. Nilai $r(t)$ boleh ditentukan dari Rajah 1-3.

Diberi: $R_{JC} = 0.8^{\circ}\text{C/W}$, $R_{CS} = 0.5^{\circ}\text{C/W}$, dan $T_A = 85^{\circ}\text{C}$.
Tentukan:


A BJT is operated in a periodic manner with the losses as shown in Figure 1-2. The value of $r(t)$ may be determined from Figure 1-3, $R_{JC} = 0.8^{\circ}\text{C/W}$, $R_{CS} = 0.5^{\circ}\text{C/W}$, and $T_A = 85^{\circ}\text{C}$. Find:

- (i) Nilai puncak ($T_J - T_C$)
the peak value of $(T_J - T_C)$, and
- (ii) Nilai R_{SA} supaya nilai puncak T_J dihadkan kepada 150°C .
the value of R_{SA} that limit the peak value of T_J at 150°C .

...4/-

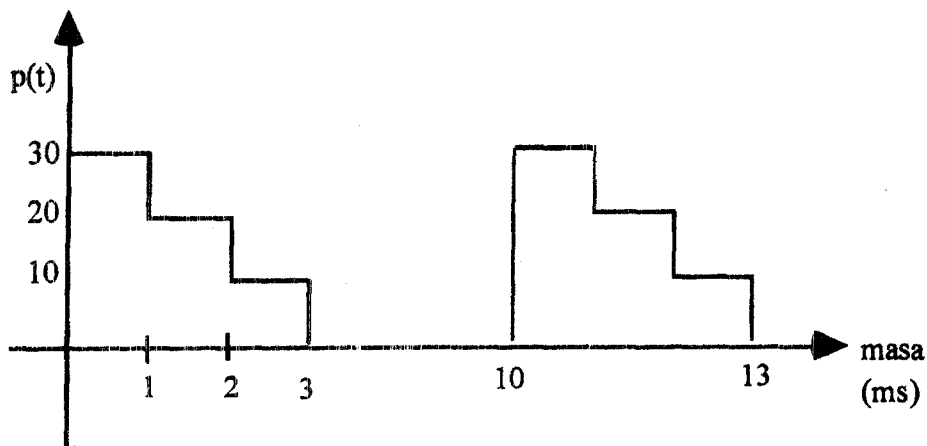

Rajah 1-2
Figure 1-2

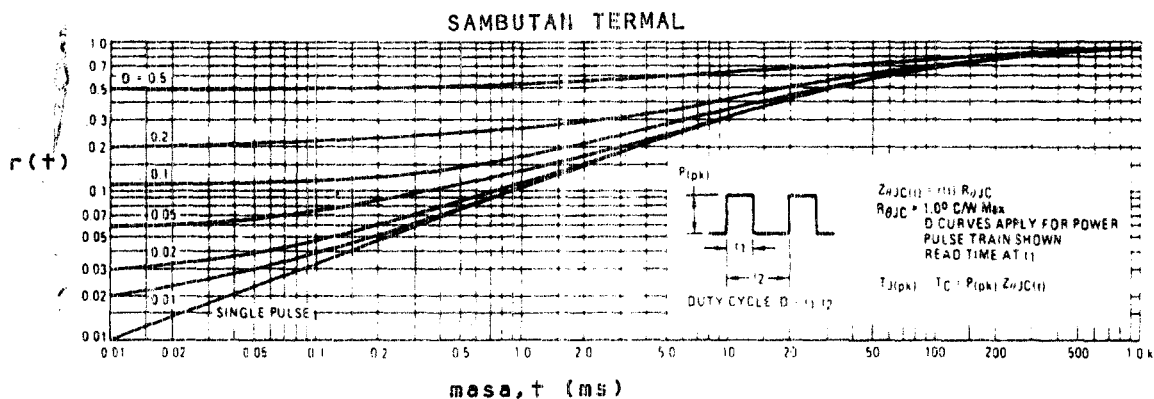

Rajah 1-3
Figure 1-3

(30%)

2. (a) **Apakah ciri v-i bagi thiristor?**
Apakah model dua transistor bagi thiristor?

Explain what is the v-i characteristic of thyristors?
Explain what is the two transistors model of thyristors?

(30%)

...5/-

- (b) **Apakah kaedah-kaedah untuk menghidupkan thiristor?
Apakah tujuan kawalan di/dt dan dv/dt ?**


What are the means of turning-on thyristors?

What are the purpose of di/dt and dv/dt protections?

(40%)


- (c) **Litar mudah untuk menghidupkan thiristor ditunjukkan oleh Rajah 2-1. Bentuk gelombang arus dan voltan untuk proses tersebut ditunjukkan oleh Rajah 2-2. Diberi: $E = 100\text{ V}$, $R = 10\ \Omega$, $C = 4\ \mu\text{F}$ dan $t_q = 30\ \mu\text{s}$. Adakah thiristor tersebut berada dalam keadaan pincang balikan yang mencukupi supaya berlaku 'turn-off'.**

A simple circuit to turn off thyristor is shown in Figure 2-1. The current and voltage waveform for the process is shown in Figure 2-2. In Figure 2-1, $E = 100\text{ volts}$, $R = 10\ \Omega$, $C = 4\ \mu\text{F}$ and required $t_q = 30\ \mu\text{s}$. Is the thyristor reverse biased long enough for turn-off to occur? Describe why?

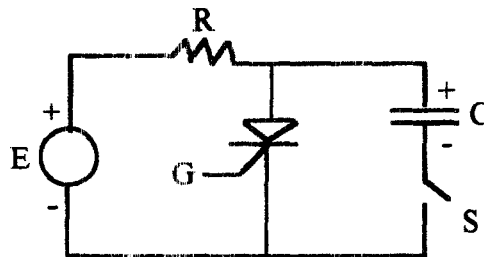

Rajah 2-1

Figure 2-1

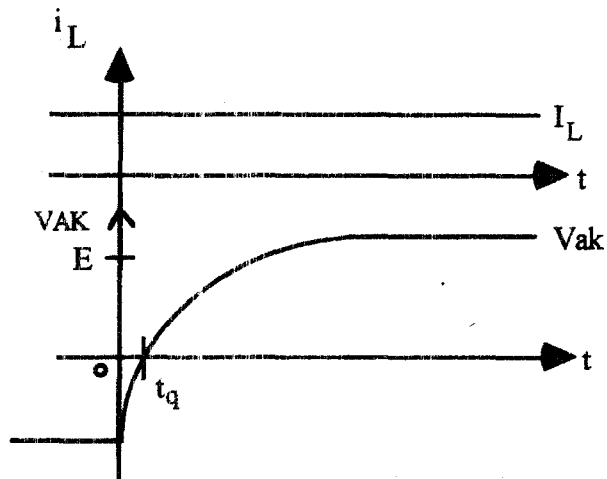

Rajah 2-2

Figure 2-2

(30%)

3. (a) Terangkan operasi bagi semikonverter satu fasa?
Terbitkan persamaan untuk voltan keluaran purata dan rms bagi semikonverter satu fasa.

Explain the operation of a single phase semiconverter? Derive the expressions for the average and rms output voltages of a single phase semiconverter.


(40%)

...7/-

- (b) Konverter penuh tiga fasa di dalam Rajah 3 dikendalikan dari punca 3 fasa sambungan Y 208V, 60Hz dan rintangan beban ialah $R = 10\Omega$. Jika voltan keluaran purata yang diperlukan ialah 60% dari voltan keluaran maksimum, kirakan:

A three phase full converter in Figure 3 is operated from a three phase Y connected 208V, 60Hz supply and the load resistance is $R = 10\Omega$. If it is required to obtain an average output voltage of 60% of the maximum possible output voltage, calculate.

- (i) sudut lengah α
the delay angle α ,
- (ii) arus keluaran rms
the rms output current,
- (iii) arus keluaran purata, dan
the average output current, and
- (iv) kecekapan penukaran
the rectification efficiency.

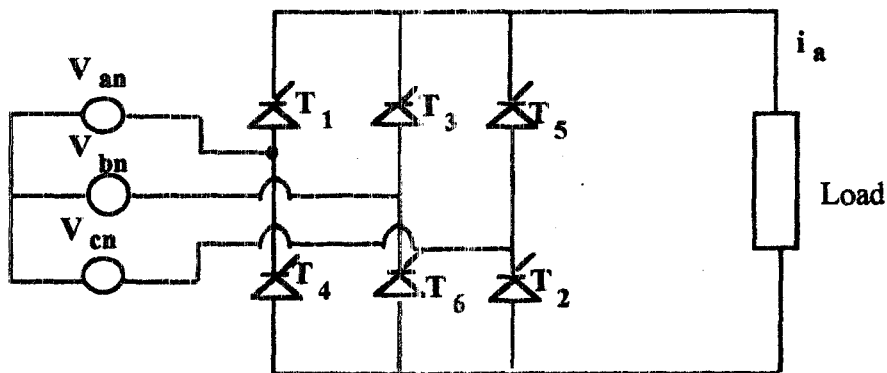

Rajah 3
Figure 3

(60%)
...8/-

4. (a) Apakah parameter-parameter keupayaan bagi pemenggal?

What are the performance parameters of a chopper?

(20%)

(b) Bagi pemenggal Buck seperti ditunjukkan oleh Rajah 4 terbitkan:

For the Buck Chopper shown in Figure 4 derive:

(i) hubungan voltan keluaran, dan
the output voltage relation, and

(ii) hubungan arus maksimum I_{max} dan arus minimum
 I_{min} .
circuit current relation, I_{max} and I_{min} .

(40%)

(c) Pemenggal Buck, seperti ditunjukkan oleh Rajah 4, dikendalikan pada 10kHz, membekalkan 100W pada 12V ke beban dari punca 20V. Tentukan:


A Buck Chopper as shown in Figure 4, operating at 10kHz, supplies 100W at 12V to a load from a 20V source. Find:

(i) nilai induktans untuk arus induktor yang berterusan
the inductance for continuous inductor current

(ii) $I_{mak} - I_{min}$, dan
 $I_{max} - I_{min}$, and

(iii) nilai kapasitans yang diperlukan supaya $\Delta V_c = 0.1V$.
the value of capacitance needed for $\Delta V_c = 0.1V$.

...9/-

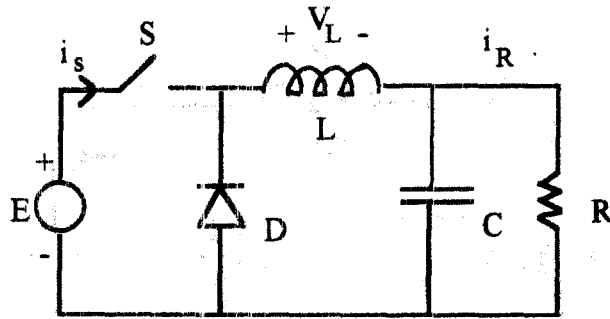

Rajah 4

Figure 4

(40%)

5. (a) Huraikan kawalan BUKA-TUTUP dalam kawalan ac.
Explain the ON-OFF control in ac controller.

(20%)

- (b) Pengawal voltan ac satu fasa separuh gelombang di dalam Rajah 5-1 mempunyai beban perintang $R = 20\Omega$ dan voltan masukan $V_s = 208V(\text{rms})$, 60Hz. Jika kuasa keluaran $P_o = 2kW$ diperlukan.


The single-phase half wave ac voltage controller in Figure 5-1 has a resistive load of $R = 20\Omega$ and the input voltage is $V_s = 208V(\text{rms})$, 60Hz. If the desired output power is $P_o = 2kW$.

- (i) Terbitkan persamaan sudut lengah dalam sebutan α
Derive the equation for delay angle in term of α

- (ii) Kira faktor kuasa masukan PF (Jika $\alpha = \frac{\pi}{2}$)
Find the input power factor PF (if $\alpha = \frac{\pi}{2}$).

(40%)

...10/-

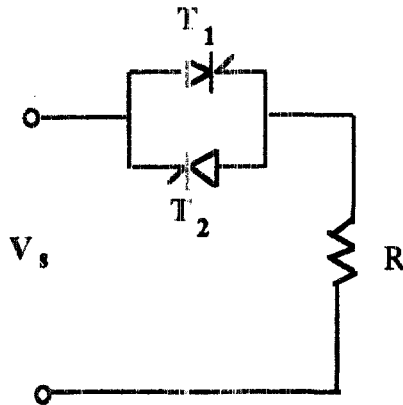

Rajah 5-1

Figure 5-1


- (c) Litar di dalam Rajah 5-2 dikawal oleh penukar tap sinkronis. Voltan utama ialah 240V (rms), 60 Hz. Voltan sekunder ialah $V_1 = 120V$ dan $V_2 = 100V$. Jika beban perintang $R = 25\Omega$, voltan beban rms ialah 200V dan $\alpha = 95^\circ$, tentukan.

The circuit in Figure 5-2 is controlled as a synchronous tap changer. The primary voltage is 240V (rms), 60Hz. The secondary voltages are $V_1 = 120V$ and $V_2 = 100V$. If the load resistance is $R = 25\Omega$, the rms load voltage is 200V, and $\alpha = 95^\circ$, determine

- (i) arus rms thiristor T_1 dan T_2 ,
the rms current of Thyristor T_1 and T_2 .
- (ii) arus rms thiristor T_3 dan T_4
the rms current of Thyristor T_3 and T_4 , and
- (iii) faktor kuasa masukan, PF.
the input power factor PF.

(40%)

...11/-

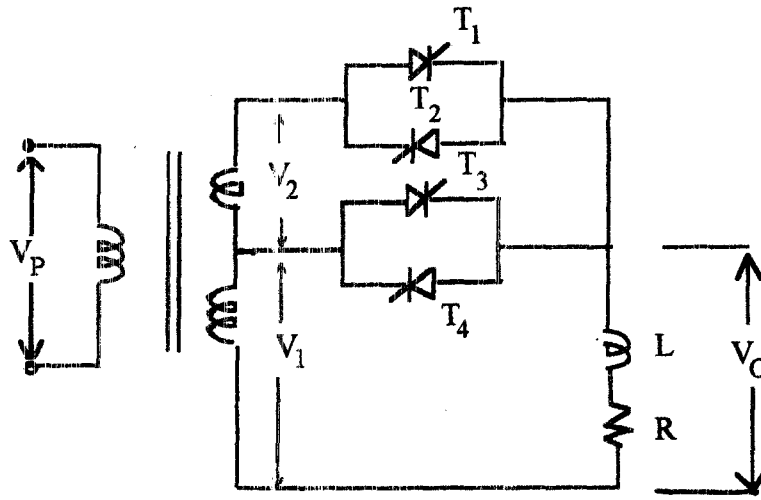

Rajah 5-2
Figure 5-2

6. (a) **Apakah prinsip operasi bagi suatu inverter?
Apakah fungsi diod suapbalik di dalam litar inverter?**

*Describe is the principle of operation of an inverter?
What are the purposes of feedback diodes in inverter?*

(30%)

- (b) **Apakah kaedah untuk menghasilkan voltan keluaran tiga fasa dari
suatu litar inverter? Terangkan untuk pengaliran 180°.**

*What are the arrangements for obtaining three phase output voltages? Explain
for 180 degree conduction.*

(40%)

...12/-

- (c) **Apakah kaedah-kaedah untuk mengawal voltan di dalam inverter satu fasa. Terangkan dua dari kaedah-kaedah yang digunakan.**

What are the methods for voltage control within the inverters? Explain two of the techniques used.

(30%)

..ooo0ooo-