
UNIVERSITI SAINS MALAYSIA

First Semester Examination
2012/2013 Academic Session

January 2013

EEE 241 – ANALOG ELECTRONIC I
[ELEKTRONIK ANALOG I]

Duration : 3 hours

[Masa : 3 jam]

Please check that this examination paper consists of NINE (9) pages of printed material before you begin the examination.

[Sila pastikan bahawa kertas peperiksaan ini mengandungi SEMBILAN (9) mukasurat bercetak sebelum anda memulakan peperiksaan ini.]

Instructions: This question paper consists SIX (6) questions. Answer **FIVE** (5) questions. All questions carry the same marks.

Arahan: *Kertas soalan ini mengandungi ENAM (6) soalan. Jawab **LIMA** (5) soalan. Semua soalan membawa jumlah markah yang sama.]*

In the event of any discrepancies, the English version shall be used.

[Sekiranya terdapat sebarang percanggahan pada soalan peperiksaan, versi Bahasa Inggeris hendaklah digunapakai.]

1. Lukis model isyarat-kecil bagi transistor NMOS dengan nilai-nilai $I_D = 150 \mu\text{A}$, $V_{SB} = 1 \text{ V}$, $V_{DS} = 2.5 \text{ V}$. Parameter-parameter peranti diberikan: $\phi_f = 0.3 \text{ V}$, $W = 20 \mu\text{m}$, $L = 1.5 \mu\text{m}$, $\gamma = 0.5 \text{ V}^{1/2}$, $k' = 200 \mu\text{A/V}^2$, $\lambda = 0.02 \text{ V}^{-1}$, $t_{ox} = 100 \text{ angstroms}$, $\psi_o = 0.6 \text{ V}$, $C_{sb0} = C_{db0} = 10 \text{ fF}$. Kapasitan bertindih daripada *gate to source* dan *gate to drain* bernilai 1 fF . Anggarkan $C_{gb} = 5 \text{ fF}$.

Draw the complete small-signal model for an NMOS transistor with $I_D = 150 \mu\text{A}$, $V_{SB} = 1 \text{ V}$, $V_{DS} = 2.5 \text{ V}$. Device parameters are: $\phi_f = 0.3 \text{ V}$, $W = 20 \mu\text{m}$, $L = 1.5 \mu\text{m}$, $\gamma = 0.5 \text{ V}^{1/2}$, $k' = 200 \mu\text{A/V}^2$, $\lambda = 0.02 \text{ V}^{-1}$, $t_{ox} = 100 \text{ angstroms}$, $\psi_o = 0.6 \text{ V}$, $C_{sb0} = C_{db0} = 10 \text{ fF}$. Overlap capacitance from gate to source and gate to drain is 1 fF . Assume $C_{gb} = 5 \text{ fF}$.

(20 markah/marks)

2. (a) Merujuk kepada Rajah 1, nyatakan sama ada C_1, C_2 dan C_3 adalah kapasitor gandingan atau pirau. Apakah kegunaan kapasitor-kapasitor ini?


Referring to Figure 1, state whether C_1, C_2 and C_3 are coupling or bypass capacitors. What are the applications of these capacitors?

(6 markah/marks)

- (b) Kirakan gandaan voltan bagi penguat pemancar- sepunya dalam Rajah 1 dengan dan tanpa kapasitor C_2 , jika transistor mempunyai $\beta_o = 150$, $\beta_F = 160$, $V_T = 26 \text{ mV}$ dan $V_{BE} = 0.7 \text{ V}$.

Calculate the voltage gain of the common-emitter amplifier in Figure 1 with and without capacitor C_2 , if the transistor has $\beta_o = 150$, $\beta_F = 160$, $V_T = 26 \text{ mV}$ and $V_{BE} = 0.7 \text{ V}$.


(14 markah/marks)

 

Rajah 1
Figure 1

3. Merujuk kepada Rajah 2, transistor dwikutub kaskod yang mengandungi pemancar-sepunya menjana tapak-sepunya diberikan. Ciri-ciri penting di dalam menganalisa litar ini adalah rintangan masukan R_i , rintangan keluaran R_o , kealiran pindah G_m , dan gandaan voltan A_v . Andaikan rintangan tapak r_b diabaikan.

In Figure 2, the bipolar cascode transistor that constitutes the common-emitter driving the common-base is shown. The key characteristics in analyzing this circuit are the input resistance R_i , output resistance R_o , system transconductance G_m , and the voltage gain A_v . Assume that base resistance r_b is negligible.

 

Rajah 2
Figure 2

- (a) Lukis litar setara isyarat kecil menggunakan model π . Tandakan litar sepenuhnya.

Draw the small signal equivalent circuit using π -model. Label the circuit completely.

(5 markah/marks)

- (b) Cari rintangan masukan R_i , dan sistem kealiran pindah G_m .

Find input resistance R_i , and the system transconductance G_m .

(10 markah/marks)


...5/-

(c) Cari gandaan voltan A_v .

Find the voltage gain A_v .

(5 markah/marks)

4.

 

Rajah 3

Figure 3

Rajah 3 menunjukkan pengkamil dengan gandaan operasi bergadaan A_{OL} .

Figure 3 shows integrator with operational amplifier has the gain of A_{OL} .

(a) Hasilkan pengkamil persamaan pindah dengan A_{OL} .

Derive integrator transfer function with finite A_{OL} .


(5 markah/marks)

- (b) Jika R adalah $1k\Omega$ and $1\mu F$ kirakan peratus perbezaan keluaran magnitude jika A_{OL} adalah 10 dan 100.

If R is $1k\Omega$ and C is $1\mu F$ calculate percentage deviation of the output magnitude if A_{OL} is 10 and 100.

(15 markah/marks)

5.

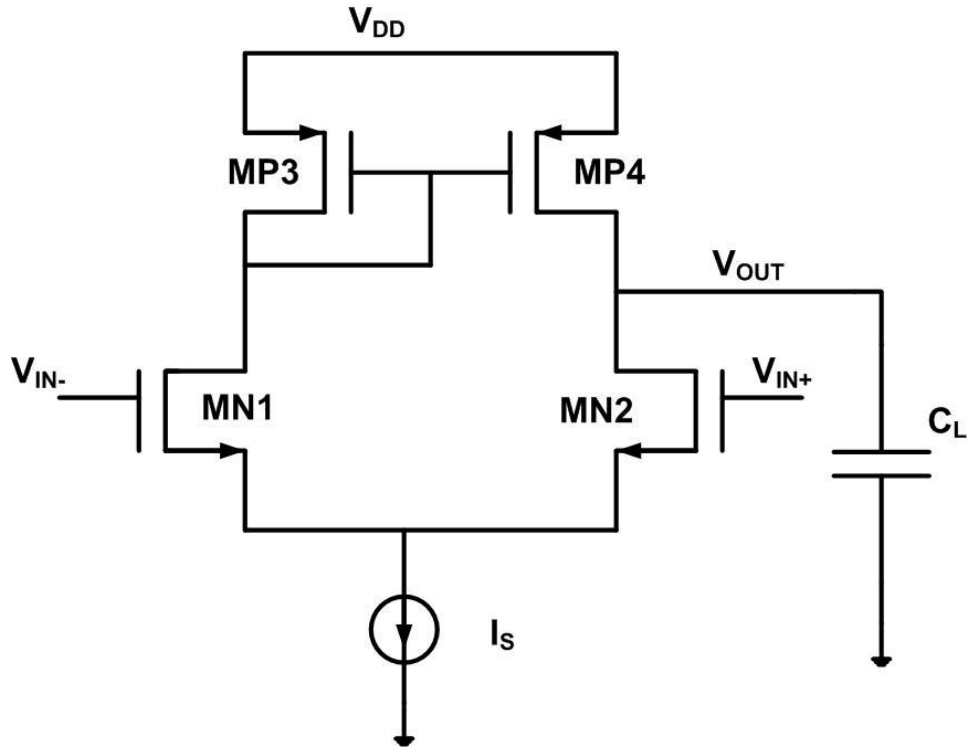

Rajah 4

Figure 4

Diagram di dalam Rajah 4 menunjukkan CMOS OTA. Jika k_n adalah $20 \frac{\mu A^2}{V}$, k_p adalah $20 \frac{\mu A^2}{V}$, W_1, W_2 is 50um, $W_3, W_4, L_1, L_2, L_3, L_4 = 5um$. I_S adalah $10\mu A$, $\lambda = 0.1$ $C_L = 1pf$.

Diagram in Figure 4 is Simple CMOS OTA. If k_n is $20 \frac{\mu A^2}{V}$, k_p is $20 \frac{\mu A^2}{V}$, W_1, W_2 is 50um, $W_3, W_4, L_1, L_2, L_3, L_4 = 5um$. I_S is $10\mu A$, $\lambda = 0.1$ $C_L = 1pf$.

- (a) Cari nilai transkonduktan g_{m1} .

Find transconductance g_{m1} .

(5 markah/marks)

- (b) Hitungkan frekuensi tiang dominan

Calculate dominant pole frequency.

(10 markah/marks)

- (c) Kira gadaan jalur lebar.

Calculate the Gainbandwidth.

(5 markah/marks)

6. Rajah 5 menunjukkan MN1 pintu dihubungkan ke parit.

Figure 5 shown MN1 has gate connected to the drain.

- (a) Lukis isyarat kecil litar.


Draw small signal equivalent circuit.

(10 markah/marks)

- (b) Dapatkan persamaan R_{out} .

Derive the expression of R_{out} .

(10 markah/marks)

 

Rajah 5

Figure 5

ooooOoooo