
UNIVERSITI SAINS MALAYSIA

Second Semester Examination

2012/2013 Academic Session

June 2013

EEE 270 – ANALOGUE ELECTRONIC II
[ELEKTRONIK ANALOG II]

Duration : 3 hours

[Masa : 3 jam]

Please check that this examination paper consists of **SEVEN (7)** pages printed material and **TWO (2)** pages of Appendices before you begin the examination.

*[Sila pastikan bahawa kertas peperiksaan ini mengandungi **SEVEN (7)** mukasurat bercetak beserta Lampiran **DUA (2)** muka surat bercetak sebelum anda memulakan peperiksaan ini.]*

Instructions: Answer **FIVE (5)** questions. Answer **TWO (2)** questions in Section A and **TWO (2)** questions from Section B and **ONE (1)** question from any section.

Arahan: Jawab **LIMA (5)** soalan. Jawab **DUA (2)** soalan dalam Bahagian A dan **DUA (2)** soalan dalam Bahagian B dan **SATU (1)** soalan daripada mana-mana Bahagian.]

Use separate answer booklets for **Section A** and **Section B**.

*[Gunakan dua buku jawapan yang berasingan bagi **Bahagian A** dan **Bahagian B**.]*

In the event of any discrepancies, the English version shall be used.

[Sekiranya terdapat sebarang percanggahan pada soalan peperiksaan, versi Bahasa Inggeris hendaklah digunapakai.]

BAHAGIAN A

PART A

1. Rekabentuk satu litar aktif kutub-tunggal penapis jalur-rendah menggunakan op amp dengan nilai $f_H = 2$ kHz, $R_{in} = 5$ k Ω dan $A_v = 40$ dB. Kemudian pilih nilai R dan C yang terdekat daripada Appendix A dan kira nilai akhir f_H . Lukiskan dan nyatakan rumus untuk nilai $A_v(s)$ litar berkenaan.

Design an active single-pole low-pass filter using an op amp with $f_H = 2$ kHz, $R_{in} = 5$ k Ω and $A_v = 40$ dB. Then pick the closest values for R and C from the Appendix A and recalculate the final f_H . Draw and give the expression of $A_v(s)$ for the mentioned circuit.

(20 markah/marks)


2. Rajah 2(a)(b) menunjukkan penguat kendalian (op amp) tidak menyongsang dan juga rangkaian dua-terminal setara bagi pengiraan rintangan keluaran. Buktikan bahawa:

Figure 2(a)(b) shows the non-inverting operational amplifier (op amp) and its equivalent two-port network to find the output resistance. Prove that:

- (a) Bagi kes op amp yang ideal, rintangan keluaran adalah kosong, dan
For ideal op amp, the output resistance is zero, and
- (b) Bagi kes op amp yang tidak ideal, rintangan keluaran mempunyai nilai tertentu.
For non-ideal op amp, the output resistance is having a value.

Gunakan andaian-andaian yang bersesuaian bagi kedua-dua kes.
Apply suitable assumptions for both cases.

(20 markah/marks)

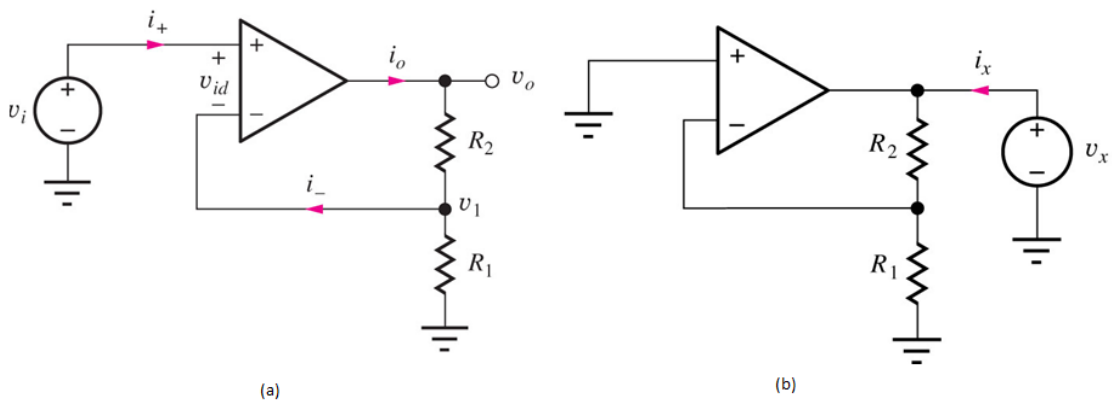

Rajah 2(a): Penguat kendalian tidak menyongsang

Rajah 2(b): Rangkaian dua-terminal setara untuk pengiraan R_{out}

Figure 2(a): Non-inverting amplifier

Figure 2(b): Equivalent two-port network to calculate R_{out}

3. Untuk op amp dengan gandaan dc bernilai 200,000 dan frekuensi gandaan-tunggal bernilai 500 kHz, cari:

For an op amp with a dc gain of 200,000 and unity-gain frequency of 500 kHz, find:

- (a) Apakah frekuensi potong bagi op amp tersebut?
What is the cut-off frequency of op amp?
- (b) Jika op amp digunakan untuk merekabentuk litar penguat penyongsang dengan gandaan gelung-tertutup bernilai 40 dB, apakah lebar jalur penguat penyongsang tersebut?

If the op amp is used to build an inverting amplifier with a closed-loop gain of 40 dB, what is the bandwidth of the feedback amp?

- (c) Berikan ungkapan fungsi pindah bagi op amp.
Write an expression for the transfer function of the op amp.


- (d) Berikan ungkapan fungsi pindah litar penguat penyongsang.

Write an expression for the transfer function of the inverting amplifier.

(20 markah/marks)

BAHAGIAN B

PART B

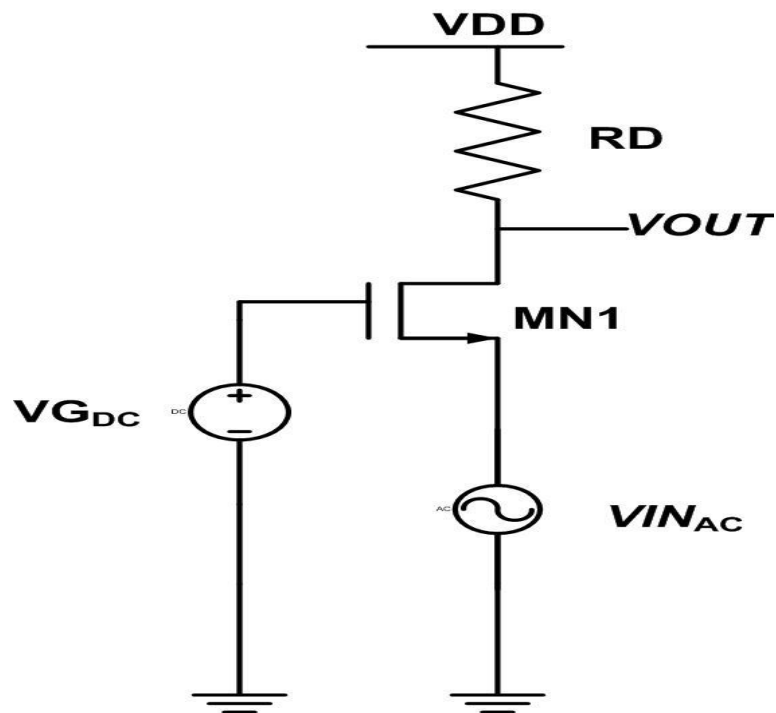

Rajah 4

Figure 4

4. (a) Cari persamaan masukan rintangan dalam Rajah 4.


Derive input resistance in Figure 4.

(10 markah/marks)

(b) Terbitkan persamaan jumlah gandaan.

Derive Total gain expression.

(10 markah/marks)

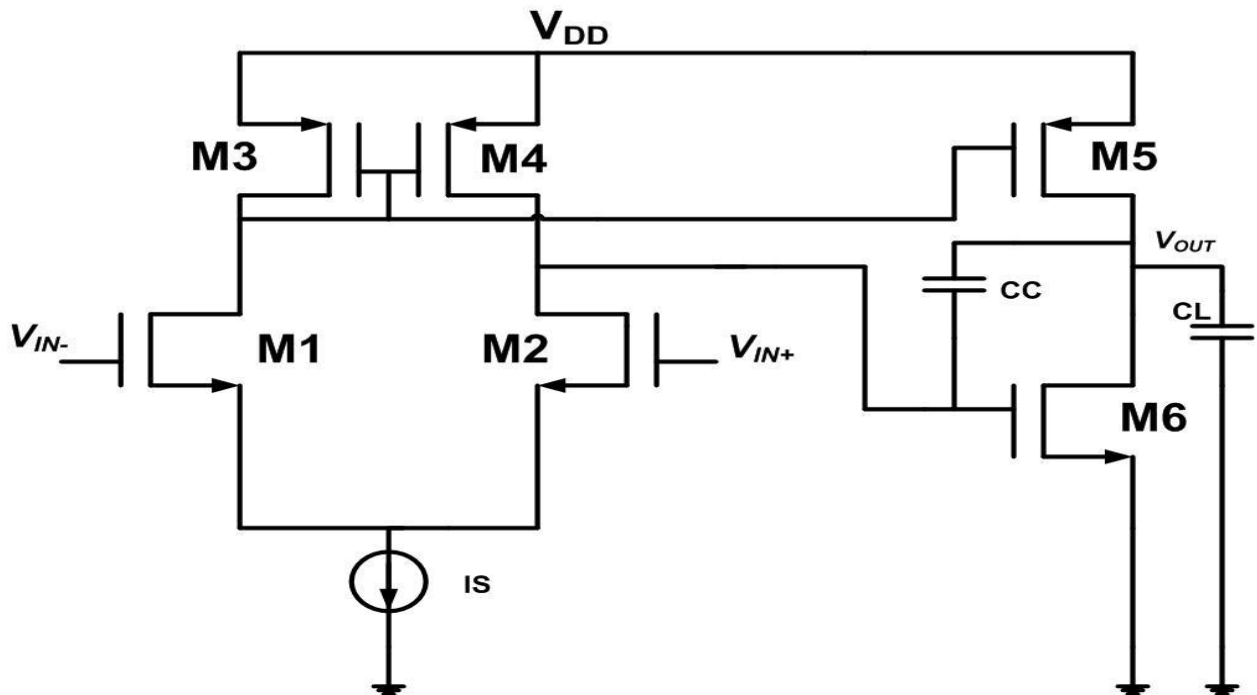

Rajah 5

Figure 5

5. Rajah 5 diatas menunjukkan konfigurasi gandaan 2 peringkat.

Figure 5 shows a 2 gain configuration stape.

(a) Terbitkan gandaan lebarjalur

Derive gainbandwidth (GBW)

(5 markah/marks)

(b) Kira nisbah g_{m1} dan g_{m6} jika fasa julat adalah 75 darjah.


Calculate the ratio g_{m1} and g_{m6} if the phase margin is 75 degrees.

(5 markah/marks)

(c) Kira g_{m1} jika $V_{DD}=5V$, $I_{D2} = 1mA$.

Calculate g_{m1} if $V_{DD}=5V$, $I_{D2} = 1mA$.

(10 markah/marks)

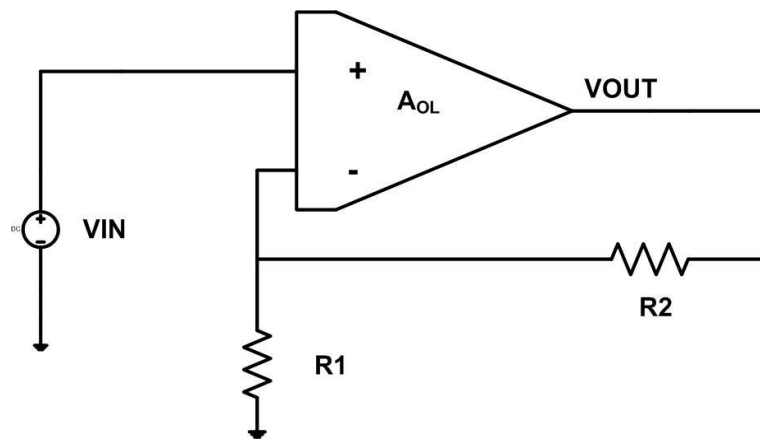

Rajah 6

Figure 6

6. Rajah 6 diatas menunjukkan konfigurasi gandaan tak menyongsang.

Figure 6 shows the noninverting configuration.

(a) Kira nilai gandaan tertutup jika $R_2 = 9 \text{ kohm}$, $R_1 = 1 \text{ kohm}$ dan gandaan terbuka = 1000 .

Calculate closed loop gain if $R_2 = 9 \text{ kohm}$ and $R_1 = 1 \text{ kohm}$ and openloop gain = 1000.

(10 markah/marks)

...7/-

- (b) Kira masa selesai jika konfigurasi tak menyongsang ini diubah kepada konfigurasi gandaan satu.

Calculate the settling time if noninverting configuration change to unity gain configuration.

(10 markah/marks)

oooOooo

Appendix A

The following are the standard resistor values available in carbon film with a 2 or 5percent tolerance. Values are in Ohms with K = 1,000 and M = 1,000,000.

1.0	10	100	1.0K	10K	100K	1.0M	10M
1.1	11	110	1.1K	11K	110K	1.1M	11M
1.2	12	120	1.2K	12K	120K	1.2M	12M
1.3	13	130	1.3K	13K	130K	1.3M	13M
1.5	15	150	1.5K	15K	150K	1.5M	15M
1.6	16	160	1.6K	16K	160K	1.6M	16M
1.8	18	180	1.8K	18K	180K	1.8M	18M
2.0	20	200	2.0K	20K	200K	2.0M	20M
2.2	22	220	2.2K	22K	220K	2.2M	22M
2.4	24	240	2.4K	24K	240K	2.4M	
2.7	27	270	2.7K	27K	270K	2.7M	
3.0	30	300	3.0K	30K	300K	3.0M	
3.3	33	330	3.3K	33K	330K	3.3M	
3.6	36	360	3.6K	36K	360K	3.6M	
3.9	39	390	3.9K	39K	390K	3.9M	
4.3	43	430	4.3K	43K	430K	4.3M	
4.7	47	470	4.7K	47K	470K	4.7M	
5.1	51	510	5.1K	51K	510K	5.1M	
5.6	56	560	5.6K	56K	560K	5.6M	
6.2	62	620	6.2K	62K	620K	6.2M	
6.8	68	680	6.8K	68K	680K	6.8M	
7.5	75	750	7.5K	75K	750K	7.5M	
8.2	82	820	8.2K	82K	820K	8.2M	
9.1	91	910	9.1K	91K	910K	9.1M	

The following are standard capacitor values. Values below 1 uF are generally available with a 5 or 10 percent tolerance. Values over 1 uF are generally available with a 10 or 20 percent tolerance. Values are in Farads with p = pico, n = nano, u = micro, and m = milli.

1p	10p	100p	1.0n	10n	100n	1.0u	10u	100u	1.0m	10m
	12p	120p	1.2n	12n	120n	1.2u				
1.5p	15p	150p	1.5n	15n	150n	1.5u	15u	150u	1.5m	15m
	18p	180p	1.8n	18n	180n	1.8u				
2.2p	22p	220p	2.2n	22n	220n	2.2u	22u	220u	2.2m	22m
	27p	270p	2.7n	27n	270n	2.7u				
3.3p	33p	330p	3.3n	33n	330n	3.3u	33u	330u	3.3m	33m
	39p	390p	3.9n	39n	390n	3.9u				
4.7p	47p	470p	4.7n	47n	470n	4.7u	47u	470u	4.7m	47m
	56p	560p	5.6n	56n	560n	5.6u				
6.8p	68p	680p	6.8n	68n	680n	6.8u	68u	680u	6.8m	68m
	82p	820p	8.2n	82n	820n	8.2u				