
UNIVERSITI SAINS MALAYSIA

Peperiksaan Semester Pertama
Sidang Akademik 2005/2006

November 2005

EEU 202 – ELEKTRONIK UNTUK JURUTERA

Masa : 2 Jam

ARAHAN KEPADA CALON:-

Sila pastikan kertas peperiksaan ini mengandungi **SEPULUH (10)** muka surat beserta **Lampiran (3 mukasurat)** bercetak dan **LIMA (5)** soalan sebelum anda memulakan peperiksaan ini.

Jawab **EMPAT (4)** soalan.

Agihan markah diberikan di sudut sebelah kanan soalan berkenaan.

Semua soalan hendaklah dijawab di dalam Bahasa Malaysia.

...2/-

Soalan 1


- (a) Berikan dua contoh unsur yang boleh ditambahkan ke silikon tulen untuk menghasilkan semikonduktor jenis N. (Sila rujuk jadual berkala yang dilampirkan.) Secara ringkas, terangkan mengapa unsur-unsur ini dipilih.

Give two examples of element that can be added to the intrinsic (pure) silicon to create an N-type semiconductor. (Please refer to the periodic table attached.) In brief, describe why these elements are chosen.

(10%)

- (b) Apakah yang diwakili oleh simbol-simbol dalam Rajah 1 ini.

What do these symbols present in Figure 1?

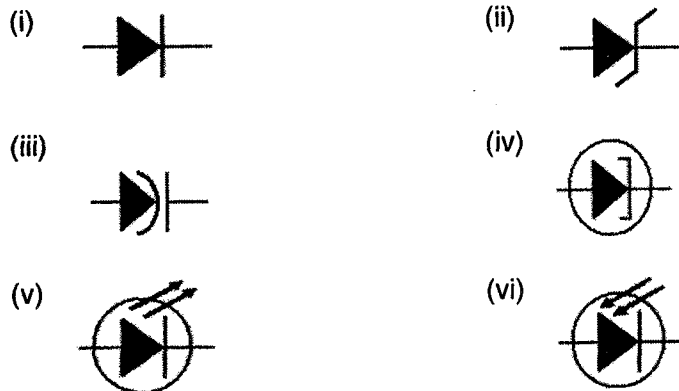

Rajah 1
Figure 1


(30%)

- (c) Bagi setiap litar dalam Rajah 2 berikut, tentukan nilai kejatuhan voltan merentasi R_L , V_{OUT} . D1 ialah diod 1N4004, manakala D2 ialah diod 1N4740AT. (Sila rujuk helaian-helaian data yang dilampirkan untuk menyelesaikan masalah ini).


For each of these circuits in Figure 2, determine the value of the voltage across R_L , V_{OUT} . D1 is a 1N4004 diode, while D2 is a 1N4740AT diode. (Please refer to the datasheets attached to solve this problem).

...3/-


(i)

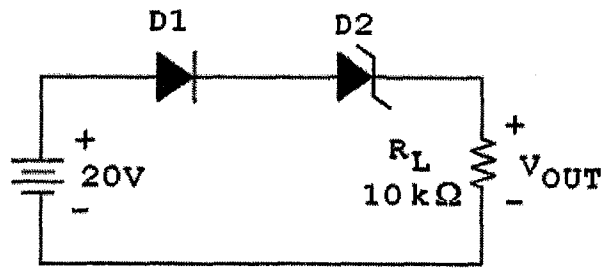


(ii)

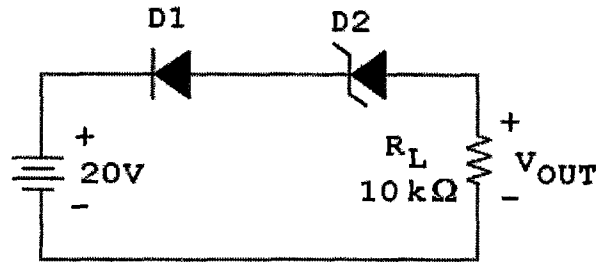


(iii)

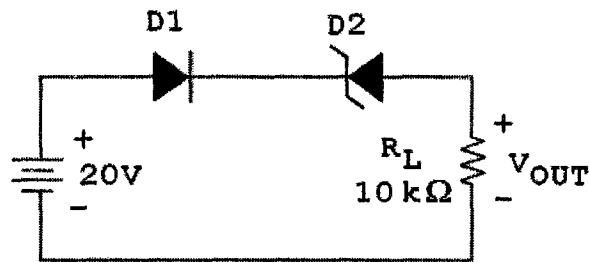

(iv)

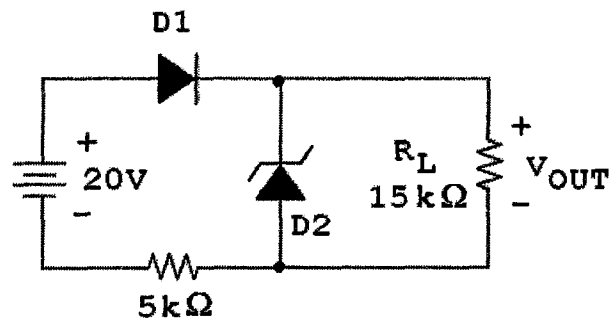


(v)

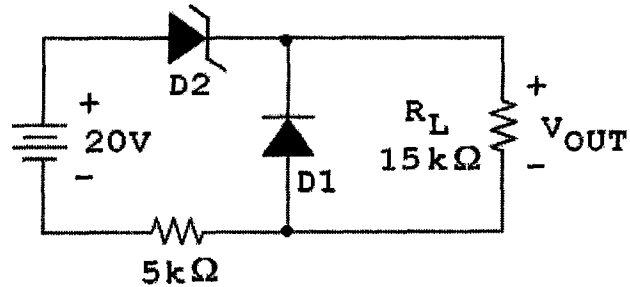

Rajah 2
Figure 2

(60%)
...4/-

Soalan 2

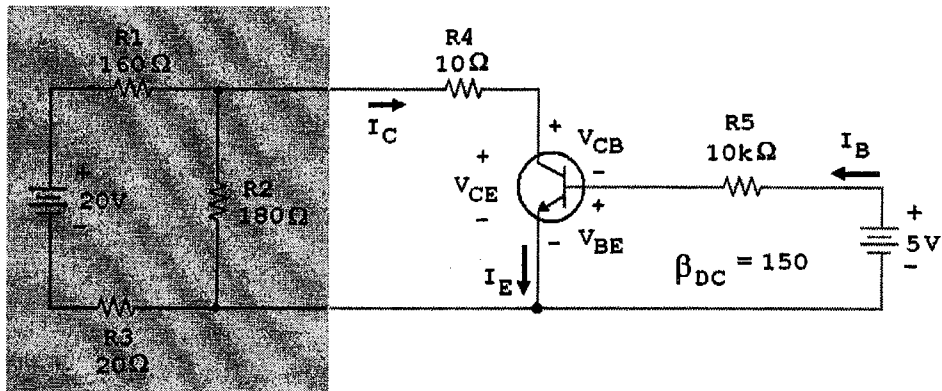

A

Rajah 3
Figure 3

- (a) Lukiskan semula litar Rajah 3 di atas dengan menggantikan litar di dalam kotak A dengan litar setara Thevenin. Tentukan nilai:

Redraw the circuit in Figure 3 above by changing the circuit in box A with a Thevenin equivalent circuit. Determine the value of:

- (i) Voltan setara Thevenin, V_{TH} .
Thevenin equivalent voltage, V_{TH} .
- (ii) Rintangan setara Thevenin, R_{TH} .
Thevenin equivalent resistance, R_{TH} .

(30%)

- (b) Tentukan nilai I_B , I_C , I_E , V_{BE} , V_{CE} , dan V_{CB} .
Determine the value of I_B , I_C , I_E , V_{BE} , V_{CE} , dan V_{CB} .

(60%)

- (c) Tentukan nilai kuasa yang dilesapkan oleh perintang R5.
Determine the power dissipated by resistor R5.

(10%)

...5/-

Soalan 3


- (a) Lukiskan model litar setara op-amp bagi Rajah 4 di bawah.

Draw an equivalent circuit model of op-amp shown in the Figure 4 below.

(10%)

- (b) Tentukan nilai I_1 .

Determine the value of I_1 .

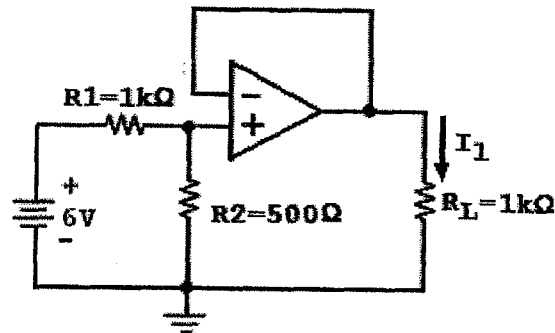


Rajah 4
Figure 4

(20%)

- (c) Apakah fungsi penguat kendalian di dalam litar berikut? Tentukan nilai gandaan voltan penguat, A_v , jika kuasa yang dilesapkan oleh perintang R_L adalah 1W. Apakah nilai R_2 dalam Rajah 5?

What is the function of the operational amplifier (op-amp) in the following circuit? Determine the voltage gain of the amplifier, A_v , if the power dissipated by R_L is equal to 1W. What is the value of R_2 in Figure 5?

(20%)

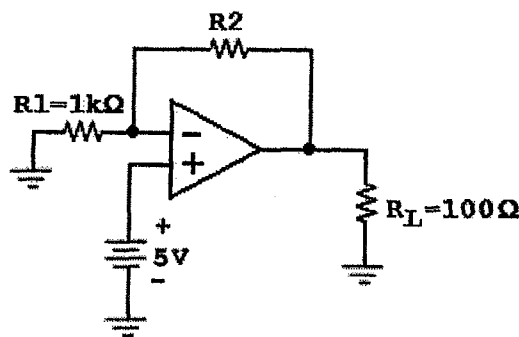


Rajah 5
Figure 5

...6/-

(d) Tentukan nilai V_{OUT} bagi litar dalam Rajah 6, apabila:

Determine the value of V_{OUT} for the circuit in Figure 6, when:

- (i) S1 dimatikan, S2 dimatikan, dan S3 dihidupkan.
S1 is turned OFF, S2 is turned OFF, and S3 is turned ON.
- (ii) S1 dihidupkan, S2 dimatikan, dan S3 dimatikan.
S1 is turned ON, S2 is turned OFF, and S3 is turned OFF.
- (iii) S1 dimatikan, S2 dihidupkan, dan S3 dimatikan.
S1 is turned OFF, S2 is turned ON, and S3 is turned OFF.
- (iv) S1 dihidupkan, S2 dihidupkan, dan S3 dihidupkan.
S1 is turned ON, S2 is turned ON, and S3 is turned ON.

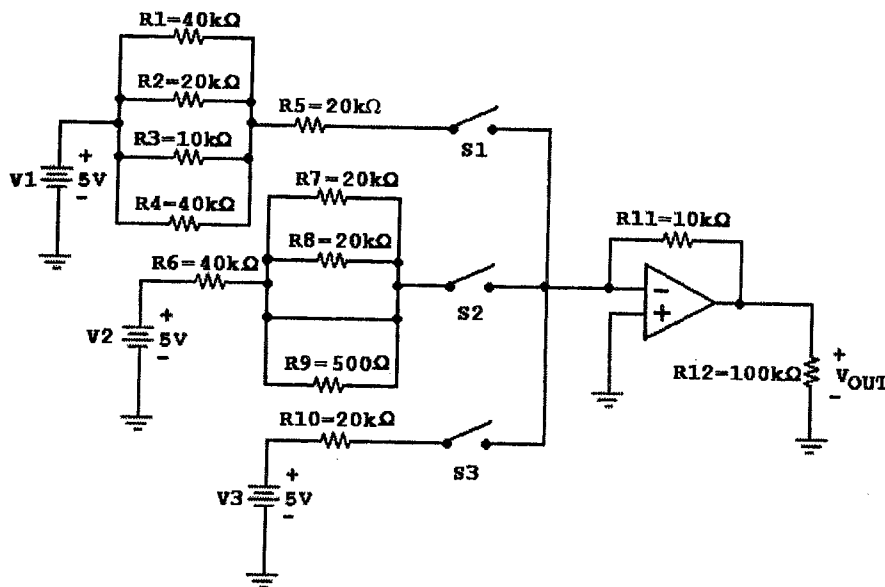

Rajah 6
Figure 6

(50%)

...7/-

Soalan 4

- (a) Dengan menggunakan peta Karnaugh, ringkaskan persamaan berikut:

Use a Karnaugh map to minimize the following expression:

$$\begin{aligned} &\overline{B}\overline{C}\overline{D} + \overline{A}B\overline{C}\overline{D} + ABC\overline{D} + \overline{A}\overline{B}CD + A\overline{B}CD \\ &+ \overline{A}\overline{B}C\overline{D} + \overline{A}BC\overline{D} + ABC\overline{D} + A\overline{B}C\overline{D} \end{aligned}$$

(20%)

- (b) Gunakan teori De Morgan ke atas persamaan berikut:

Apply De Morgan theorem to each expression:

(a) $\overline{A+B}$

(b) \overline{AB}

(c) $\overline{A+B+C}$

(d) \overline{ABC}

(20%)

- (c) Dengan menggunakan flip-flop JK, rekabentuk pembilang binari 3 bit.

Design a 3 bit binary counter using JK flip-flop.

(60%)

...8/-

Soalan 5

(a) Gunakan teori De Morgan ke atas persamaan berikut:

Apply De Morgan theorems to each of the following expression:

(a) $\overline{A(B+C)}$

(b) $\overline{AB+CD}$


(c) $\overline{AB+CD}$

(d) $\overline{(A+\overline{B})(\overline{C}+D)}$

(20%)

(b) Dapatkan simbol get logik dan Persamaan Boolean bagi litar dalam Rajah 7.

Determine the logic gate symbol and Boolean expression for the circuit in Figure 7.

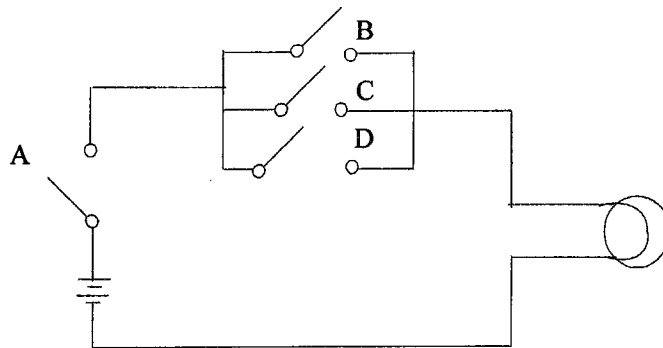


Rajah 7
Figure 7

(20%)


...9/-

- (c) Dapatkan bentuk gelombang Q mengikut isyarat jam jika isyarat yang ditunjukkan dalam Rajah 8 diberikan kepada masukan flip-flop JK bagi litar dalam Rajah 9. Andaikan Q pada mulanya berada pada logik 0.

Determine the Q waveform relative to the clock if the signals shown in Figure 8 are applied to the inputs of the JK flip-flop as shown in Figure 9. Assume that Q is initially low.

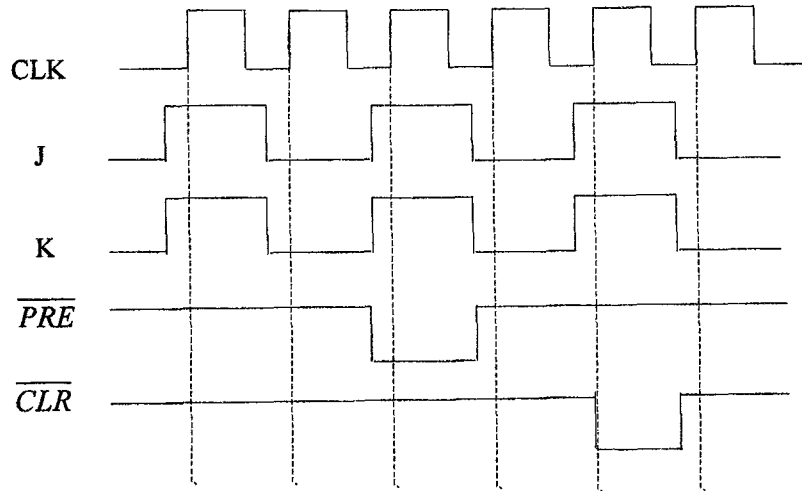

Rajah 8
Figure 8

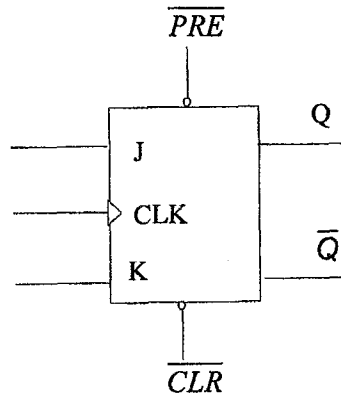


Rajah 9
Figure 9


(30%)
...10/-

- (d) 74LS195A merupakan daftar anjak masukan selari-keluaran selari. Ia juga boleh digunakan untuk operasi masukan sesiri-keluaran selari. Blok logik untuk 74LS195A ditunjukkan dalam Rajah 10. Dapatkan gelombang keluaran jika isyarat yang ditunjukkan dalam Rajah 11 digunakan sebagai masukan kepada 74LS195A.

74LS195A is a parallel in-parallel out shift register. It can also be used as a serial-in parallel-out shift register. The logic block is shown in Figure 10. Determine the output waveform if the signals shown in Figure 11 are applied to the inputs of the 74LS195A.

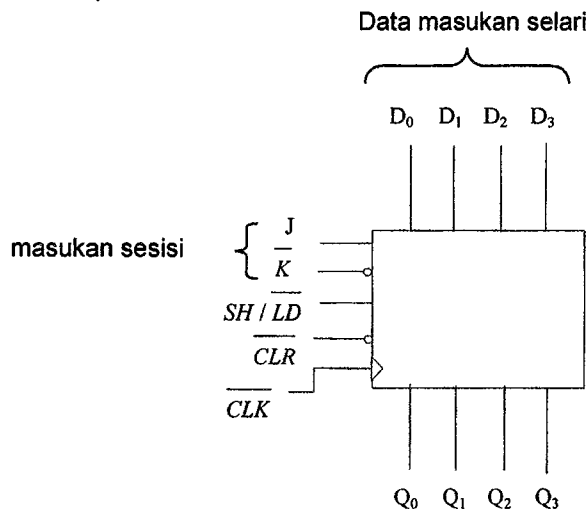

Rajah 10
Figure 10

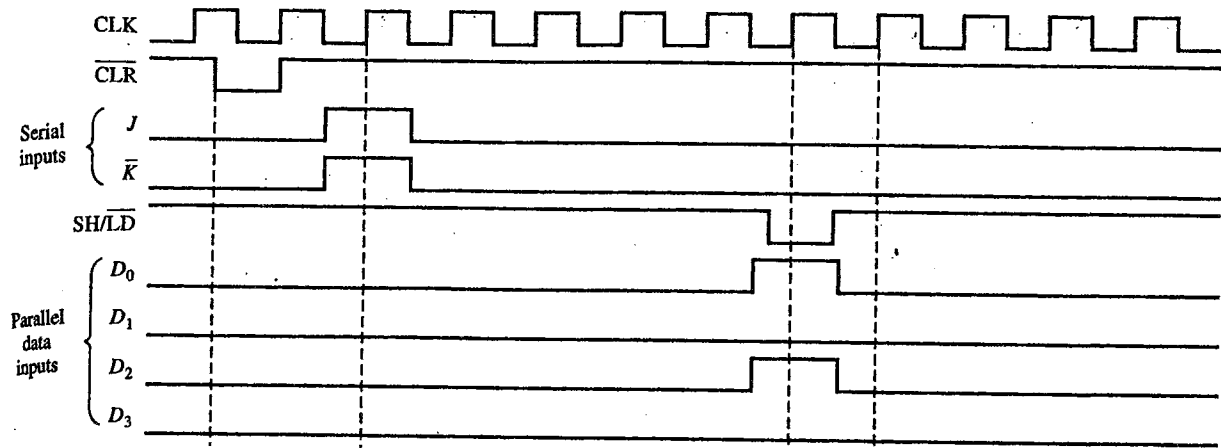

Rajah 11
Figure 11

(30%)

ooo0ooo

JADUAL PERKALAAAN UNSUR

Jadual Isotop-isotop Radioaktif

Isotop-isotop radioaktif yang wujud semula jadi ditunjukkan oleh nombor jisim berwarna biru. Tempoh dalam kurungan ditunjukkan dalam minit, jam, hari dan tahun mengemasing. Simbol-simbol mengelaskan keadaan reputan dan pancaran yang dihibitkan ditakrifkan seperti berikut:

- α zarah alfa
- β zarah beta
- β⁺ positron
- γ pancaran gamma
- ε tangkapan elektron L
- SF pembelahan spontan
- SN sinaran gamma
- e penukaran elektron dalam.

KALIAN

KUMPULAN IA

1 1.00787 H 1 Hidrogen	3 6.939 Li 3 Litium	4 9.0122 Be 4 Berilium
11 22.989769 Na 11 Natrium	12 24.312 Mg 12 Magnesium	

IIA

2 4.0026 He 2 Helium	10 20.183 Ne 10 Neon	18 39.948 Ar 18 Argon
---	---	--

IIIB

IVB

VB

VIB

VII B

VIII

IB

II B

III A

IV A

V A

VIA

VII A


VIIIA

VIIIA

19 39.102 K 19 Kalium	20 40.08 Ca 20 Kalsium	21 44.956 Sc 21 Skandium	22 47.90 Ti 22 Titanium	23 50.942 V 23 Vanadium	24 51.996 Cr 24 Kromium	25 54.938 Mn 25 Mangan	26 55.847 Fe 26 Besen	27 58.933 Co 27 Kobalt	28 58.71 Ni 28 Nikel	29 63.54 Cu 29 Kuprum	30 65.37 Zn 30 Zink	31 69.72 Ga 31 Galium	32 72.59 Ge 32 Germanium	33 74.922 As 33 Arsenik	34 78.96 Se 34 Selenium	35 79.909 Br 35 Bromin	36 83.80 Kr 36 Kripton
37 85.47 Rb 37 Rubidium	38 87.62 Sr 38 Strontium	39 88.905 Y 39 Yttrium	40 91.22 Zr 40 Zirkonium	41 92.906 Nb 41 Niobium	42 95.94 Mo 42 Molibdenum	43 (98) Tc 43 Teknium	44 101.07 Ru 44 Ruthenium	45 102.905 Rh 45 Rodium	46 106.4 Pd 46 Paladium	47 107.870 Ag 47 Argentum	48 112.40 Cd 48 Kadmium	49 114.82 In 49 Indium	50 118.68 Sn 50 Stannum	51 121.75 Sb 51 Antimon	52 127.60 Te 52 Telurium	53 126.904 I 53 Iodin	54 131.30 Xe 54 Xenon
55 132.905 Cs 55 Sesium	56 137.34 Ba 56 Barium	57 138.91 La 57 Lantanum	58 140.907 Ce 58 Sesium	59 140.907 Pr 59 Praseodimium	60 144.24 Nd 60 Neodimium	61 (147) Pm 61 Prometium	62 150.35 Sm 62 Samarium	63 151.96 Eu 63 Europium	64 157.25 Gd 64 Gadolium	65 158.924 Tb 65 Terbium	66 162.50 Dy 66 Dysprosium	67 164.930 Ho 67 Holmium	68 167.26 Er 68 Erbium	69 168.934 Tm 69 Thulium	70 173.04 Yb 70 Ytterbium	71 174.97 Lu 71 Lutetium	
87 (223) Fr 87 Fransium	88 (226) Ra 88 Radium	89 (227) Ac 89 Aktinium	90 232.038 Th 90 Thorium	91 (231) Pa 91 Protaktinium	92 238.03 U 92 Uranium	93 (237) Np 93 Neptunium	94 (242) Pu 94 Plutonium	95 (243) Am 95 Americium	96 (247) Cm 96 Kuriutium	97 (247) Bk 97 Berkelium	98 (249) Cf 98 Kalifornium	99 (254) Es 99 Einsteinium	100 (253) Fm 100 Fermium	101 (256) Md 101 Mendelevium	102 (254) No 102 Nobelium	103 (257) Lw 103 Lawrensium	

330

Lampiran 1
Appendix 1

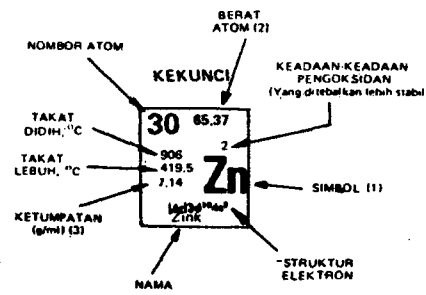

- CATITAN:
- (1) Hitam - pepejal. Merah - gas. Biru - cecair. Gariskan - disediakan secara sintetik.
 - (2) Berdasarkan kepada Karbon - 12.
 - (3) Nilai-nilai unsur-unsur gas dalam bentuk cecair pada takat didih.

Zeners 1N4728A - 1N4764A

Electrical Characteristics (Continued) $T_A = 25^\circ\text{C}$ unless otherwise noted

Device	V_Z (V) @ I_Z (Note 1)	Test Current I_Z (mA)	Max. Zener Impedance			Leakage Current	
			Z_0 @ I_Z (Ω)	Z_{0K} @ I_{ZK} (Ω)	I_{ZK} (mA)	V_K (V)	
1N4758A	56	4.5	110	2000	0.25	5	42.6
1N4759A	62	4	125	2000	0.25	5	47.1
1N4760A	68	3.7	150	2000	0.25	5	51.7
1N4761A	75	3.3	175	2000	0.25	5	56
1N4762A	82	3	200	3000	0.25	5	62.2
1N4763A	91	2.8	250	3000	0.25	5	69.2
1N4764A	100	2.5	350	3000	0.25	5	76

V_Z Forward Voltage = 1.2V Max @ $I_Z = 200\text{mA}$

Notes:
1. V_Z Voltage (V)
2. The zener voltage is measured with the device junction in the thermal equilibrium at the lead temperature (T_L) at 30°C ± 1°C and 30° lead length.

©2002 Fairchild Semiconductor Corporation 1N4728A - 1N4764A, Rev. D

Zeners 1N4728A - 1N4764A

FAIRCHILD SEMICONDUCTOR

Zeners
1N4728A - 1N4764A

Absolute Maximum Ratings * $T_A = 25^\circ\text{C}$ unless otherwise noted

Symbol	Parameter	Value	Units
P_D	Power Dissipation @ $T_L \leq 50^\circ\text{C}$, Lead Length = 3/8"	1.0	W
	Derate above 50°C	6.67	mW/°C
T_L , T_{stg}	Operating and Storage Temperature Range	-65 to +200	°C

* These ratings are limiting values above which the serviceability of the device may be impaired.

Electrical Characteristics $T_A = 25^\circ\text{C}$ unless otherwise noted

Device	V_Z (V) @ I_Z (Note 1)	Test Current I_Z (mA)	Max. Zener Impedance			Leakage Current	
			Z_0 @ I_Z (Ω)	Z_{0K} @ I_{ZK} (Ω)	I_{ZK} (mA)	V_K (V)	
1N4728A	3.3	76	10	400	1	100	1
1N4729A	3.6	69	10	400	1	100	1
1N4730A	3.9	64	9	400	1	50	1
1N4731A	4.3	58	8	400	1	10	1
1N4732A	4.7	53	8	500	1	10	1
1N4733A	5.1	49	7	550	1	10	1
1N4734A	5.6	45	5	600	1	10	2
1N4735A	6.2	41	2	700	1	10	3
1N4736AT	6.8	37	3.5	700	1	10	4
1N4737AT	7.5	34	4	700	0.5	10	5
1N4738AT	8.2	31	4.5	700	0.5	10	6
1N4739AT	9.1	28	5	700	0.5	10	7
1N4740AT	10	25	7	700	0.25	10	7.6
1N4741AT	11	23	8	700	0.25	5	8.4
1N4742AT	12	21	9	700	0.25	5	9.1
1N4743AT	13	19	10	700	0.25	5	9.9
1N4744AT	15	17	14	700	0.25	5	11.4
1N4745AT	16	15.5	16	700	0.25	5	12.2
1N4746AT	18	14	20	750	0.25	5	13.7
1N4747AT	20	12.5	22	750	0.25	5	15.2
1N4748A	22	11.5	23	750	0.25	5	16.7
1N4749A	24	10.5	25	750	0.25	5	18.2
1N4750A	27	9.5	35	750	0.25	5	20.6
1N4751A	30	8.5	40	1000	0.25	5	22.8
1N4752A	33	7.5	45	1000	0.25	5	25.1
1N4753A	36	7	50	1000	0.25	5	27.4
1N4754A	39	6.5	60	1000	0.25	5	29.7
1N4755A	43	6	70	1500	0.25	5	32.7
1N4756A	47	5.5	80	1500	0.25	5	35.8
1N4757A	51	5	95	1500	0.25	5	38.8

DO-41 Glass case
COLLAR BAND RESTRICTS COMPACT

©2002 Fairchild Semiconductor Corporation 1N4728A - 1N4764A, Rev. D



1N4001 Thru 1N4007

1 AMP PLASTIC SILICON RECTIFIER

FEATURES


- Rating to 1000V PRV
- Low cost
- Diffused junction
- Low leakage
- Low forward voltage drop
- High current capability
- Easily cleaned with freon, alcohol, chlorothene and similar solvents
- UL recognized 94V-O plastic material

Mechanical Data


- Case: JEDEC DO-41
- Terminals: Axial leads, solderable per MIL-STD-202, Method 208
- Polarity: Color band denotes cathode
- Weight: 0.012 ounce, 0.3 grams
- Mounting Position: Any

Maximum Ratings & Characteristics

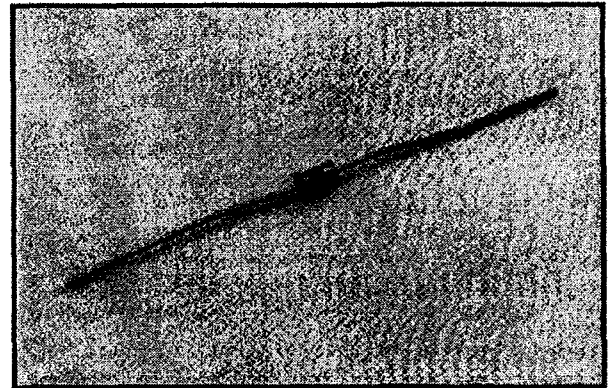- Ratings at 25° C ambient temperature unless otherwise specified
- Single phase, half wave, 60Hz, resistive or inductive load
- For capacitive load, derate current by 20%



Outline Drawing

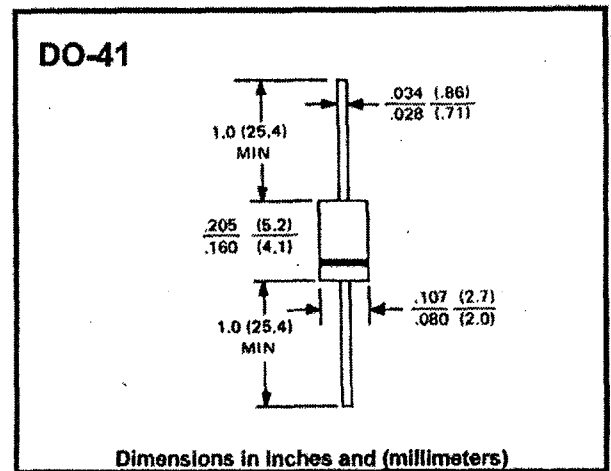

		1N4001	1N4002	1N4003	1N4004	1N4005	1N4006	1N4007	Units
Maximum Recurrent Peak Reverse Voltage	V_{RRM}	50	100	200	400	600	800	1000	V
Maximum RMS Voltage	V_{RMS}	35	70	140	280	420	560	700	V
Maximum DC Blocking Voltage	V_{DC}	50	100	200	400	600	800	1000	V
Maximum Average Forward Rectified Current .375 (9.5mm) Lead Lengths @ $T_A = 75^\circ C$	$I_{(AV)}$	1.0							A
Peak Forward Surge Current 8.3 ms Single Half-Sine-Wave Superimposed On Rated Load	I_{FSM}	40							A
Maximum Forward Voltage At 1.0A DC	V_F	1.0							V
Maximum DC Reverse Current @ $T_A = 25^\circ C$ At Rated DC Blocking Voltage @ $T_A = 100^\circ C$	I_R	5 50							μA
Typical Junction Capacitance (Note 1) $T_A = 25^\circ C$	C_J	15							pF
Typical Thermal Resistance (Note 2)	R_{thJA}	26							$^\circ C/W$
Operating Temperature Range	T_J	-65 to +175							$^\circ C$
Storage Temperature Range	T_{STG}	-65 to +175							$^\circ C$

Notes: 1. Measured at 1.0 MHz and applied reverse voltage of 4.0V DC