
UNIVERSITI SAINS MALAYSIA

First Semester Examination
Academic Session 2007/2008

October/November 2007

EEE 510 – ADVANCED ANALOGUE CIRCUIT DESIGN

Duration: 3 hours

Please check that this examination paper consists of EIGHT pages of printed material before you begin the examination.

This paper contains SIX questions.

Instructions: Answer **FIVE (5)** questions.

Answer to any question must start on a new page.

Distribution of marks for each question is given accordingly

All questions must be answered in English.

1. Figure1 shows a series-shunt amplifier with a feedback factor $\beta = 1$. The amplifier is designed so that $v_o = 0$ for $v_s = 0$, with small deviations in v_o from 0V dc being minimized by negative feedback action. The technology utilized has $k'n = 2k'p = 120 \frac{\mu A}{V^2}$, $|V_t| = 0.7V$, and $|V' A| = 24V$.

- (a) Calculate g_m and r_o of each transistor. (10 marks)
- (b) Find the values of A. Assume that the bias current sources are ideal. (10 marks)

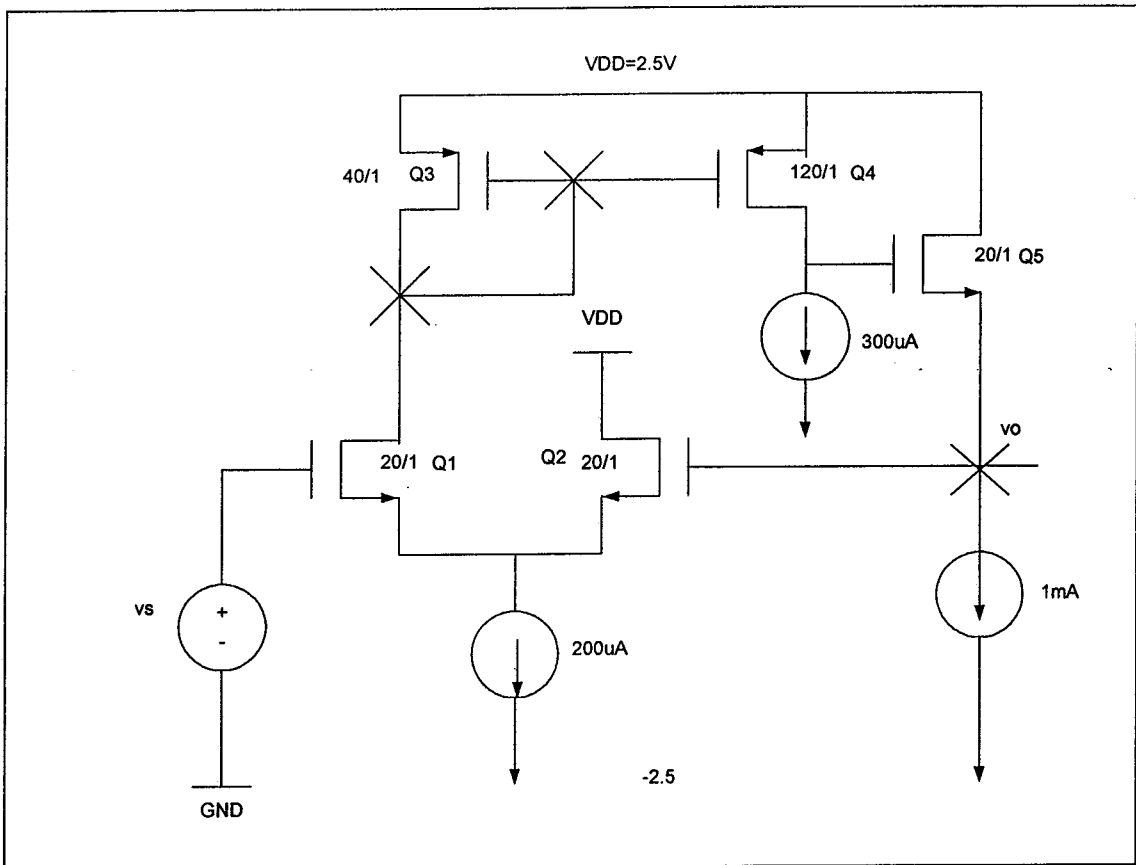


Figure 1

2. The MOSFET current source shown in the Figure 2 is required to deliver a DC current of 1mA with $V_{GS} = 0.8V$. If the MOSFET has $V_t = 0.55 V$, $V_A = 20V$ and the body trans-conductance factor $\chi = 0.2$, find the value of R that results in a current-source output resistance of $200 k\Omega$. Also determine the dc voltage V_{BIAS} .

(20 marks)

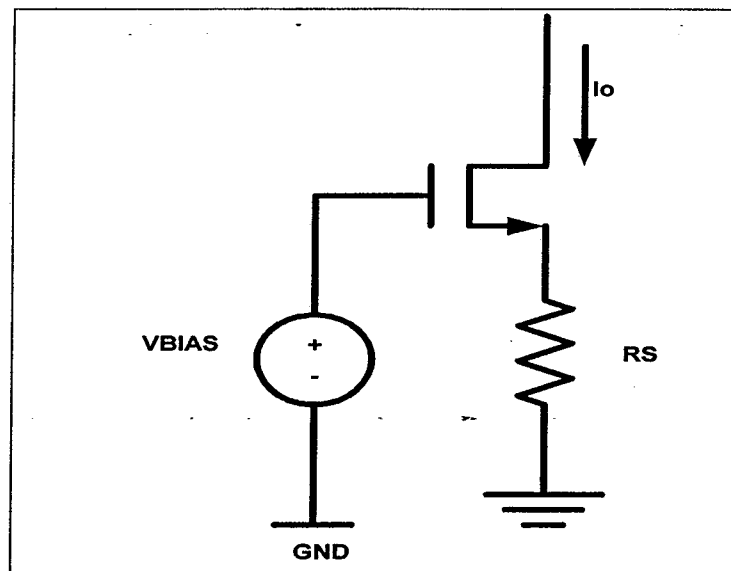


Figure 2

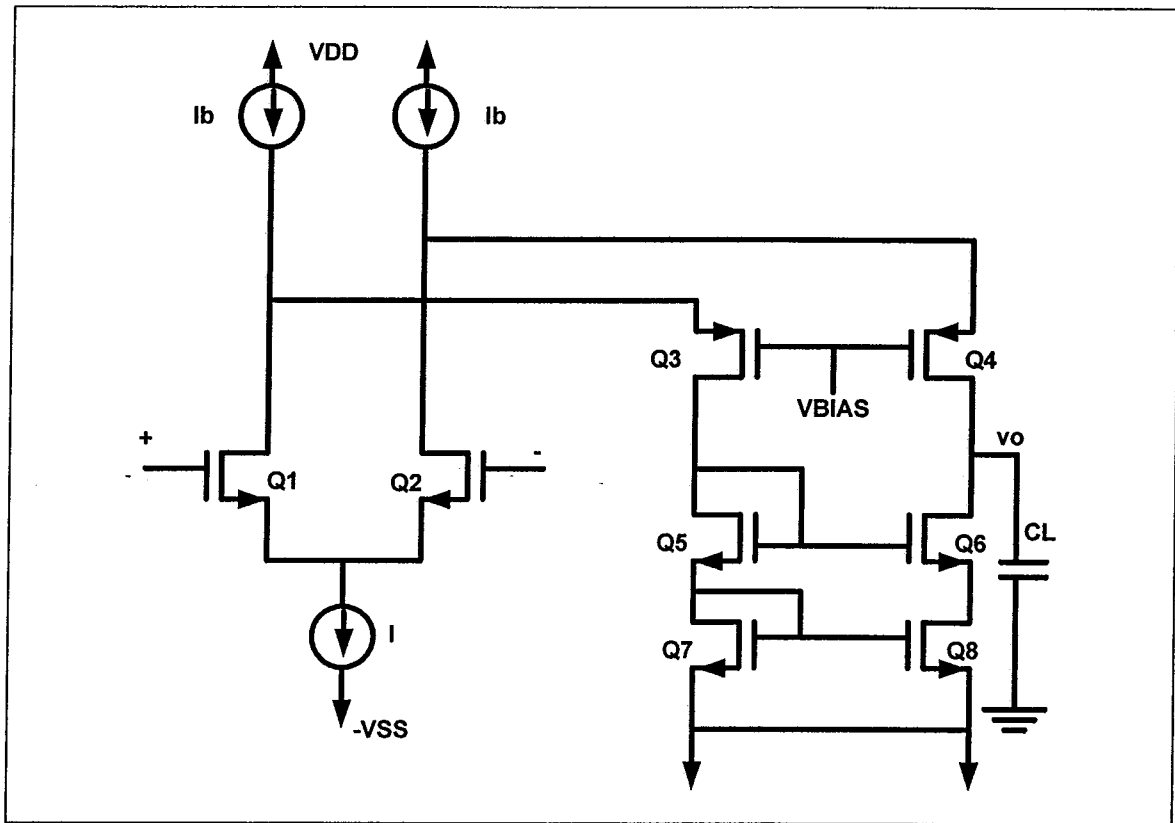


Figure 3

3. For the folded cascode in Figure 3, the op amp has bias currents $I = 125\mu\text{A}$ and $I_B = 150\mu\text{A}$ and with all transistors operated at the overdrive voltages of 0.2V .
- (a) Find W/L ratios for all devices. Assume that the technology available is characterized by $k'_n = 250 \mu\text{A}/\text{V}^2$ and $k'_p = 90 \mu\text{A}/\text{V}^2$. (5 marks)
- (b) What is the expression of the output resistance. (5 marks)

- (c) Based on the specification given, if we were to add C_L of 350f to the output , what would be your amplifier gainbandwidth?
(5 marks)
- (d) If V_A is 10V, where do you anticipate the dominant pole?
(5 marks)

4. (a) What is the difinition of transition frequency, f_T ? Explain how the f_T of a bipolar transistor can be measured and calculated. Neglect r_{ex} and r_{μ} . Show that

$$f_T = \frac{1}{2\pi} \frac{g_m}{C_{\pi} + C_{\mu}}$$

(8 marks)

- (b) Derive the complete small-signal model (i.e. find g_m , g_{mb} , r_o , C_{sb} , C_{db} , C_{ox} , C_{gs} and draw the small-signal model with all these elements in it) for an NMOS transistor with $I_D = 100 \mu A$, $V_{SB} = 1 V$, $V_{DS} = 2 V$. Device parameters are $\phi_f = 0.3 V$, $W = 10 \mu m$, $L = 1 \mu m$, $\gamma = 0.5 V^{1/2}$, $k' = \mu n C_{ox} = 200 \mu A/V^2$, $\lambda = 0.02 V^{-1}$, $t_{ox} = 100$ angstroms, $\psi_o = 0.6 V$, $C_{sbo} = C_{dbo} = 10$ fF. Overlap capacitance from gate to source and gate to drain is 1fF. Assume $C_{gb} = 5$ fF.

(12 marks)

5. (a) Show that the transconductance of the amplifier circuit in Figure 4 can be represented by $\frac{1}{(1 + \chi)R_s}$ when $r_o \gg R_s$ and R_s is large. χ is the body transconductance to the transistor's transconductance ratio.

(10 marks)

...6/-

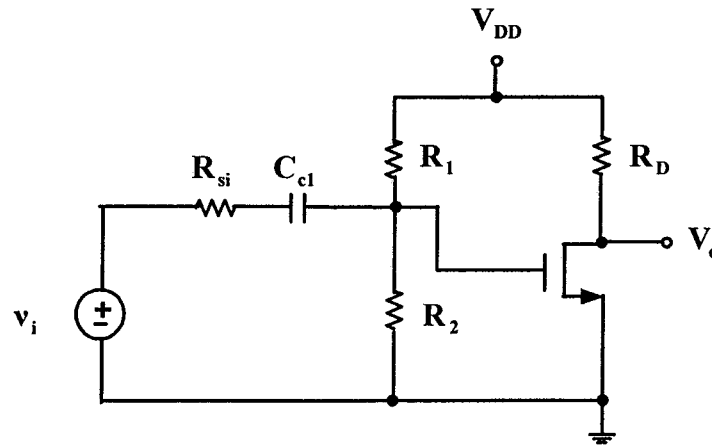


Figure 5

6. (a) Describe the advantages of using an amplifier of the Darglington configuration.

(5 marks)

- (b) For each transistor in the circuit in Figure 6,-the parameters are: $\beta=125$, $V_{BE}=0.7$ V, and $r_o = \infty$.

- (i) Determine the Q-points of each transistor (i.e. I_{CQ1} , V_{CEQ1} , I_{CQ2} , V_{CEQ2})
- (ii) Find the overall small-signal voltage gain

$$a_v = \frac{v_o}{v_s}$$

- (iii) Determine the input resistance R_i and the output resistance R_o .

(15 marks)