

---

UNIVERSITI SAINS MALAYSIA

Semester I Examination  
Academic Session 2004/2005

October 2004

**EEE 532 – MICROWAVE CIRCUIT DESIGN**

Time : 2 hours

---

**INSTRUCTION TO CANDIDATE:**

Please ensure that this examination paper contains **SIX (6)** printed pages including Appendices (6 pages) and **SIX (6)** questions before answering.

This question paper has two sections, **Section A** and **Section B**.

Answer **TWO (2)** questions in **Section A** and **TWO (2)** questions in **Section B**.

Use two answer booklets which is provided where the answer for questions in **Section A** are in one answer booklet and for **Section B** in another answer booklet.

Answer **FOUR (4)** questions.

Distribution of marks for each question is given accordingly.

All questions must be answered in English.


**SECTION A**

**INSTRUCTION:** Answer **TWO** questions in this section.


1. Design a two sections of L-network to match a load of  $Z_L = 200 - j25\text{ohm}$  to a 50 ohm line using lumped components at frequency of 1GHz.

(25 marks)

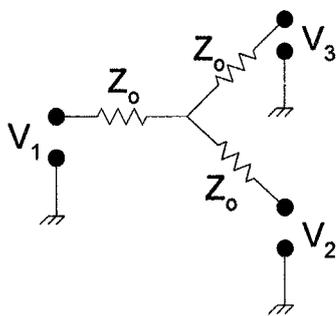2. Determine the S-parameter of the 3-ports network as in Figure 1 and give your comment.



(a) Star 3 port network

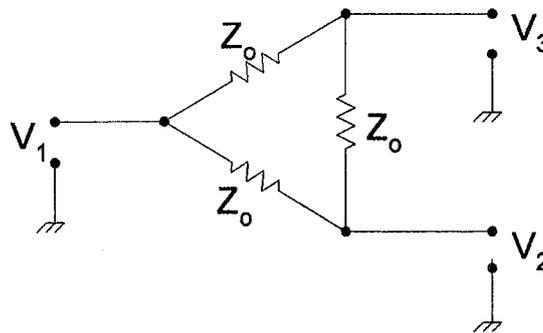

(b) Delta 3 port network

Figure 1

(25 marks)

**SECTION B**

**INSTRUCTION:** Answer **TWO** questions in this section.

4. Design a third order microstrip low pass filter having the cutoff frequency of 6 GHz, 0.5 dB equal-ripple characteristic and to be used in  $50\Omega$  system. Use the Kuroda's identities in your design. The element values are given in Table 2. Use an approximate formula in the calculation of the microstrip width. The Duroid microwave laminate have a dielectric constant of 2.5, the thickness of 0.78 mm and the copper thickness is  $35\ \mu\text{m}$ .

(25 Marks)

5. A ATF transistor 35143 has S parameters tabulated in Table 1. The S parameter was measured on  $50\Omega$  systems.

S <sub>11</sub>		S <sub>21</sub>		S <sub>12</sub>		S <sub>22</sub>	
Mag	Ang	Mag	Ang	Mag	Ang	Mag	Ang
0.60	145.61	2.53	12.43	0.157	-41.00	0.31	-138.01

Table 1: ATF 35413 transistor S parameters measured at 7 GHz.

If the source impedance,  $Z_s$  is  $30\Omega$  and the load impedance,  $Z_L$  is  $40\Omega$ . Calculate the transistor's:

- (i) Power Gain. (5 Marks)
- (ii) Available Gain. (5 Marks)
- (iii) Transducer power gain. (5 Marks)
- (iv) Determine the transistor stability. (10 Marks)

6. (a) Referring to Figure 2, prove that the reflection coefficients  $\Gamma_L$  and  $\Gamma_{in}$  are related as  $\Gamma_L \Gamma_{in} = 1$  for steady-state oscillation of the negative resistance oscillator.

(10 Marks)

- (b) Explain what is the phase noise in the oscillator. (5 Marks)

- (c) Explain what is the resonator and name three type of resonators that are typically used in oscillator design.

(5 Marks)

- (d) Briefly describe the feedback type oscillator topology and explain what are the important criterion in the design of the oscillator.

(5 Marks)

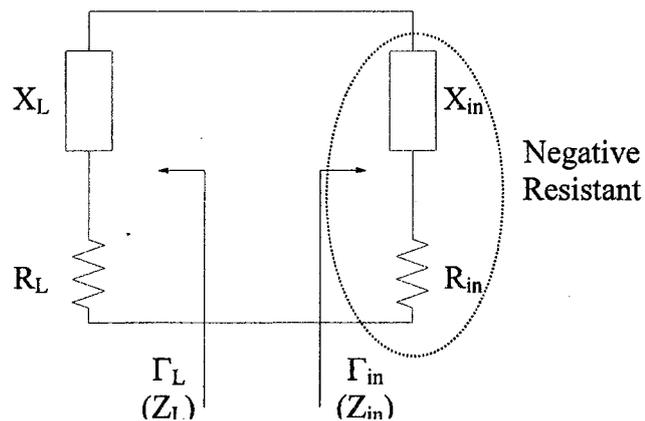


Figure 2

N	$g_1$	$g_2$	$g_3$	$g_4$	$g_5$	$g_6$	$g_7$	$g_8$	$g_9$	$g_{10}$	$g_{11}$
1	0.6986	1.000									
2	1.4029	0.7071	1.9841								
3	1.5963	1.0967	1.5963	1.000							
4	1.6703	1.1926	2.3661	0.8419	1.9841						
5	1.7058	1.2296	2.5408	1.2296	1.7058	1.000					
6	1.7254	1.2479	2.6064	1.3137	2.4758	0.8696	1.9841				
7	1.7372	1.2583	2.6381	1.3444	2.6381	1.2583	1.7372	1.000			
8	1.7451	1.2647	2.6564	1.3590	2.6964	1.3389	2.5093	0.8796	1.9841		
9	1.7504	1.2690	2.6678	1.3673	2.7239	1.3673	2.6679	1.2690	1.000		
10	1.7543	1.2721	2.6754	1.3725	2.7392	1.3806	2.7231	1.3485	2.5239	0.8842	1.9841

Table 2: Element values for Equal-Ripple Low-Pass Filter Prototypes 0.5 dB ripple.

ooo0ooo

## APPENDIX

[EEE 532]

### Important Formulas:

#### Network parameters

##### S-parameter

$$S_{11} = \left. \frac{V_{r1}}{V_{i1}} \right|_{V_{r2}=0} \quad S_{12} = \left. \frac{V_{i2}}{V_{i2}} \right|_{V_{r2}=0} \quad S_{21} = \left. \frac{V_{i1}}{V_{i1}} \right|_{V_{r1}=0} \quad S_{22} = \left. \frac{V_{r2}}{V_{i2}} \right|_{V_{r1}=0}$$

##### ABCD parameter

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

##### Conversion

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \frac{1}{Z_o A + B + Z_o^2 C + Z_o D} \begin{bmatrix} Z_o A + B - Z_o^2 C - Z_o D & 2Z_o(AD - BC) \\ 2Z_o & -Z_o A + B - Z_o^2 C + Z_o D \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{2S_{21}} \begin{bmatrix} (1+S_{11})(1-S_{22}) + S_{12}S_{21} & Z_o((1+S_{11})(1+S_{22}) - S_{12}S_{21}) \\ \frac{1}{Z_o}((1-S_{11})(1-S_{22}) - S_{12}S_{21}) & (1-S_{11})(1+S_{22}) + S_{12}S_{21} \end{bmatrix}$$

##### Butterworth lowpass filter

$$g_k = 2 \sin(2k-1) \frac{\pi}{2n} \quad \text{where } k=1, \dots, n$$

$$g_0 = g_{n+1} = 1$$

$$n = \frac{\log_{10}(10^{A/10} - 1)}{2 \log_{10}(\omega/\omega_c)}$$

$$C_k = \frac{g_k}{Z_o \omega_c}$$


$$L_k = \frac{Z_o g_k}{\omega_c}$$

##### Bandpass filter

$$J_{01} = \left( \frac{\pi \Omega}{2g_0 g_1} \right)^{\frac{1}{2}}$$

$$J_{k,k+1} = \left( \frac{\pi \Omega}{2} \right) \frac{1}{\sqrt{g_k \cdot g_{k+1}}} \quad \text{where } k=1, \dots, n$$

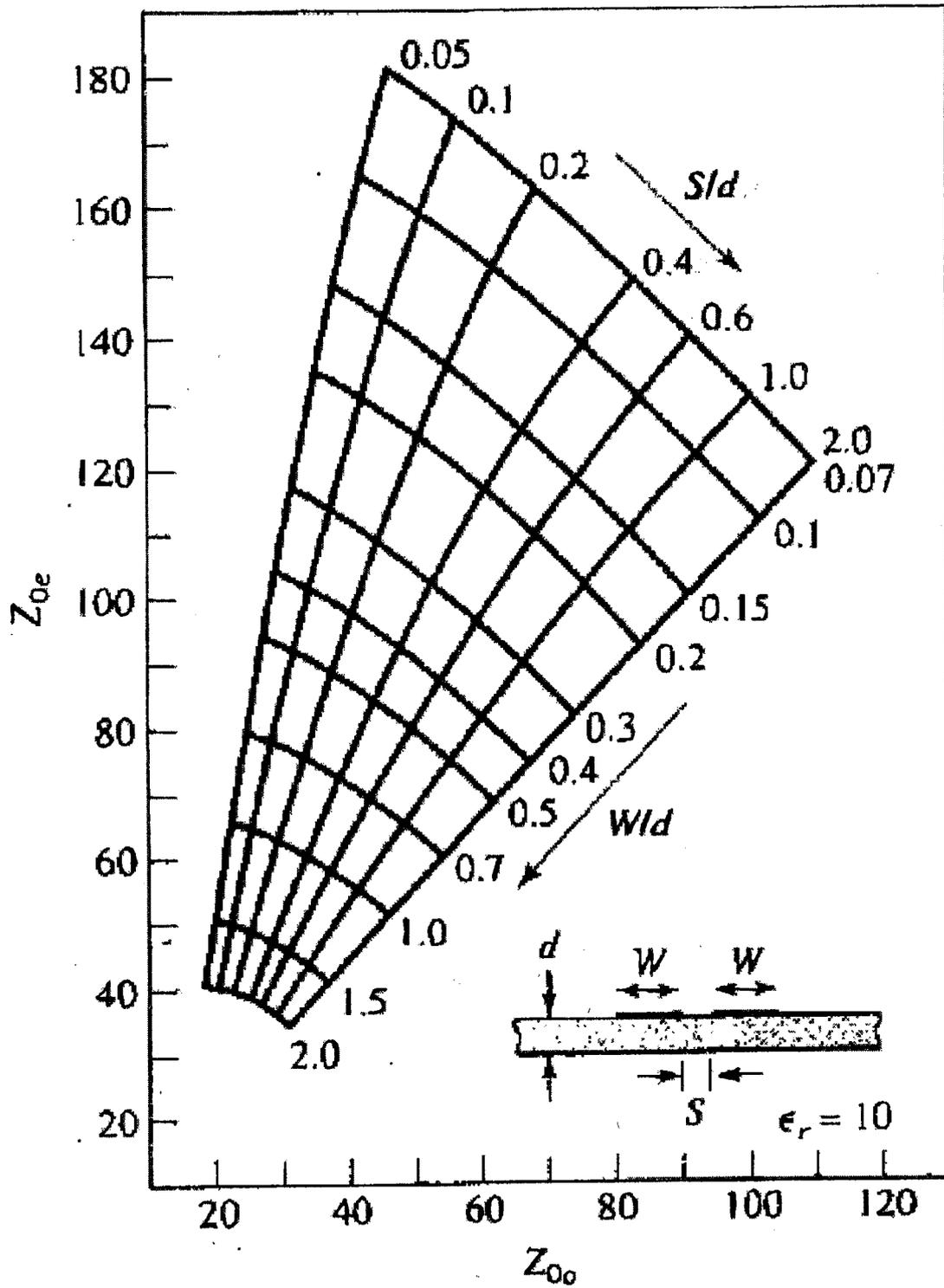
$$J_{n,n+1} = \left( \frac{\pi \Omega}{2 \cdot g_n \cdot g_{n+1}} \right)$$



Even and odd-mode characteristic impedances design data for coupled microstrip lines

NAME	TITLE	DWG. NO.
		DATE
SMITH CHART FORM ZY-01-N		Microwave Circuit Design - EE523 - Fall 2000

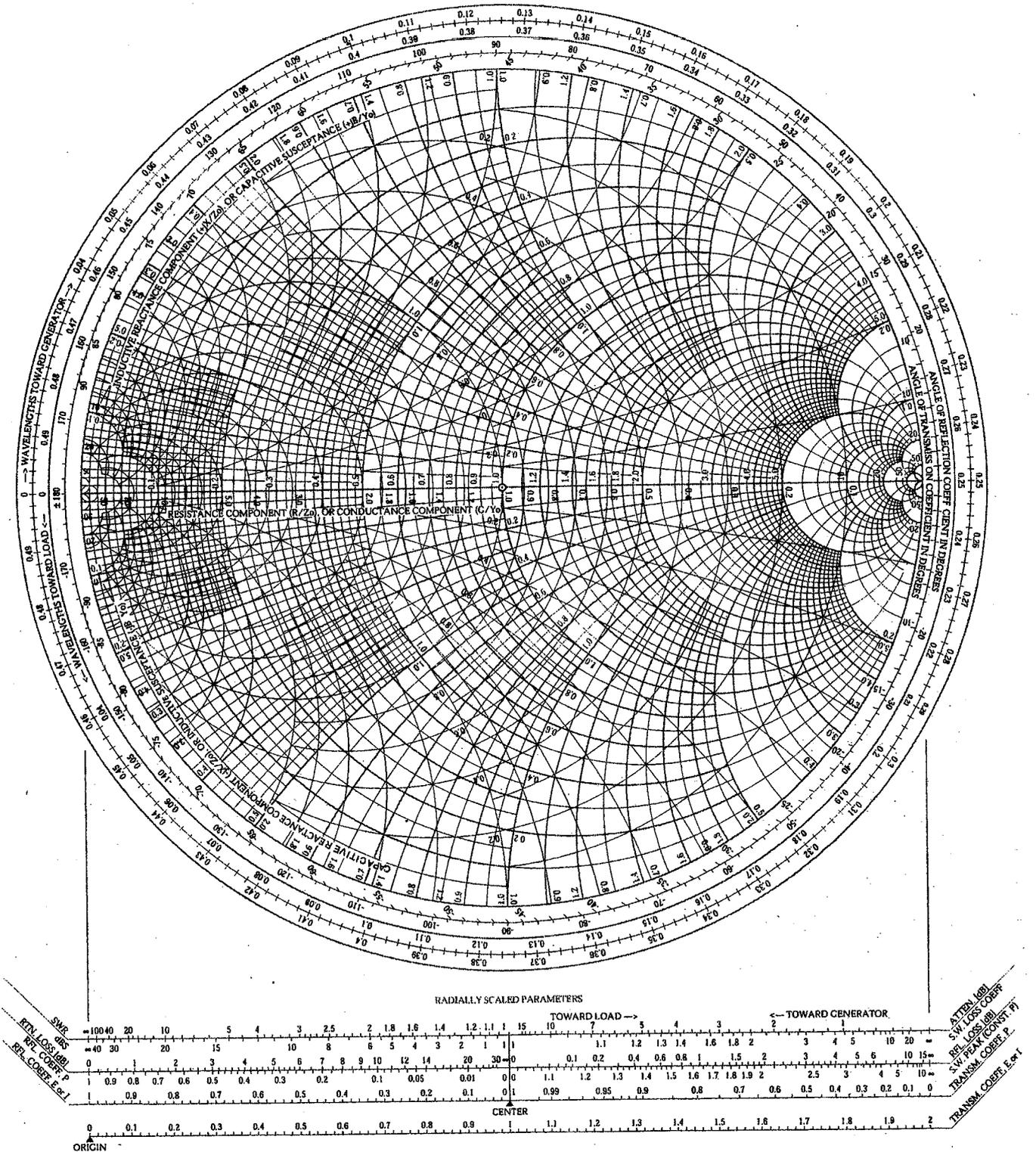NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES



NAME	TITLE	DWG. NO.
SMITH CHART FORM 82-8SPR(9-66)	KAY ELECTRIC COMPANY, PINE BROOK, N.J. ©1966. PRINTED IN U.S.A.	DATE

IMPEDANCE OR ADMITTANCE COORDINATES

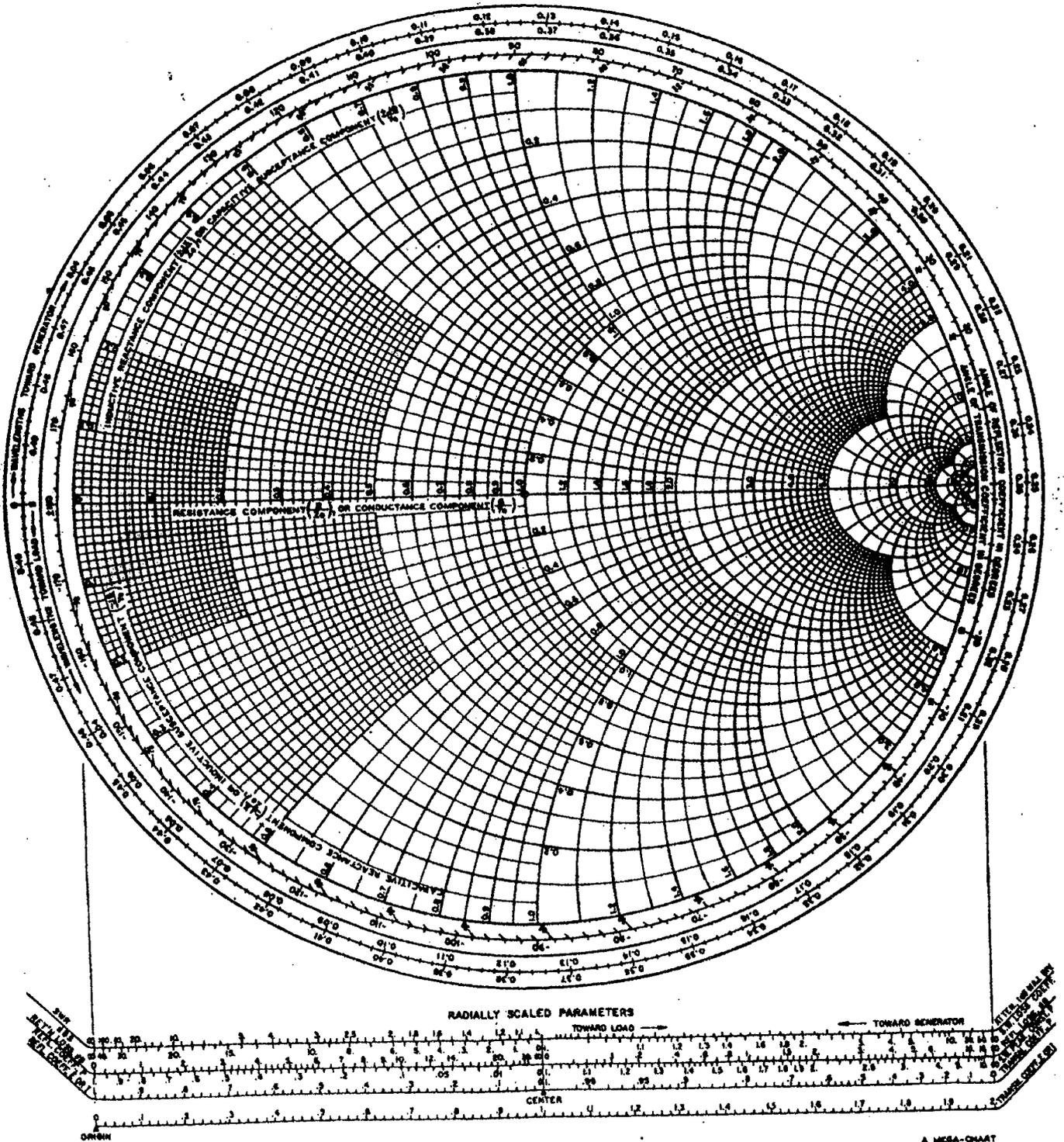


Figure 4.8 Smith chart, reprinted by permission of P. H. Smith, renewal copyright, 1976.