

---

# UNIVERSITI SAINS MALAYSIA

First Semester Examination  
Academic Session 2006/2007

October/November 2006

## EEE 532 – MICROWAVE CIRCUIT DESIGN

Duration: 2 hours

---

Please check that this examination paper consists of FOUR pages of printed material and ELEVEN pages Appendices before you begin the examination.

This paper contains SIX questions. TWO questions in Section A, TWO questions in Section B and TWO questions in Section C.

**Instructions:** Answer **FOUR (4)** questions. Answer **ONE (1)** question from Section A, Section B and Section C. **ONE (1)** question from any Section.

Use three answer booklets which is provided where the answer for questions in Section A, B and C are in difference answer booklets.

Answer to any question must start on a new page.

Distribution of marks for each question is given accordingly.

All questions must be answered in English.

**Section A: Answer ONE (1) question**

1. (a) Design a matching section using a single L-network to match a load of  $Z_L = 50 - j50$  ohm to a 100 ohm line using lumped components at frequency 1GHz. Give all possible solutions.

(10%)

- (b) Design a three section binomial transformer to match 100 ohm load to a 50 ohm line.

(15%)

2. Design a 25dB 3 sections coupled line coupler with a maximally flat coupling response. Assume  $Z_o = 50 \Omega$ , and find  $Z_{oe}$ ,  $Z_{oo}$  for each section. Using a substrate of  $\epsilon_r = 10$  and thickness of 1mm with center frequency of 3GHz, calculate all the parameters of the stripline using the graph in Appendix I. The voltage at port 3 in terms of port 1 is

$$V_3 = 2jV_1 \sin \theta e^{-jN\theta} \left[ C_1 \cos(N-1)\theta + C_2 \cos(N-3)\theta + \dots \frac{1}{2} C_M \right]$$

where  $N = \text{number of section}$ ,  $M = (N+1)/2$ ,  $C_o = \left. \frac{V_3}{V_1} \right|_{\theta = \pi/2}$

Assume the coupler is symmetrical such that  $C_1 = C_N$ ,  $C_2 = C_{N-1}$  etc.

(25%)

...3/-

**Section B: Answer ONE (1) question**

3. (a) A certain two-port network is measured and the following scattering matrix is obtained:

$$[S] = \begin{bmatrix} 0.1\angle 0 & 0.8\angle 90^\circ \\ 0.8\angle 90^\circ & 0.2\angle 0 \end{bmatrix}$$

From this data, determine whether the network is reciprocal or lossless. If a short-circuit is placed on port 2, what will be the resulting return loss at port 1?

(11%)

- (b) Find the S parameter for the series and shunt load shown in Figure 1. Show that  $S_{12} = 1 - S_{11}$  for the series case, and  $S_{12} = 1 + S_{11}$  for the shunt case. Assume characteristic impedance  $Z_0$ . [Hint: Refer to Table 1 in Appendix]

(14%)

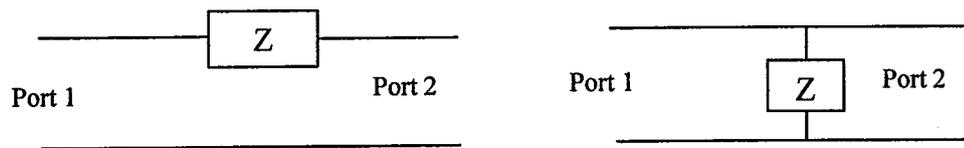


Figure 1


4. Design a low-pass composite filter with cutoff frequency of 2GHz and impedance of 75Ω. Place the infinite attenuation pole at 2.05GHz, and sketch the frequency response from 0 to 4GHz.

(25%)

...4/-

**Section C: Answer ONE (1) question**

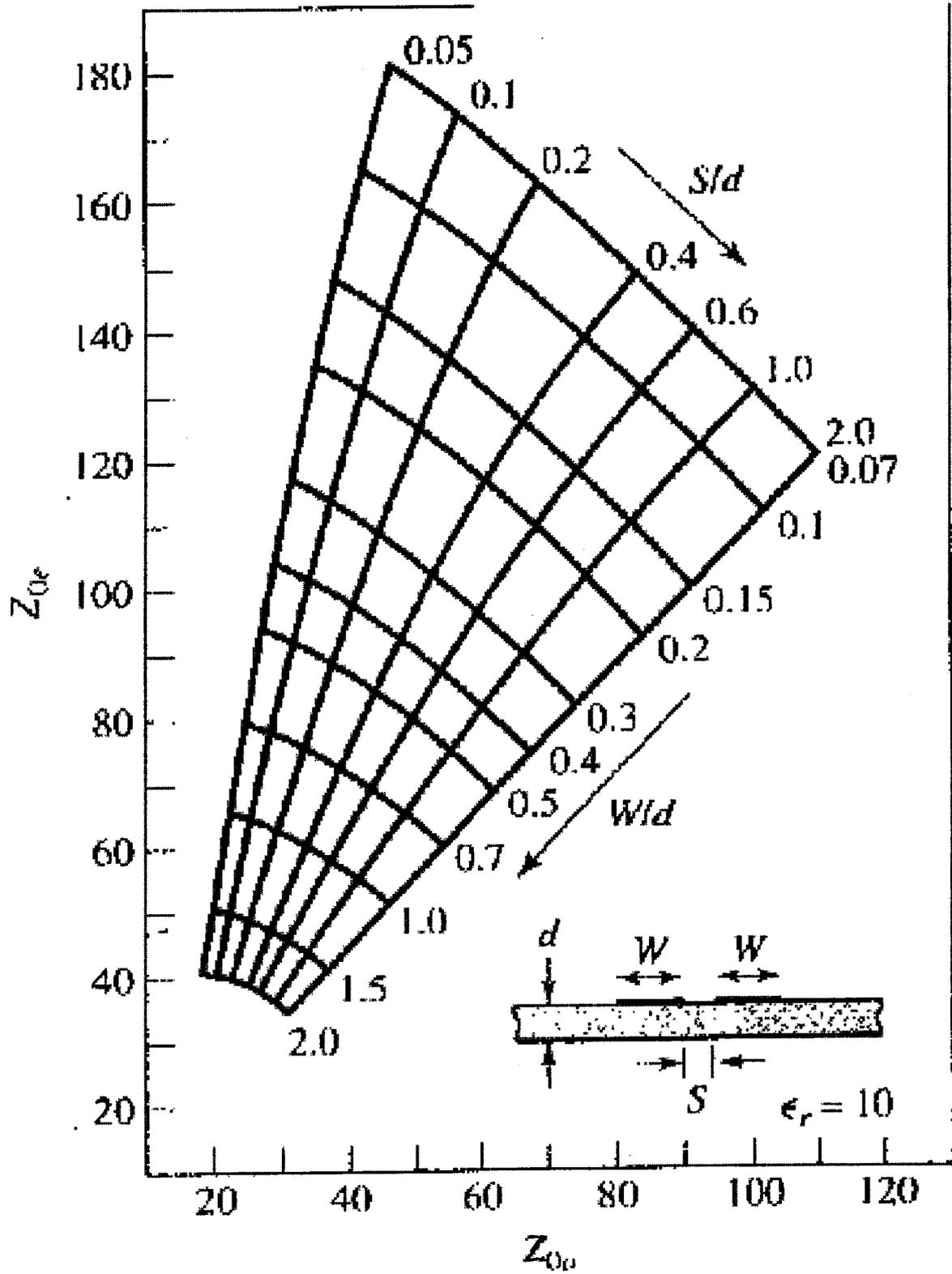5. Design a Low Noise Amplifier operating at 4 GHz, the biasing of the LNA should be at  $V_{DS} = 2$  V and  $I_{DS} = 5$  mA. The required noise figure must be 1.2 dB. Select  $\Gamma_{in}$  for input matching at a point of  $C_{in}$ . Use single stub matching technique and the length of the microstrip should be in millimeter. The parameters of the transistor can be found in Appendix V. (25%)
6. (a) Explain the operation of the negative resistance oscillator with the aid of the diagram. (10%)
- (b) Explain what a resonator is and name three type of resonators that are typically used in the oscillator design. (5%)
- (c) Briefly describe the feedback type oscillator topology and explain what are the important criterions in the design of the feedback oscillator. (5%)
- (d) Explain what is phase noise in an oscillator. (5%)



## APPENDIX II

[EEE 532]

### Important Formulas:

#### Network parameters

S-parameter

$$S_{11} = \left. \frac{V_{r1}}{V_{i1}} \right|_{V_{r2}=0} \quad S_{12} = \left. \frac{V_{i2}}{V_{i2}} \right|_{V_{r2}=0} \quad S_{21} = \left. \frac{V_{i1}}{V_{i1}} \right|_{V_{r1}=0} \quad S_{22} = \left. \frac{V_{r2}}{V_{i2}} \right|_{V_{r1}=0}$$

ABCD parameter

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad D = \left. \frac{I_1}{-I_2} \right|_{V_2=0}$$

Conversion

$$\begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} = \frac{1}{Z_o A + B + Z_o^2 C + Z_o D} \begin{bmatrix} Z_o A + B - Z_o^2 C - Z_o D & 2Z_o(AD - BC) \\ 2Z_o & -Z_o A + B - Z_o^2 C + Z_o D \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \frac{1}{2S_{21}} \begin{bmatrix} (1+S_{11})(1-S_{22}) + S_{12}S_{21} & Z_o((1+S_{11})(1+S_{22}) - S_{12}S_{21}) \\ \frac{1}{Z_o}((1-S_{11})(1-S_{22}) - S_{12}S_{21}) & (1-S_{11})(1+S_{22}) + S_{12}S_{21} \end{bmatrix}$$

Butterworth lowpass filter

$$g_k = 2 \sin(2k-1) \frac{\pi}{2n} \quad \text{where } k=1, \dots, n$$

$$g_0 = g_{n+1} = 1$$

$$n = \frac{\log_{10}(10^{A/10} - 1)}{2 \log_{10}(\omega / \omega_c)}$$

$$C_k = \frac{g_k}{Z_o \omega_c}$$

$$L_k = \frac{Z_o g_k}{\omega_c}$$

Bandpass filter

$$J_{01} = \left( \frac{\pi \Omega}{2g_0 g_1} \right)^{\frac{1}{2}}$$

$$J_{k,k+1} = \left( \frac{\pi \Omega}{2} \right) \frac{1}{\sqrt{g_k \cdot g_{k+1}}} \quad \text{where } k=1, \dots, n$$

$$J_{n,n+1} = \left( \frac{\pi \Omega}{2 \cdot g_n \cdot g_{n+1}} \right)$$

**Bilateral**

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|}{2|S_{12}S_{21}|}$$

$$\Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1} \quad B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \quad C_1 = S_{11} - \Delta S_{22}^*$$

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2} \quad B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2 \quad C_2 = S_{22} - \Delta S_{11}^*$$

$$\Gamma_{in} = \Gamma_S^* = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \quad \Gamma_{out} = \Gamma_L^* = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$$

$$C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad R_L = \left| \frac{S_{12}S_{21}}{|S_{22}|^2 - |\Delta|^2} \right|$$

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad R_S = \left| \frac{S_{12}S_{21}}{|S_{11}|^2 - |\Delta|^2} \right|$$

$$G_{T \max} = \frac{1}{1 - |\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2}$$

**Low Noise Amplifier**

Center:  $C_i = \frac{\Gamma_{opt}}{(1 + N_i)}$

Radius:  $R_i = \frac{1}{1 + N_i} \sqrt{N_i^2 + N_i(1 - |\Gamma_{opt}|^2)}$

$$N_i = \frac{\left[ (F_r - F_{\min}) |1 + \Gamma_{opt}|^2 \right]}{4 \frac{R_n}{Z_o}}$$


$$\Gamma_L = \left( S_{22} + \frac{S_{12}S_{21}\Gamma_{in}}{1 - S_{11}\Gamma_{in}} \right)^*$$

**APPENDIX III**

**[EEE 532]**

NAME	TITLE	DWG. NO.
SMITH CHART FORM 27-01-N	Microwave Circuit Design - EEE23 - Fall 2000	DATE

**NORMALIZED IMPEDANCE AND ADMITTANCE COORDINATES**

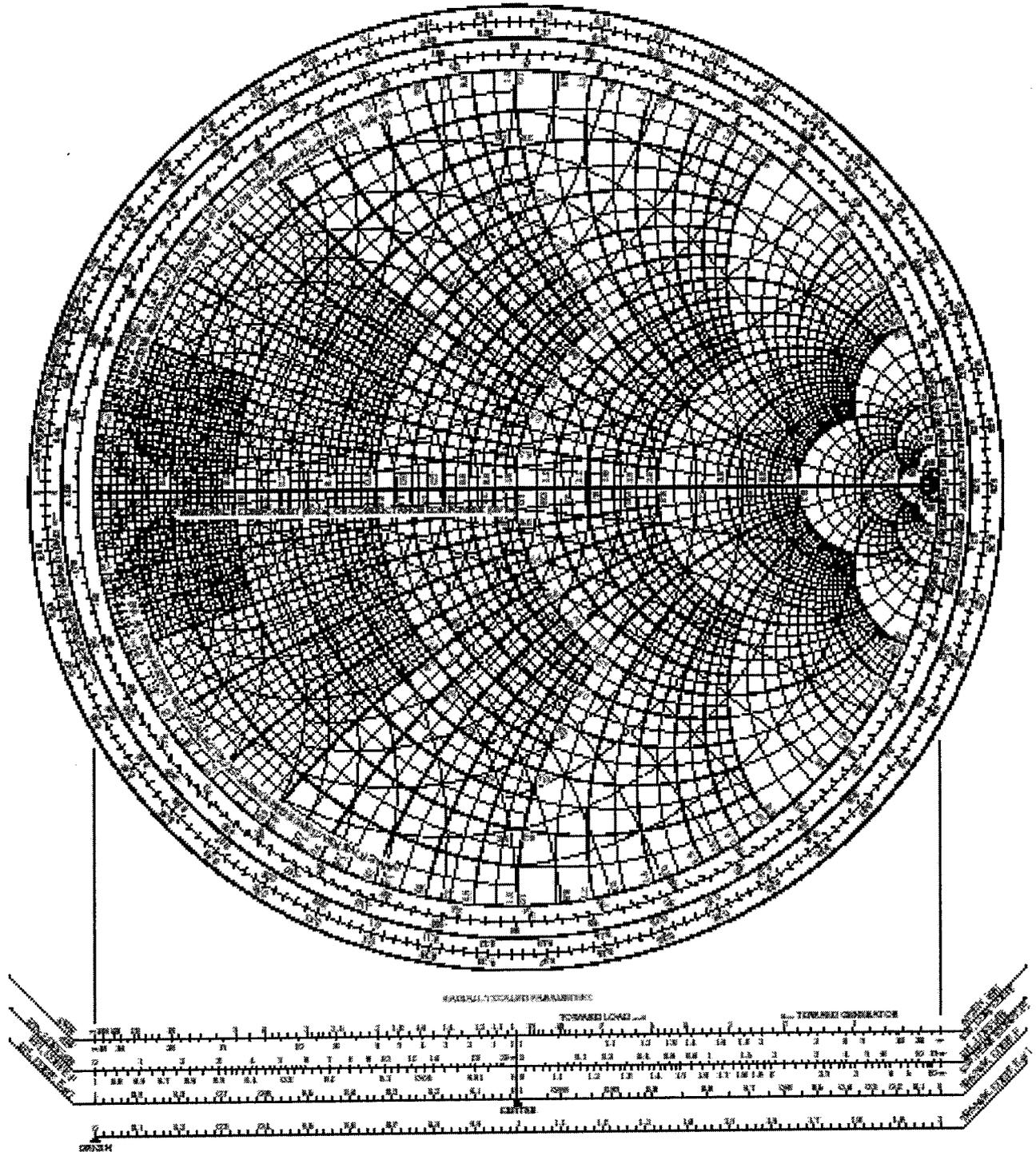

NE34018

**ABSOLUTE MAXIMUM RATINGS<sup>1</sup>** (T<sub>A</sub> = 25°C)

SYMBOLS	PARAMETERS	UNITS	RATINGS
V <sub>DS</sub>	Drain to Source Voltage	V	4
V <sub>GD0</sub>	Gate to Drain Voltage	V	-3
V <sub>GSO</sub>	Gate to Source Voltage	V	-3
I <sub>DS</sub>	Drain Current	mA	I <sub>DSS</sub>
T <sub>CH</sub>	Channel Temperature	°C	125
T <sub>SRG</sub>	Storage Temperature	°C	-65 to +125
P <sub>T</sub>	Total Power Dissipation	mW	150


Note:

1. Operation in excess of any one of these parameters may result in permanent damage.



**TYPICAL NOISE PARAMETERS** (T<sub>A</sub> = 25°C)

FREQ. (MHz)	NF <sub>OPT</sub> (dB)	G <sub>A</sub> (dB)	Γ <sub>OPT</sub>		R <sub>n</sub> /50
			MAG	ANG	
<b>V<sub>DS</sub> = 2 V, I<sub>DS</sub> = 10 mA</b>					
900	.56	20.5	.76	30	.45
2000	.63	16.3	.61	41	.28
2500	.68	14.1	.49	51	.18
3000	.70	13.6	.39	49	.16
3500	.76	12.3	.28	71	.12
4000	.82	11.6	.20	80	.10
<b>V<sub>DS</sub> = 2 V, I<sub>DS</sub> = 30 mA</b>					
2000	.60	17.0	.56	39	.23
2500	.70	15.3	.43	46	.15
3000	.76	14.2	.32	50	.26
<b>V<sub>DS</sub> = 3 V, I<sub>DS</sub> = 20 mA</b>					
900	.56	20.2	.74	26	1.54
2000	.62	16.8	.62	42	.43
2500	.66	14.9	.56	50	.31
3000	.70	14.0	.45	65	.24
3500	.80	13.2	.36	76	.14
4000	.84	12.8	.29	85	.10
4500	.90	11.0	.20	98	.08

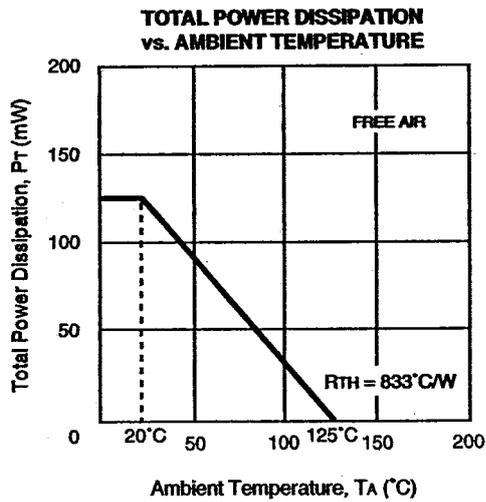**TYPICAL PERFORMANCE CURVES** (T<sub>A</sub> = 25°C)



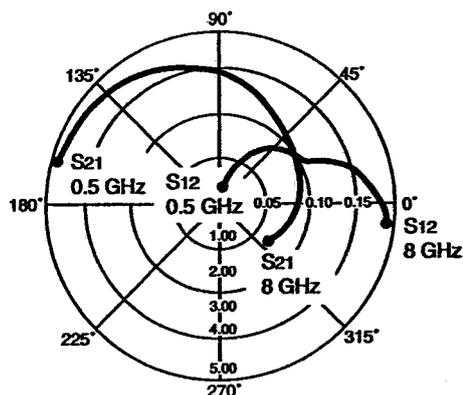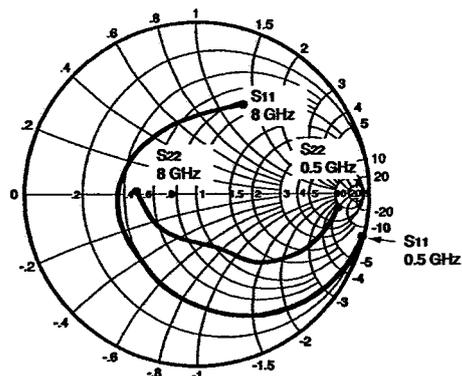**TYPICAL SCATTERING PARAMETERS (TA = 25°C)**



V<sub>DS</sub> = 2 V, I<sub>DS</sub> = 5 mA

FREQUENCY (GHz)	S <sub>11</sub>		S <sub>21</sub>		S <sub>12</sub>		S <sub>22</sub>		K	MAG <sup>1</sup> (dB)
	MAG	ANG	MAG	ANG	MAG	ANG	MAG	ANG		
0.50	0.984	-15.1	4.945	165.0	0.020	80.6	0.807	-7.2	0.135	23.931
0.60	0.979	-18.0	4.908	162.3	0.023	78.9	0.803	-8.6	0.152	23.292
0.70	0.973	-21.0	4.899	159.4	0.027	77.0	0.798	-10.0	0.174	22.587
0.80	0.965	-23.9	4.871	156.7	0.031	75.3	0.793	-11.5	0.195	21.963
0.90	0.958	-26.8	4.843	153.9	0.034	73.7	0.788	-12.9	0.213	21.536
1.00	0.949	-29.8	4.825	151.1	0.038	72.1	0.781	-14.4	0.231	21.037
1.20	0.930	-35.7	4.783	145.6	0.045	68.7	0.767	-17.3	0.270	20.265
1.40	0.906	-41.5	4.723	140.2	0.052	65.4	0.751	-20.2	0.314	19.582
1.60	0.881	-47.5	4.660	134.7	0.058	62.2	0.734	-23.1	0.354	19.050
1.80	0.853	-53.6	4.605	129.3	0.064	59.1	0.715	-26.0	0.395	18.570
2.00	0.821	-59.8	4.531	123.8	0.070	56.0	0.696	-28.9	0.438	18.111
2.50	0.737	-76.3	4.332	110.5	0.082	48.2	0.648	-36.0	0.542	17.229
3.00	0.648	-94.2	4.092	97.6	0.092	41.4	0.600	-42.4	0.643	16.481
3.50	0.569	-113.6	3.805	85.3	0.098	35.3	0.556	-47.7	0.748	15.891
4.00	0.512	-133.0	3.516	73.9	0.102	30.5	0.518	-51.8	0.845	15.374
4.50	0.482	-150.9	3.248	63.8	0.105	27.2	0.480	-54.9	0.932	14.904
5.00	0.472	-165.2	3.025	54.7	0.108	25.3	0.444	-57.8	1.004	14.074
5.50	0.468	-175.7	2.846	46.4	0.112	24.5	0.405	-61.0	1.068	12.459
6.00	0.464	176.0	2.714	38.4	0.118	23.7	0.367	-65.4	1.107	11.622
6.50	0.456	167.9	2.601	30.5	0.126	22.4	0.331	-71.6	1.130	10.955
7.00	0.441	158.2	2.505	22.1	0.134	20.2	0.302	-80.8	1.149	10.372
7.50	0.422	144.3	2.417	13.3	0.142	18.0	0.283	-92.2	1.161	9.874
8.00	0.411	127.5	2.321	4.0	0.151	15.0	0.281	-105.9	1.152	9.503

Note:

1. Gain Calculations:

$$MAG = \frac{|S_{21}|}{|S_{12}|} (K \pm \sqrt{K^2 - 1})$$


. When  $K \leq 1$ , MAG is undefined and MSG values are used.  $MSG = \frac{|S_{21}|}{|S_{12}|}$ ,  $K = \frac{1 + |\Delta|^2 - |S_{11}|^2 - |S_{22}|^2}{2 |S_{12} S_{21}|}$ ,  $\Delta = S_{11} S_{22} - S_{21} S_{12}$

MAG = Maximum Available Gain

MSG = Maximum Stable Gain

# The Complete Smith Chart

## Black Magic Design

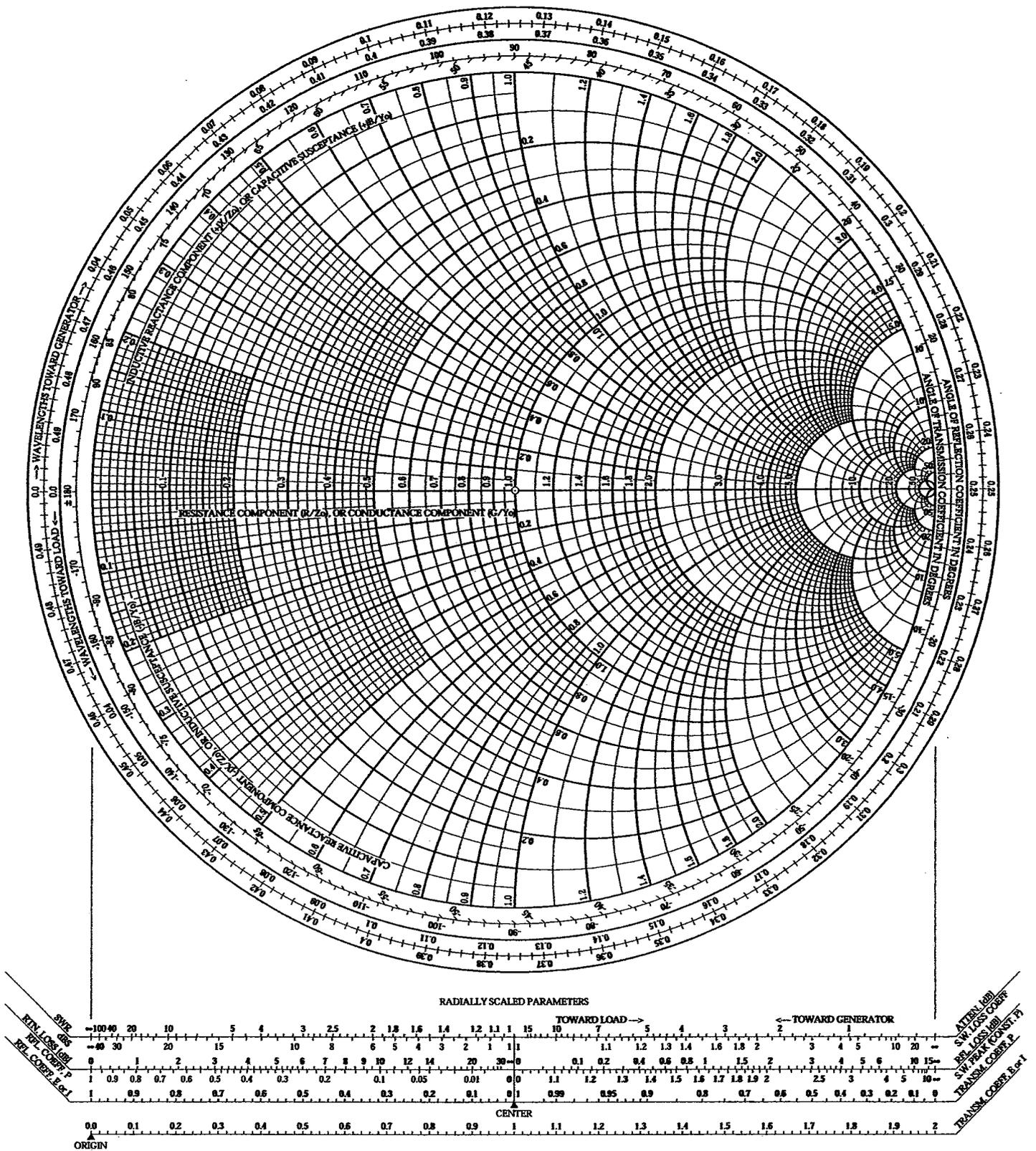

# The Complete Smith Chart

## Black Magic Design

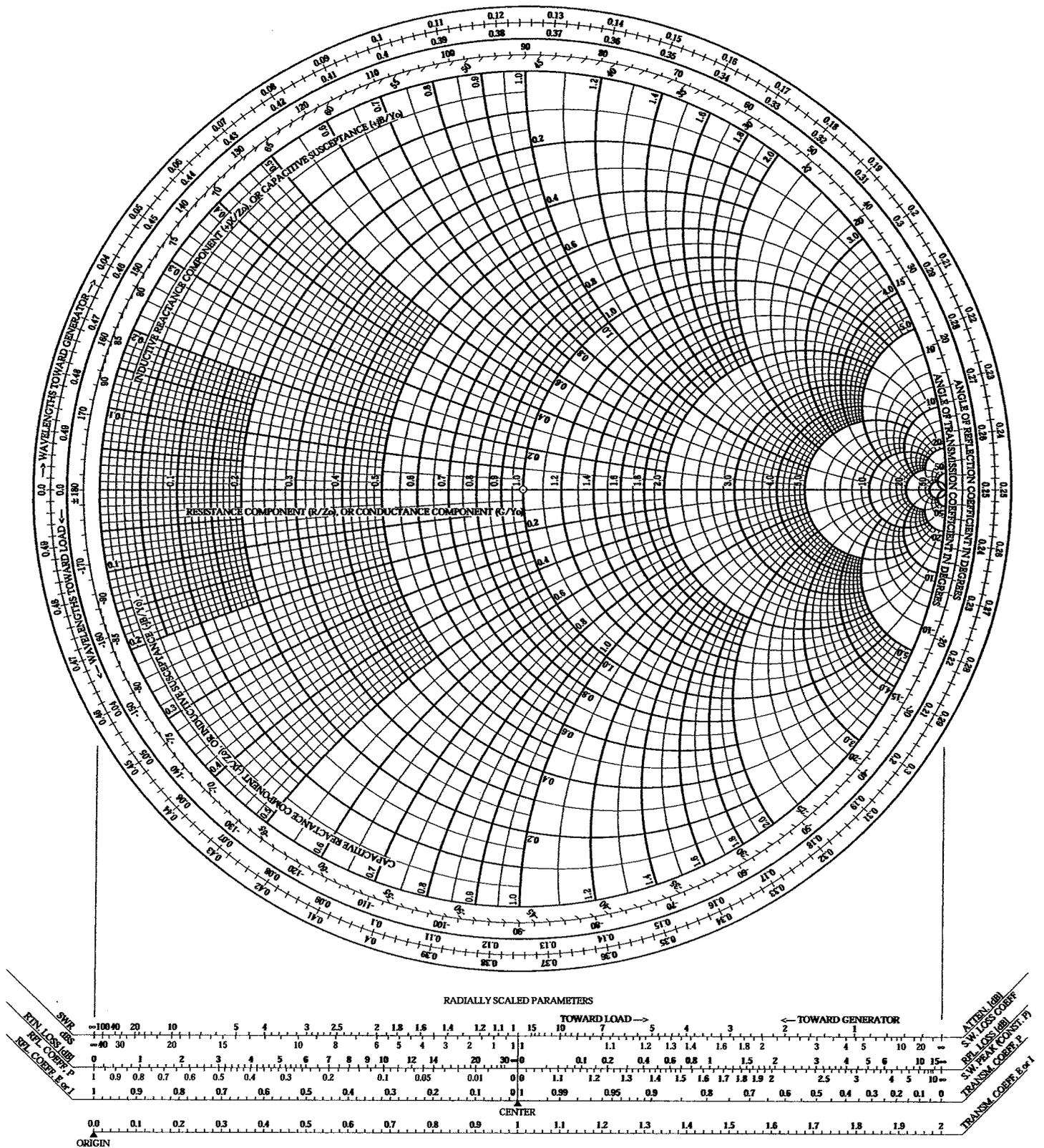


Table 1 Conversions between two-port network parameters

	<i>S</i>	<i>Z</i>	<i>Y</i>	<i>ABCD</i>
<i>S</i> <sub>11</sub>	<i>S</i> <sub>11</sub>	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 - D}$
<i>S</i> <sub>12</sub>	<i>S</i> <sub>12</sub>	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 - D}$
<i>S</i> <sub>21</sub>	<i>S</i> <sub>21</sub>	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 - D}$
<i>S</i> <sub>22</sub>	<i>S</i> <sub>22</sub>	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 - D}$
<i>Z</i> <sub>11</sub>	$Z_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>11</sub>	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
<i>Z</i> <sub>12</sub>	$Z_0 \frac{2S_{12}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>12</sub>	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
<i>Z</i> <sub>21</sub>	$Z_0 \frac{2S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>21</sub>	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
<i>Z</i> <sub>22</sub>	$Z_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}$	<i>Z</i> <sub>22</sub>	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
<i>Y</i> <sub>11</sub>	$Y_0 \frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{22}}{ Z }$	<i>Y</i> <sub>11</sub>	$\frac{D}{B}$
<i>Y</i> <sub>12</sub>	$Y_0 \frac{-2S_{12}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{12}}{ Z }$	<i>Y</i> <sub>12</sub>	$\frac{BC - AD}{B}$
<i>Y</i> <sub>21</sub>	$Y_0 \frac{-2S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{-Z_{21}}{ Z }$	<i>Y</i> <sub>21</sub>	$\frac{-1}{B}$
<i>Y</i> <sub>22</sub>	$Y_0 \frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}$	$\frac{Z_{11}}{ Z }$	<i>Y</i> <sub>22</sub>	$\frac{A}{B}$
<i>A</i>	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	<i>A</i>
<i>B</i>	$Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{ Z }{Z_{21}}$	$\frac{-1}{Y_{21}}$	<i>B</i>
<i>C</i>	$\frac{1}{Z_0} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{1}{Z_{21}}$	$\frac{- Y }{Y_{21}}$	<i>C</i>
<i>D</i>	$\frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{22}}{Z_{21}}$	$\frac{-Y_{11}}{Y_{21}}$	<i>D</i>

$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}$ ;  $|Y| = Y_{11}Y_{22} - Y_{12}Y_{21}$ ;  $\Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}$ ;  $\Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}$ ;  $Y_0 = 1/Z_0$

MU