
UNIVERSITI SAINS MALAYSIA
Peperiksaan Semester Pertama
Sidang Akademik 2004/2005

Oktober 2004

EEU 104 – TEKNOLOGI ELEKTRIK

Masa : 3 Jam

ARAHAN KEPADA CALON:-

Sila pastikan kertas peperiksaan ini mengandungi **SEBELAS** (11) muka surat bercetak dan **ENAM** (6) soalan sebelum anda memulakan peperiksaan ini.

Jawab **LIMA** (5) soalan.

Agihan markah diberikan di sisi sebelah kanan soalan berkenaan.

Semua soalan hendaklah dijawab di dalam Bahasa Malaysia.

1. (a) Penggunaan sebahagian daripada peralatan elektrik di sebuah rumah persendirian adalah seperti dalam Jadual 1. Sekiranya tarif tenaga elektrik ialah RM0.25/kWh, kira kos tenaga yang perlu dibayar oleh pengguna tersebut. (Anggapkan 1 hp = 746 W).

The usage of some of electrical household appliances in a private residence is as shown in Table 1. If the tariff for electrical energy is RM0.25/kWh, calculate the cost of electricity to be paid by the consumer. (Assume 1 hp = 746 W).

(40%)

JADUAL 1
TABLE 1

Peralatan <i>Appliance</i>	Kadar kuasa <i>Power rating</i>	Kuantiti (unit) <i>quantity (units)</i>	Kadar penggunaan sehari (jam) <i>Usage per day (hours)</i>
1. Penyaman udara (<i>air-conditioner</i>)	1.5 hp	2	4
2. Pemanas air (<i>water heater</i>)	3.5 kW	2	0.75
3. Lampu (<i>electric lamp</i>)	40 W	24	1.5
4. Ketuhar (<i>oven</i>)	4 kW	1	2
5. Peti sejuk (<i>refrigerator</i>)	200 W	2	8
6. Peti televisyen (<i>television</i>)	190 W	3	4.5
7. Seterika (<i>electric iron</i>)	750 W	1	1

- (b) Satu punca elektrik membekalkan arus sebanyak 30 A kepada satu alat menerusi sepasang dawai tembaga sepanjang 50 m. Garispusat keratan rentas dawai ialah 3.5 mm. Kira kejatuhan voltan sepanjang dawai dan kuasa yang dilesapkan oleh dawai. (Andaikan kerintangan bagi tembaga ialah $0.01723 \times 10^{-6} \Omega\text{-m}$).

An electric source supplies 30 A to an electrical equipment through a pair of 50 m copper wire. The cross-sectional diameter of the wire is 3.5 mm. Calculate the voltage across the whole length of the wire and the power dissipated by the wire. (Assume the resistivity of copper is $0.01723 \times 10^{-6} \Omega\text{-m}$).

(30%)

- (c) Gegelung tembaga sebuah motor elektrik mengambil arus sebanyak 1.47 A daripada punca voltan 240 V. Setelah beroperasi beberapa jam, arus turun kepada nilai yang stabil 1.25 A. Kira suhu gegelung. (Andaikan pekali suhu rintangan bagi tembaga pada suhu 20 °C ialah 0.00393).

The copper winding of an electric motor draws 1.47 A from a 240 V source when its temperature is 20 °C. After operating for several hours, the current drops to a stable value of 1.25 A. Calculate the temperature of the winding. (Assume the temperature coefficient for copper at 20 °C is 0.00393).

(30%)

2. (a) Cari nilai I_S , I_2 dan V_3 dalam Rajah 2(a).


Find I_S , I_2 and V_3 in Figure 2(a).

(30%)

- (b) Cari nilai I dan V_a dalam Rajah 2(b).

Find I and V_a in Figure 2(b).

(30%)

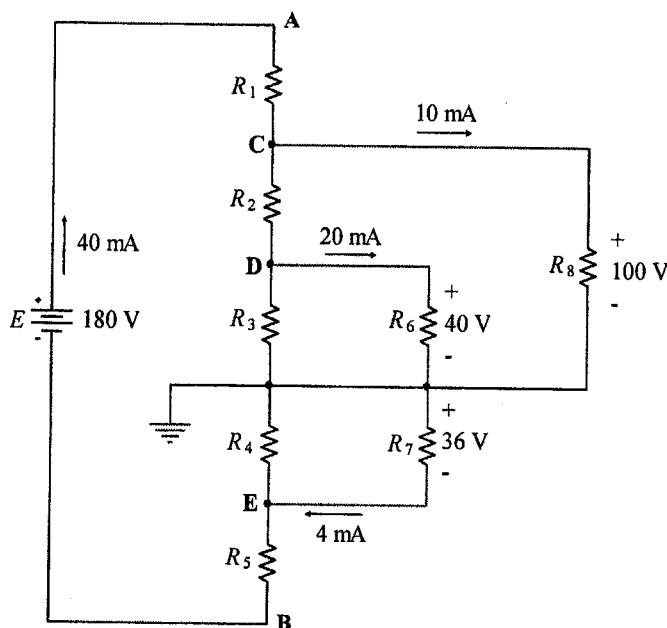

Rajah 2(c)
Figure 2(c)

3. (a) Gunakan gelung-gelung I_1 dan I_2 seperti yang ditandakan dalam Rajah 3(a) bagi mendapatkan persamaan-persamaan gelung bagi rangkaian.

Use the loops I_1 and I_2 indicated in Figure 3(a) to obtain the mesh equations for the network.


(20%)

- (b) Cari beza upaya pada titik **b** dalam **Rajah 3(a)** dengan menggunakan persamaan-persamaan yang diperolehi dalam (a) di atas atau dengan cara-cara lain.

Find the potential at point **b** in Figure 3(a) by means of the equations obtained in (a) above or any other method.

(20%)

...6/-

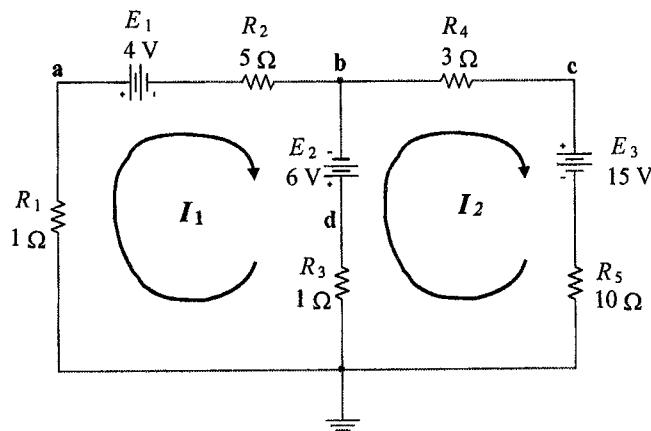

Rajah 3(a)
Figure 3(a)

- (c) Dengan menggunakan arus-arus I_1 , I_2 , I_3 , I_4 dan I_5 seperti yang ditandakan dalam **Rajah 3(b)**, dapatkan persamaan-persamaan nod 1 dan nod 2.


*Use the currents I_1 , I_2 , I_3 , I_4 and I_5 as indicated in **Figure 3(b)**, to obtain the nodal equations for node 1 and node 2.*

(30%)

- (d) Dengan menggunakan persamaan-persamaan yang diperolehi dalam (c) di atas atau dengan cara lain, cari kuasa yang dilepas oleh R_3 dalam **Rajah 3(b)**.

*By means of the equations obtained in (c) above or otherwise, find the power dissipated by R_3 in **Figure 3(b)**.*

(30%)

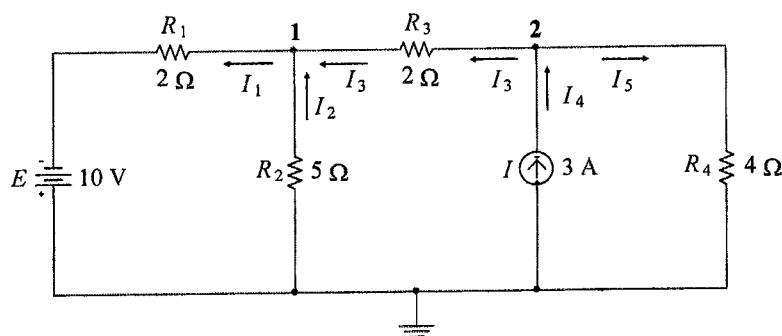

...71-

Rajah 3(b)
Figure 3(b)

4. (a) Satu persamaan voltan diwakili oleh $v = 282.8 \sin(3142 t)$ volt membekali satu litar dengan galangan 50 ohm dan arus yang mengalir ketinggalan sebanyak 20° kepada voltan bekalan. Cari

A voltage represented by $v = 282.8 \sin(3142 t)$ volt is applied to a circuit of impedance 50 ohms and current lags the supply voltage by 20° . Find

- [i] frekuensi
frequency
- [ii] arus puncak, I_m
peak current I_m
- [iii] arus I
current I
- [iv] rintangan, R
resistance R
- [v] kearuhan, L dan
inductance L and
- [vi] voltan pmkd merentasi R
rms voltage across R .

(50%)

- (b) Satu gegelung aruhan mempunyai nilai $L = 0.05 \text{ H}$ dan rintangan $R = 100 \text{ ohm}$ dijadikan litar beresonan dengan menyambungkan satu pemuat, $C = 0.01 \text{ mikrofarad}$ secara selari dengan gegelung aruhan. Kirakan

An inductance coil having $L = 0.05 \text{ H}$ and a resistance $R = 100 \text{ ohms}$ is tuned to resonance by connecting a capacitor of $C = 0.01 \text{ micro farads}$ in parallel with inductive coil. Calculate

[i] jumlah galangan

total impedance

[ii] frekuensi resonan jika mengambil kira nilai R dan

frequency of resonance taking R into account and

[iii] frekuensi resonan tanpa mengambil kira nilai R

frequency of resonance, neglecting R .

(50%)

5. (a) Tiga gegelung aruhan mempunyai nilai galangan yang sama setiap satu disambungkan secara bintang kepada bekalan voltan 3-fasa seimbang 400 V, 50 Hz dan menghasilkan arus sebanyak 20 A. Jumlah kuasa yang diserap ialah 12 kW. Cari

Three inductive coils of same impedance are connected in star and a balanced 3-phase voltage of 400 V, 50Hz is impressed across it, which caused a current of 20 A. The total power absorbed is 12 KW. Find

[i] rintangan, R

resistance R

9/-...

- [ii] kearuhan, **L** dan
inductance L, and
- [iii] jika sambungan litar diubah kepada sambungan delta, cari jumlah kuasa yang diserap bagi bekalan voltan yang sama.

if now these three coils are connected in delta, calculate the total power absorbed with the same supply.

(50%)


- (b) Bagi litar R, L dan C siri yang ditunjukkan dalam Rajah 5 (b), cari
For the following R, L and C series circuit shown in Figure 5(b), find

$$i = 25 \sin(314t - 65^\circ) \text{ dan } v = 707 \sin(314t - 20^\circ)$$

$$i = 25 \sin(314 t - 65^\circ) \text{ and } v = 707 \sin(314 t - 20^\circ)$$

- [i] rintangan, **R**
resistance R
- [ii] kemuatan, **C**
capacitance C
- [iii] kuasa kompleks, **S** dan
complex power, S and
- [iv] lukiskan gambarajah vektor/fasa
draw vector diagram.

(50%)

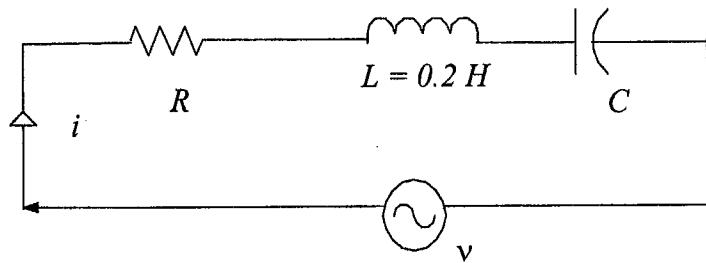


Rajah 5(b)
Figure 5(b)

6. (a) Bagi gambarajah alatubah seperti dalam Rajah 6 (a), cari kecekapan, dalam unit % pada beban separuh dengan faktor kuasa 0.8 ketinggalan. Diberikan kehilangan kuprum beban-penuh $P_c = 160 \text{ W}$ dan kehilangan besi $P_i = 100 \text{ W}$.

For the following transformer shown in Figure 6(a), find percentage efficiency in unit % at half full load and 0.8 pf lag. Given full load copper loss $P_c = 160 \text{ watts}$ and iron loss $P_i = 100 \text{ watts}$.

(40%)

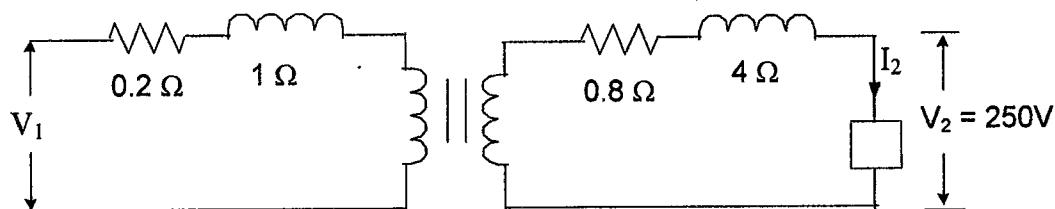

$$\frac{N_2}{N_1} = 2 = K$$

Rajah 6(a)
Figure 6(a)

... 11/-

- (b) Bahagian primer sebuah alatubah disambungkan kepada bekalan voltan 250V, 50 Hz. Lilitan primer ialah 250 dan lilitan sekunder ialah 500. Cari

The primary of a transformer is connected to 250 V, 50 Hz supply. Primary turns are 250 and secondary turns are 500. Find

[i] voltan sekunder, V_2

secondary voltage V_2

[ii] fluks maksimum

maximum flux

(20%)

- (c) Sebuah alatubah mempunyai rintangan primer dan sekunder iaitu 5 ohm dan 10 ohm beserta reaktan iaitu 10 ohm dan 20 ohm masing-masing. Nisbah lilitan ialah 1 : 2. Apakah nilai galangan setara merujuk kepada

A transformer has primary and secondary resistances of 5 ohms and 10 ohms and reactances of 10 ohms and 20 ohms. Turn ratio is 1:2. What is the equivalent impedance referred to

[i] primer

primary

[ii] sekunder

secondary

(40%)