



Second Semester Examination  
2017/2018 Academic Session

May/June 2018

**EEE 505 – Advanced Analog Integrated Circuit Design**

Duration : 3 hours

---

Please ensure that this examination paper consists of **SEVEN (7)** pages before you begin the examination.

Instructions: Answer **FIVE (5)** questions. Answer **TWO (2)** questions in Part A and **TWO (2)** questions from Part B and **ONE (1)** question from any section.

Use two-book answers for **Part A** and **Part B**.

All questions carry the same marks

...2/-

**Part A :**

1. Investigate the cascode configuration of multi-transistor  $M_1$  (common-source) and  $M_2$  (common-gate) as shown in Figure 1 below.
  - (a) Draw the small signal model for the circuit. (6 marks)
  - (b) Derive the expression for output resistance,  $R_O$ . (6 marks)
  - (c) Give your opinion on the method of increasing output resistance using the cascode configuration. [Hint: You may need to find the expression for small signal voltage gain,  $A_v$ .] (8 marks)

 


Figure 1.

2. By referring to Figure 2 below,

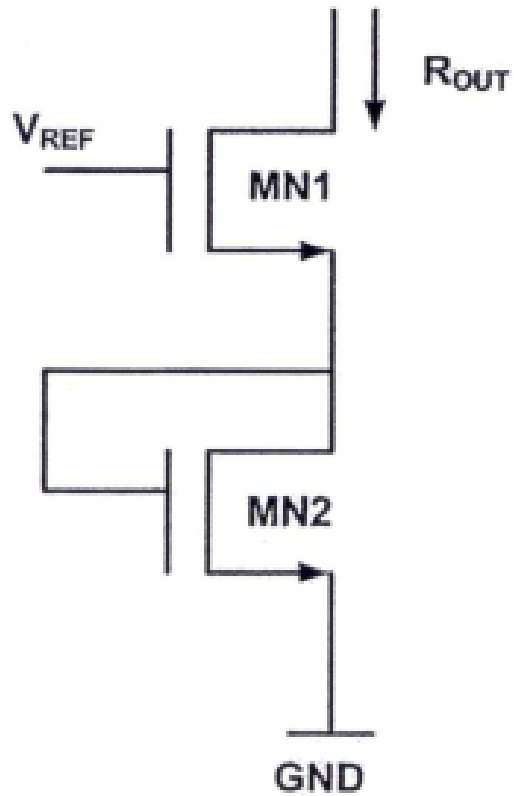


Figure 2

(a) Draw the small signal model for the circuit.

(10 marks)

(b) Derive the expression for  $R_{out}$ .

(10 marks)

3. Figure 3 refers to a differential amplifier design with common-mode and differential-mode inputs.

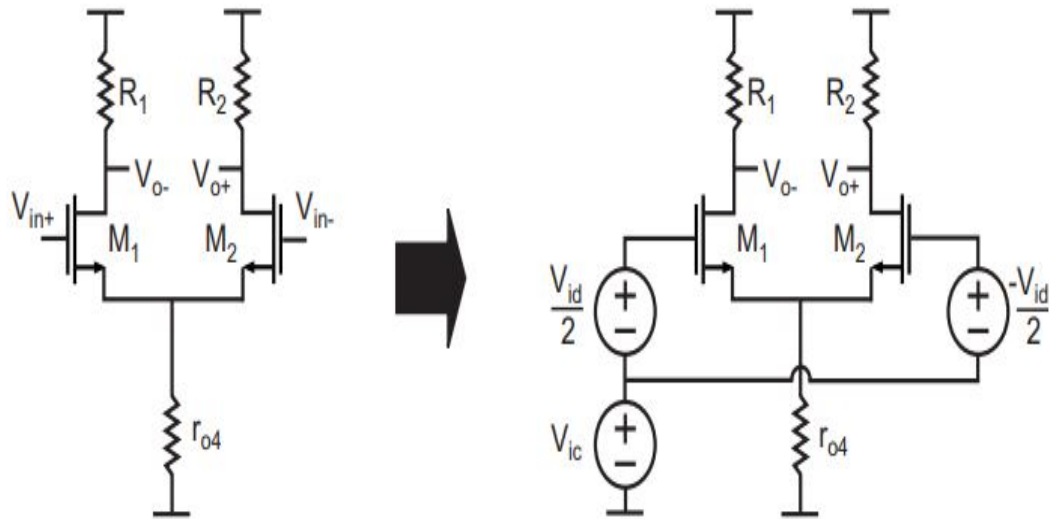


Figure 3

- (a) Derive the differential-mode gain,  $A_{dm}$ .

(10 marks)

- (b) Derive the common-mode gain,  $A_{cm}$ .

(10 marks)

**Part B :**

4.

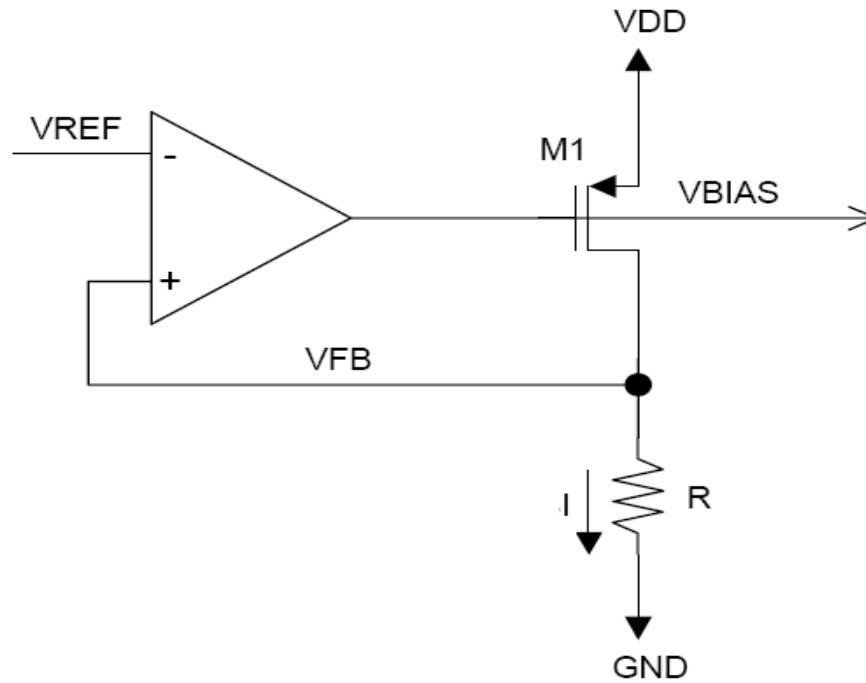


Figure 4:

- (a) Figure 4 shows the biasing circuitries for a typical current steering DAC.
- (i) Explain the function of the operational amplifier. (2 marks)
  - (ii) What is the value of current  $I$ , if  $R$  is  $1.2 \text{ k}\Omega$  and  $V_{REF} = 1.2 \text{ V}$ ? (2 marks)
  - (iii) Assuming  $V_{DD} = 3.6 \text{ V}$  and  $M1$  is in saturation,  $W/L = 12/2$ ,  $V_{tp} = -1\text{V}$ ,  $K_p = 40 \mu\text{A/V}^2$ , calculate the required  $V_{SG}$ . (6 marks)

...6/-

- (b) Draw the basic 6-bit DAC which must include the biasing circuitries and the DAC resistor string. (10 marks)
5. (a) (i) State a simplified 3-bit DAC mathematical model. The model is based on current steering-resistor string approach.
- (ii) Draw the schematic of the DAC.
- (iii) Explain the functions of all the components in the schematic. (12 marks)
- (b) Extend the model up to 8-bit. Explain your model. (8 marks)
- 6.

 


Figure 6: Switched Capacitor Resistor

- (a) Figure 6 illustrates the switched capacitor resistor circuit. By referring to the figure:
- (i) Explain the function of C. (2 marks)
- (ii) Derive the equivalent resistance of the circuit in Figure 6. (6 marks)

(iii) Calculate the resistance if the clock frequency is 0.5 MHz and  $C$  is 1 pF.  
(2 marks)

(b) What is the operation of MOSFET whereby the behaviour of  $V_{GS}$  is similar as  $V_{BE}$  of bandgap device? Together with switched capacitor resistor, design a PTAT current generator. The final equation must be included together with the design.

(10 marks)