



Second Semester Examination  
2017/2018 Academic Session

May/June 2018

**EEK373 – ADVANCED POWER ELECTRONICS  
(ELEKTRONIK KUASA LANJUTAN)**

Duration : 3 hours  
(Masa : 3 jam)

---

Please ensure that this examination paper consists of THIRTEEN (13) pages and SEVEN (7) pages of printed appendices material before you begin the examination.

[*Sila pastikan bahawa kertas peperiksaan ini mengandungi TIGA BELAS (13) muka surat dan TUJUH (7) muka surat lampiran yang bercetak sebelum anda memulakan peperiksaan ini.*]

**Instructions:** This question paper consists of **FIVE (5)** questions. Answer **ALL** questions. All questions carry the same marks.

**Arahian:** *Kertas soalan ini mengandungi **LIMA (5)** soalan. Jawab **SEMUA** soalan. Semua soalan membawa jumlah markah yang sama.]*

In the event of any discrepancies, the English version shall be used.

*[Sekiranya terdapat sebarang percanggahan pada soalan peperiksaan, versi Bahasa Inggeris hendaklah digunakan.]*

1. (a) Describe and compare the operation of on-off control, phase control and cyclo-converter of AC-AC voltage converters. Sketch simple diagrams to illustrate the output waveform of each converter.

*Terang dan bandingkan operasi kawalan on-off, kawalan fasa dan penukar-siklo bagi penukar voltan AC-AC. Lakarkan gambar rajah mudah bentuk gelombang keluaran bagi setiap penukar*

(30 marks/markah)

- (b) The ac voltage controller is used for heating resistive load of  $R = 5\Omega$  and the input voltage  $V_s = 230V, 50Hz$ . The thyristor switch is on for  $n = 125$  cycles and is off for  $m = 75$  cycles. Determine;

*Pengawal voltan AC-AC digunakan untuk pemanasan rintangan beban sebanyak  $R = 5\Omega$ . Voltan masuk adalah  $V_s = 230V, 50Hz$ . Suis tiristor dihidupkan untuk  $n = 125$  kitaran dan dimatikan untuk  $m = 75$  kitaran. Tentukan;*

- (i) The rms output voltage,  $V_o$

*Nilai rms voltan keluaran,  $V_o$*

(10 marks/markah)

- (ii) The input power factor, PF

*Nilai faktor kuasa masuk, PF*

(10 marks/markah)

- (iii) The average and rms thyristor currents

*Nilai purata dan rms arus tiristor*

(10 marks/markah)

- (c) A single phase full wave ac voltage controller has a resistive load of  $R = 10 \Omega$  and the input voltage is  $V_s = 230V, 50Hz$ . The delay angle of thyristor T1 and T2 are equal:  $\alpha_1 = \alpha_2 = \alpha = \pi/3$ . Determine

*Sebuah pengawal AC fasa tunggal penuh mempunyai beban rintangan  $R = 10 \Omega$  dan disambungkan kepada sumber  $V_s = 230V, 50Hz$ . Sudut kelewatan bagi tiristor T1 dan T2 adalah sama:  $\alpha_1 = \alpha_2 = \alpha = \pi/3$ . Tentukan*

- (i) The rms output voltage  $V_o$

*Nilai rms voltan keluaran,  $V_o$*

(10 marks/markah)

- (ii) The input power factor PF

*Nilai faktor kuasa masuk PF*

(10 marks/markah)

- (iii) The average current of thyristor

*Nilai arus purata tiristor*

(10 marks/markah)

- (iv) The rms current of thyristor

*Nilai arus rms tiristor*

(10 marks/markah)

2. (a) With the aid of diagram, explain the operation of forward converter for ON and OFF respectively, your answer should include the derivations and waveforms.

*Dengan bantuan gambarajah, terangkan operasi bagi penukar depan semasa suis masing-masing dihidupkan dan dimatikan, jawapan anda mesti merangkumi penerbitan dan bentuk gelombang.*

(50 marks/markah)

- (b) A fly-back converter with a 1:3 turn ratio is supplied with 24 V as source voltage. The magnetizing inductance and the capacitance are 500  $\mu\text{H}$  and 200  $\mu\text{F}$  respectively. The load consists of  $7 \Omega$  and the output voltage across the load is 5 V. If the converter is operated with switching frequency of 40 kHz, calculate the following:

*Satu penukar terbang-balik dengan nisbah pusingan 1:3 dibekalkan voltan 24 V. Kearuhan pemagnetan dan kemuatan masing-masing adalah 500  $\mu\text{H}$  and 200  $\mu\text{F}$ . Beban terdiri daripada  $7 \Omega$  dan voltan keluaran merentasi beban adalah 5 V. Jikalau penukar tersebut beroperasi pada frekuensi pensuisan 40 kHz, kirakan:*

- (i) required duty cycle.

*kitar tugas yang diperlukan.*

(16 marks/markah)

- (ii) average, maximum and minimum magnetizing inductance currents.

*nilai purata, maxima dan minima bagi arus kearahan pemagnetan.*

(24 marks/markah)

- (iii) output voltage ripple in percentage.

*riak voltan keluaran dalam peratus.*

(10 marks/markah)

3. (a) A three-phase inverter bridge shown in Figure Q 3 transfers power from an ideal DC bus bar of  $V_d = 600$  V to a three-phase resistive load of  $R = 100 \Omega$  per phase using  $120^\circ$  conduction. The switching and voltage waveforms of phase voltages  $V_{as}$ ,  $V_{bs}$  and  $V_{cs}$  are given in Figure Q 3.

*Satu penyongsang tiga fasa yang ditunjukkan dalam Rajah Q 3 mengalami pindahan kuasa dari satu palang bus unggul  $V_d = 600$  V ke satu beban rintangan tiga fasa  $R = 100 \Omega$  per fasa dengan  $120^\circ$  mod pengaliran. Gelombang pensuisan dan voltan fasa  $V_{as}$ ,  $V_{bs}$  dan  $V_{cs}$  adalah yang seperti ditunjukkan dalam Rajah Q 3.*

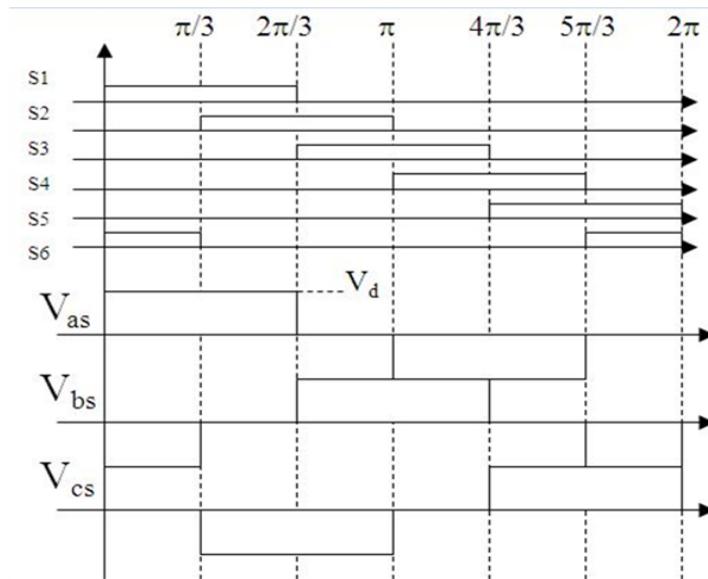
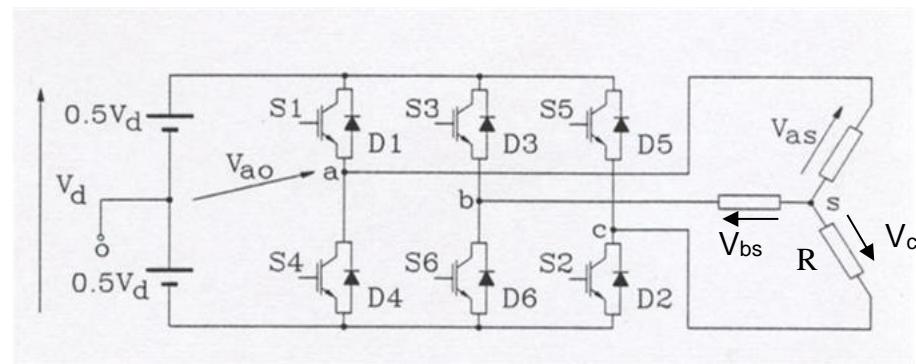


Figure Q 3 Switching and voltage waveforms of phase voltages  $V_{as}$ ,  $V_{bs}$  and  $V_{cs}$   
*Rajah Q 3 Gelombang pensuisan dan voltan fasa  $V_{as}$ ,  $V_{bs}$  dan  $V_{cs}$*

- (i) Indicate which of the six switches are conducting during each interval of the cycle.

*Tunjukkan suis yang dihidupkan setiap selang masa bagi kitar tersebut.*

(15 marks/markah)

- (ii) Sketch the waveforms for line voltages  $V_{AB}$ ,  $V_{BC}$  and  $V_{CA}$ .

*Lakarkan gelombang bagi voltan talian  $V_{AB}$ ,  $V_{BC}$  and  $V_{CA}$ .*

(18 marks/markah)

- (b) With the balanced three-phase resistive load of  $R = 100 \Omega$  connected in star shown in Figure Q 3, calculate:

*Dengan satu beban rintangan seimbang tiga fasa  $R = 100 \Omega$  disambung secara bintang seperti yang ditunjukkan dalam Rajah Q 3, kirakan:*

- (i) the rms phase current.

*Nilai rms arus fasa.*

(13 marks/markah)

- (ii) the source current.

*arus bekalan.*

(10 marks/markah)

- (c) A single-phase voltage source inverter is supplied with input voltage  $V_{dc} = 200$  V for RL load. Calculate the following for  $180^\circ$  conduction mode:

*Satu penyongsang sumber voltan satu fasa dibekalkan dengan voltan masukan  $V_{dc} = 200$  V bagi bebanan RL. Dengan menggunakan  $180^\circ$  mod pengaliran, kirakan:*

- (i) Distortion factor.

*faktor herotan.*

(29 marks/markah)

- (ii) the total harmonic distortion.

*jumlah herotan harmonik.*

(15 marks/markah)

4. (a) A series resonant inverter circuit as shown in Figure Q 4 (a), has  $C = 5 \mu F$ ,  $L = 30 \mu H$ ,  $R = 0$ , and  $V_s = 220V$ . The turn-off time of transistor,  $t_{off} = 15\mu s$ . The output frequency is  $f_o = 20$  kHz.

*Suatu siri litar penyongsang resonan seperti ditunjukkan dalam Rajah Q 4 (a), mempunyai  $C = 5 \mu F$ ,  $L = 30 \mu H$ ,  $R = 0$ , dan  $V_s = 220V$ . Masa mematikan transistor,  $t_{off} = 15\mu s$ . Frekuensi keluaran adalah  $f_o = 20$  kHz.*

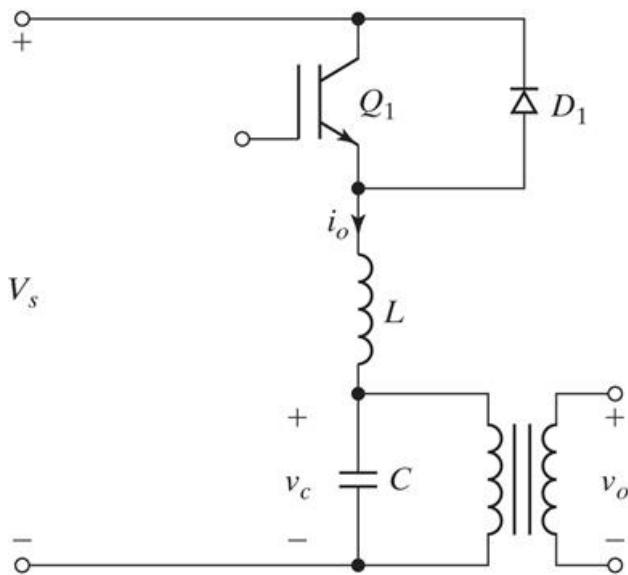


Figure Q 4 (a)  
Rajah Q 4 (a)

- (i) Determine the peak supply current  $I_p$

*Tentukan arus masukan puncak  $I_p$ .*

(5 marks/markah)

- (ii) Determine the average current  $I_A$

*Tentukan arus purata  $I_A$ .*

(15 marks/markah)

- (iii) Determine the rms device current  $I_R$

*Tentukan nilai rms arus peranti  $I_R$ .*

(15 marks/markah)

- (iv) Determine the peak to peak capacitor voltage  $V_{pp}$

*Tentukan nilai puncak ke puncak voltan kapasitor  $V_{pp}$ .*

(5 marks/markah)

- (v) Determine the maximum inverter frequency  $f_{\max}$

*Tentukan frekuensi maksimum penyongsang  $f_{\max}$ .*

(10 marks/markah)

- (vi) Determine the average supply current  $I_s$

*Tentukan arus purata bekalan  $I_s$ .*

(5 marks/markah)

- (b) A parallel resonant inverter as in Figure Q 4 (b) delivers a load power of  $P_L = 3 \text{ kW}$  at a peak sinusoidal load voltage of  $V_p = 220 \text{ V}$  and at resonance. The load resistance is  $R = 7.5 \Omega$ . The resonant frequency is  $f_o = 30 \text{ kHz}$ .

*Suatu penyongsang resonan sejajar seperti dalam Rajah Q 4 (b) menyampaikan kuasa beban sebanyak  $P_L = 3 \text{ kW}$  pada voltan beban sinusoidal puncak  $V_p = 220 \text{ V}$  dan pada resonan. Rintangan beban adalah  $R = 7.5 \Omega$ . Frekuensi resonan adalah  $f_o = 30 \text{ kHz}$ .*

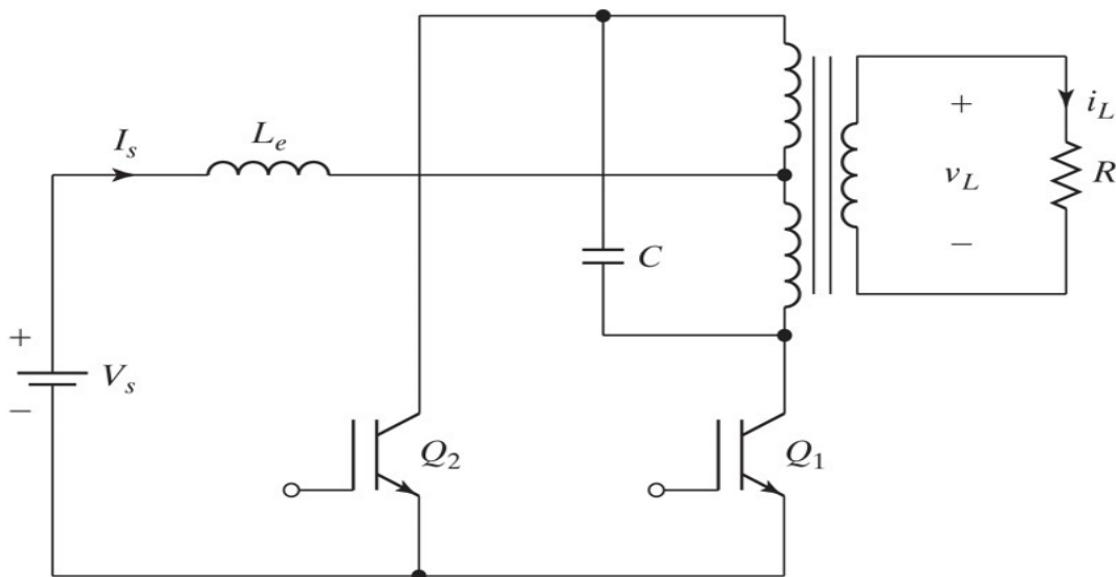


Figure Q 4 (b)

Rajah Q 4 (b)

...10/-

- (i) Determine the dc supply input current  $I_s$

*Tentukan arus masukan dc bekalan  $I_s$ .*

(10 marks/markah)

- (ii) Determine the quality factor  $Q_p$  if it is required to reduce the load power to 1500 W by frequency control so that  $u = 1.25$

*Tentukan faktor kualiti  $Q_p$  jika kuasa beban perlu dikurangkan kepada 1500 W oleh frekuensi kawalan supaya  $u = 1.25$*

(10 marks/markah)

- (iii) Determine the capacitor C value

*Tentukan nilai muatan C.*

(10 marks/markah)

- (iv) Determine the inductor L value

*Tentukan nilai aruhan L.*

(10 marks/markah)

5. (a) Figure Q 5 (a) shows an example of Flyback converter. There are two modes of operation: (1) mode 1 when switch Q1 is turned on, and (2) mode 2 when switch Q1 is turned off.

*Rajah Q 5 (a) menunjukkan contoh penukar Flyback. Terdapat dua mod operasi: (1) mod 1 apabila suis Q1 dihidupkan, dan (2) mod 2 apabila suis Q1 dimatikan.*

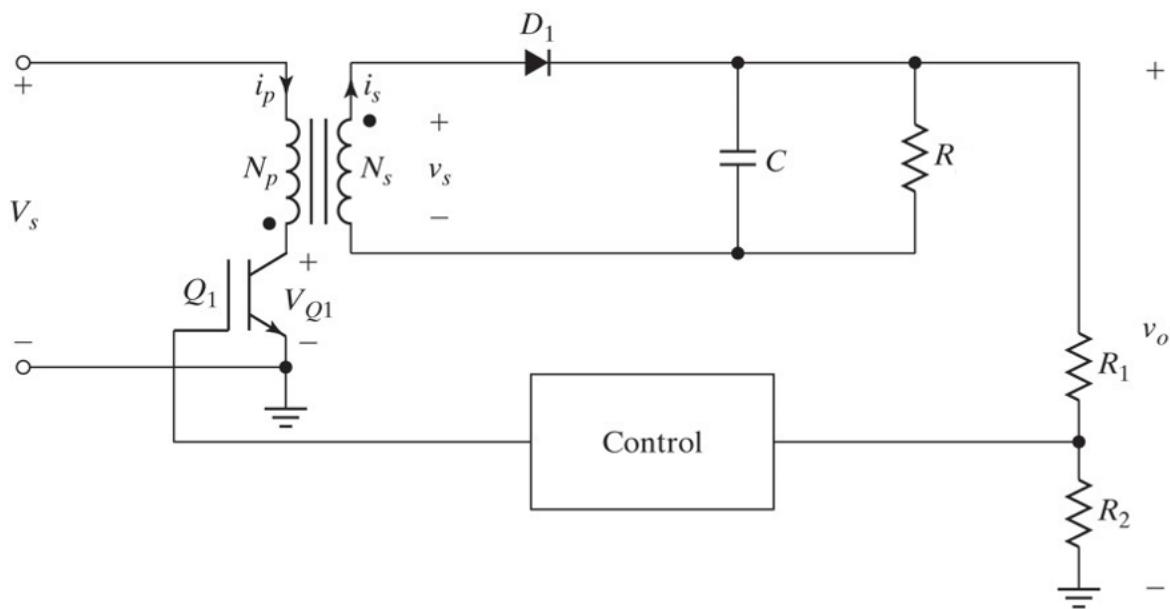


Figure Q 5 (a)

Rajah Q 5 (a)

- (i) Explain briefly about the operation of the circuit, subjected to the main application of this circuit and the two operation (1) mode 1 when switch  $Q_1$  is turned on, and (2) mode 2 when switch  $Q_1$  is turned off.

*Terangkan secara ringkas mengenai operasi litar, tertakluk kepada aplikasi utama litar ini dan dua operasi (1) mod 1 apabila suis  $Q_1$  dihidupkan, dan (2) mod 2 apabila suis  $Q_1$  dimatikan.*

(15 marks/markah)

- (ii) Sketch waveforms of transistor  $Q_1$  voltage  $V_{Q1}$ , secondary voltage  $V_s$ , primary current  $i_p$ , secondary current  $i_s$  and output voltage  $V_o$

*Lakarkan bentuk gelombang voltan transistor  $Q_1$   $V_{Q1}$ , voltan sekunder  $V_s$ , arus premier  $i_p$ , arus sekunder  $i_s$  dan voltan keluaran  $V_o$ .*

(30 marks/markah)

- (iii) Double-ended Flyback converter is used when the voltage supply is too high and above voltage  $V_{Q1}$ . Draw a double-ended flyback converter by referring to Figure Q 5 (a).

*Penukar Flyback dua hala digunakan apabila bekalan voltan terlalu tinggi dan melebihi voltan  $V_{Q1}$ . Lukiskan penukar flyback dua hujung dengan merujuk kepada Rajah Q 5 (a).*

(15 marks/markah)

- (b) Figure Q 5 (b) shows an example of Forward converter.

*Rajah Q 5 (b) menunjukkan contoh penukar hadapan.*

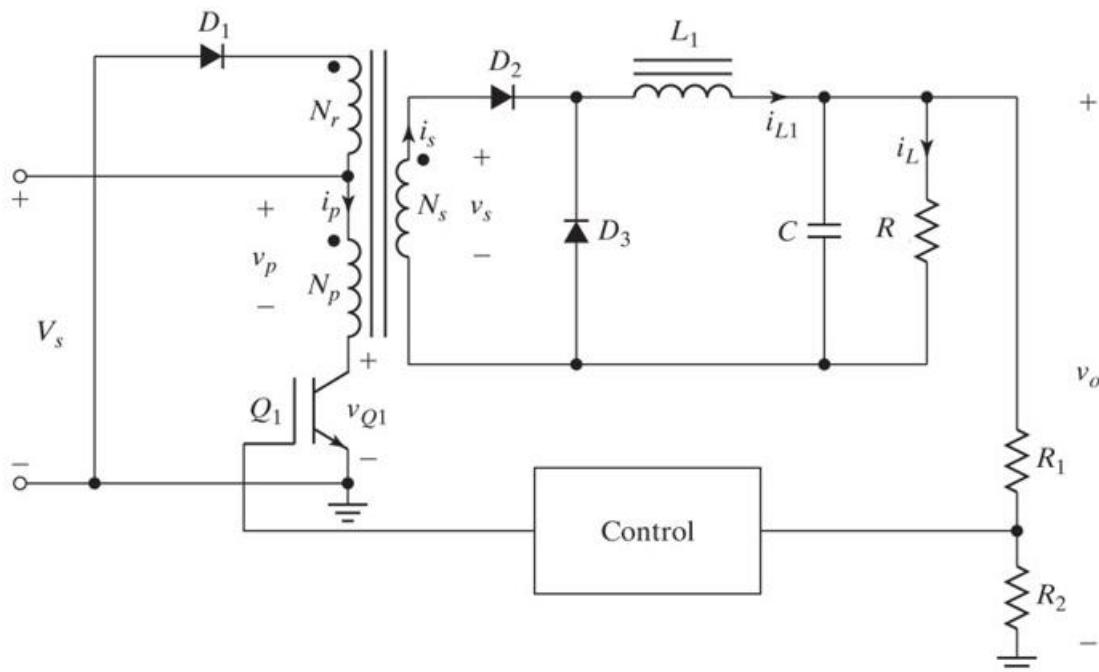


Figure Q 5 (b)

*Rajah Q 5 (b)*

- (i) Sketch waveforms of primary voltage  $V_p$ , transistor Q1 voltage  $V_{Q1}$ , primary current  $I_p$ , current of diode D3  $I_{D3}$ , current of Inductor  $I_L$  and output voltage  $V_o$ .

*Lakarkan bentuk gelombang voltan premium  $V_p$ , voltan transistor Q1  $V_{Q1}$ , arus premier  $I_p$ , arus diode D3  $I_{D3}$ , arus arahan  $I_L$  dan voltan keluaran  $V_o$ .*

(30 marks/markah)

- (ii) Explain briefly the differences between Flyback and forward converter.

*Jelaskan secara ringkas perbezaan antara penukar Flyback dan penukar hadapan.*

(10 marks/markah)

oooOooo

**APPENDIX****LAMPIRAN**

**Course Outcomes (CO) – Programme Outcomes (PO) Mapping**  
***Pemetaan Hasil Pembelajaran Kursus – Hasil Program***

<b>Questions <i>Soalan</i></b>	<b>CO</b>	<b>PO</b>
1	1	2
2	1	2
3	2	3
4	2	3
5	3	3
6		