



First Semester Examination  
Academic Session 2018/2019

December 2018/January 2019

**EEE505 – Advanced Analog Integrated Circuit Design**

Duration : 3 hours

---

Please check that this examination paper consists of SIX (6) pages of printed material before you begin the examination.

Instructions : Answer **FIVE (5)** questions. Answer TWO (2) questions in Part A and TWO (2) questions from Part B and ONE (1) question from any section.

Use two-book answers for **Part A** and **Part B**.

All questions carry the same marks

**Part A :**

1. For the circuit shown in Figure 1 below, assume that all transistors are operating in the saturation region. Calculate the following using these parameters:  
 $K'_n = \mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ ,  $V_t = 0.4 \text{ V}$ ,  $\lambda = 0.1 \text{ V}^{-1}$

- a) Output current,  $I_{out}$  (5 marks)  
 b) Minimum output voltage,  $V_{out,min}$  (5 marks)  
 c) Output resistance,  $R_{out}$  (10 marks)

Note: For part (a) and (b) the  $\lambda$  effect can be neglected. BUT you need to use  $\lambda$  for calculating part (c).

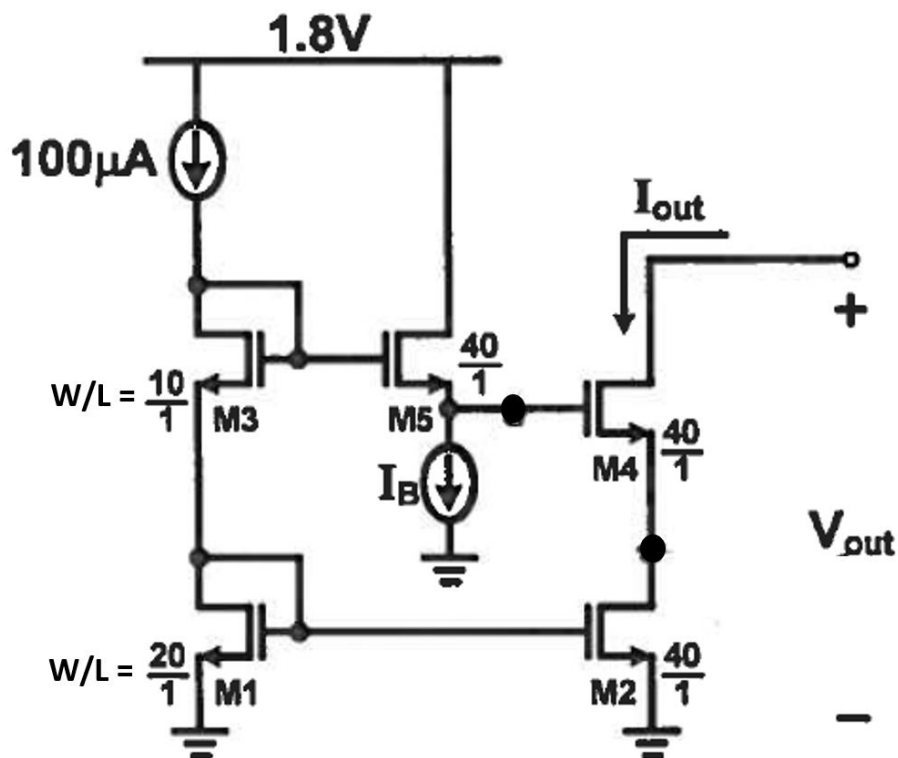


Figure 1.

2. For an active-loaded MOS differential amplifier shown in Figure 2, assume that for all transistors,  $W/L = 7.2 \mu\text{m}/0.36 \mu\text{m}$ ,  $\mu_n C_{ox} = 387 \mu\text{A}/\text{V}^2$ ,  $\mu_p C_{ox} = 86 \mu\text{A}/\text{V}^2$ ,  $|V'_{An}| = 5 \text{ V}/\mu\text{m}$ ,  $|V'_{Ap}| = 6 \text{ V}/\mu\text{m}$ , the bias current  $I = 0.2 \text{ mA}$  and  $R_{ss} = 25 \text{ k}\Omega$ .
- a) Determine the value of differential-mode gain,  $A_{dm}$ . (Note: you may need to find the overdrive voltage,  $g_m$  and  $r_o$  for each transistor) (15 marks)
- b) Given the common-mode gain,  $A_{cm} = -1/(2 \cdot g_m \cdot R_{ss})$ , determine the CMRR  $(\frac{|A_{dm}|}{|A_{cm}|})$ . (5 marks)

 


Figure 2.

3. Figure 3 refers to a folded cascode operational transconductance amplifier (OTA) with all transistors operate at the overdrive voltage of 0.2 V.

 


Figure 3.

- Find the expression for output resistance,  $R_o$ . (5 marks)
- Find the expression for  $A_v$ . (5 marks)
- Find the expression for peak-to-peak output voltage swing. (10 marks)

**Part B :**

4. (a) Figure 4 depicts the switched capacitor resistor circuit. By referring to the figure:
- (i) Derive the input equivalent resistance of the circuit in Figure 4. (7 marks)
  - (ii) Calculate the equivalent resistance if the clock frequency is 0.5 MHz and  $C$  is 2 pF. (3 marks)
  - (iii) What is the operation of MOSFET whereby the behaviour of  $V_{GS}$  is similar as  $V_{BE}$  of bandgap device? Together with switched capacitor resistor, design a PTAT current generator. The final equation must be included together with the design. (10 marks)

 


Figure 4

5. (a) Design DAC schematic and derive out the mathematical model equation. The model is based on current steering-resistor string approach. Draw the schematic of the DAC. Explain the functions of all the components in the schematic. (12 marks)
- (b) Extend the model up to 8-bit. Explain your model. (8 marks)
6. (a) Figure 6 shows the biasing circuitries for a typical current steering DAC.
- (i) Explain the function of the operational amplifier. (2 marks)
- (ii) What is the value of resistance  $R$ , if  $I$  is 1 mA and  $V_{REF} = 1.2$  V? (2 marks)
- (iii) Assuming  $V_{DD} = 3.6$  V and M1 is in saturation,  $W/L = 24/2$ ,  $V_{tp} = -1$ ,  $K_p = 40 \mu A/V^2$ , calculate the required  $V_{SG}$ . (6 marks)
- (b) Draw the basic 8-bit DAC which must include the biasing circuitries and the DAC resistor string. (10 pts)

 


Figure 6