

SULIT



Second Semester Examination
2018/2019 Academic Session

June 2019

EEE270 – Analog Circuit II
(Litar Analog II)

Duration : 3 hours
(Masa : 3 jam)

Please check that this examination paper consists of EIGHT (8) pages and ONE (1) appendix before you begin the examination.

[*Sila pastikan bahawa kertas peperiksaan ini mengandungi LAPAN (8) muka surat dan SATU (1) lampiran yang bercetak sebelum anda memulakan peperiksaan ini.*]

Instructions : This paper consists of **FIVE (5)** questions. Answer **ALL** questions. All questions carry the same marks.

Arahan : *Kertas ini mengandungi LIMA (5) soalan. Jawab SEMUA soalan. Semua soalan membawa jumlah markah yang sama.]*

In the event of any discrepancies, the English version shall be used.

[*Sekiranya terdapat sebarang percanggahan pada soalan peperiksaan, versi Bahasa Inggeris hendaklah digunakan.*]

-2-

1. Design a differential amplifier as shown in Figure 1. The gain, A_{DM} for the amplifier should be around 20 dB and differential-mode output resistance, R_{od} of 10 k Ω . Given value for $V_{DD} = V_{SS} = 5$ V. Assume $V_{TN} = 1$ V and $K_n = 25$ mA/V². Use a correct estimation (rule-of-thumb) to check feasibility of your design before starting with design calculation of the circuit. Then, find:

Reka bentuk satu litar penguat kebezaan seperti ditunjukkan oleh Rajah 1. Nilai gandaan, A_{DM} bagi litar penguat harus dalam lingkungan 20 dB dan rintangan keluaran mod-kebezaan, R_{od} adalah bernilai 10 k Ω . Nilai diberikan ialah $V_{DD} = V_{SS} = 5$ V. Anggap $V_{TN} = 1$ V and $K_n = 25$ mA/V². Gunakan anggaran yang betul (rule-of-thumb) sebelum memulakan proses pengiraan bagi reka bentuk litar tersebut. Kemudian, dapatkan:

- (a) Sketch the small signal models for differential-mode and common-mode of this circuit.

Lakarkan model isyarat kecil mod-kebezaan dan mod-sepunya bagi litar ini.

(20 marks/markah)

- (b) Transconductance, g_m

Transkonduktan, g_m

(20 marks/markah)

- (c) Resistance, R_D and R_{SS}

Rintangan R_D and R_{SS}

(30 marks/markah)

- (d) Current, I_D

Arus, I_D

(20 marks/markah)

- (e) Estimation value of CMRR for this circuit

Anggaran nilai CMRR bagi litar ini

(10 marks/markah)

-3-

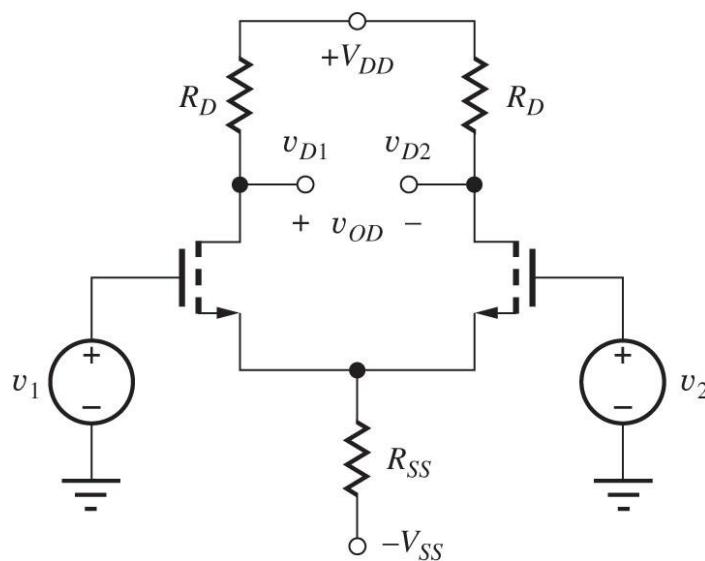


Figure 1

Rajah 1

2. Analyze the circuit of Figure 2. Given values are: $V_{CC} = V_{EE} = 5 \text{ V}$, $I_1 = 200 \mu\text{A}$, $I_2 = 500 \mu\text{A}$, $I_3 = 2 \text{ mA}$, $R_L = 2 \text{ k}\Omega$, $R_1 = 2 \text{ M}\Omega$. Assume $V_A = 70 \text{ V}$, $V_{TN} = 0.7 \text{ V}$, $K_n = 5 \text{ mA/V}^2$ and $\beta_o = 100$. Based on the given values, find:

Analisa litar Rajah 2. Nilai-nilai yang diberikan adalah: $V_{CC} = V_{EE} = 5 \text{ V}$, $I_1 = 200 \mu\text{A}$, $I_2 = 500 \mu\text{A}$, $I_3 = 2 \text{ mA}$, $R_L = 2 \text{ k}\Omega$, $R_1 = 2 \text{ M}\Omega$. Anggap $V_A = 70 \text{ V}$, $V_{TN} = 0.7 \text{ V}$, $K_n = 5 \text{ mA/V}^2$ dan $\beta_o = 100$. Berdasarkan nilai-nilai tersebut, dapatkan:

- (a) Q-points values

Nilai-nilai titik-Q

(30 marks/markah)

- (b) Differential mode voltage gain, A_{dm}

Gandaan voltage mod kebezaan, A_{dm}

(40 marks/markah)

- (c) CMRR

CMRR

(10 marks/markah)

- (d) Input resistances, R_{id} and R_{out}

Rintangan masukan, R_{id} dan R_{out}

(20 marks/markah)

...4/-

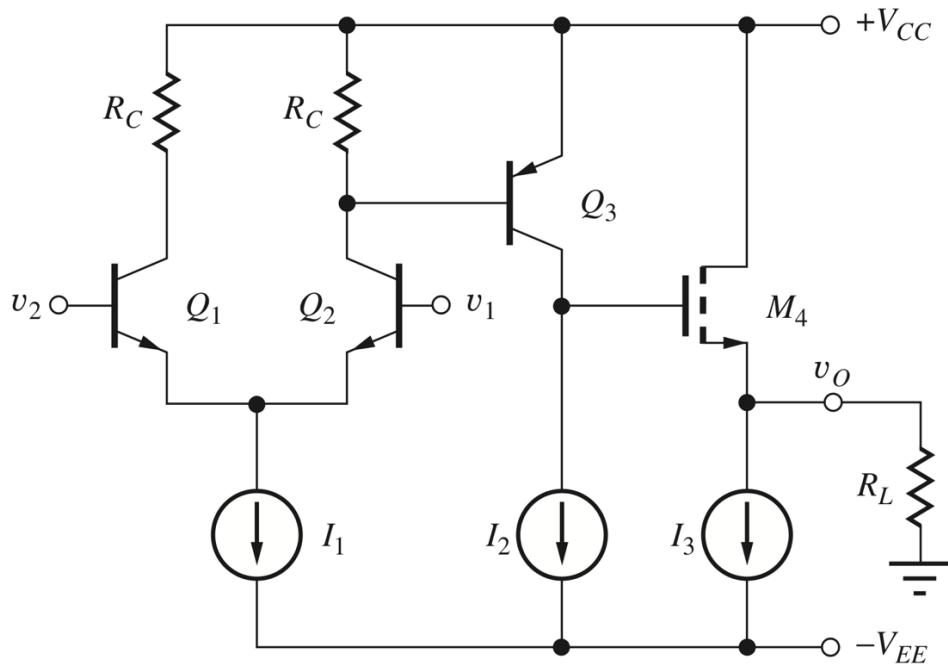


Figure 2

Rajah 2

3. (a) Calculate the current, I_d in the circuit of Figure 3 (a). Given values are:
 $V_{TN} = 0.75$ V, $V_{TP} = -0.75$ V, $K_n = 400 \mu\text{A/V}^2$, $K_p = 200 \mu\text{A/V}^2$, $I_G = 500 \mu\text{A}$ and $R_G = 4 \text{k}\Omega$.

*Kirakan arus, I_d bagi litar Rajah 3 (a). Nilai-nilai yang diberikan adalah:
 $V_{TN} = 0.75$ V, $V_{TP} = -0.75$ V, $K_n = 400 \mu\text{A/V}^2$, $K_p = 200 \mu\text{A/V}^2$, $I_G = 500 \mu\text{A}$ dan $R_G = 4 \text{k}\Omega$.*

(20 marks/markah)

-5-

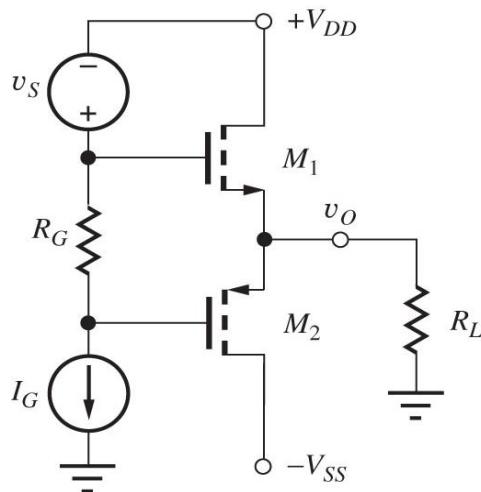


Figure 3 (a)

Rajah 3 (a)

- (b) Calculate the output current and output resistance, I_o and R_{out} in the circuit of Figure 3 (b). Given values are:

$V_o = V_{DD} = 12 \text{ V}$, $R_3 = 330 \text{ k}\Omega$, $R_4 = 680 \text{ k}\Omega$, $R_S = 3 \text{ k}\Omega$, $K_n = 500 \mu\text{A/V}^2$, $V_{TN} = 0.7 \text{ V}$ and $\lambda = 0.01 \text{ V}^{-1}$.

Kirakan arus keluaran dan rintangan keluaran I_o dan R_{out} bagi litar Rajah 3 (b). Nilai parameter diberikan adalah:

$V_o = V_{DD} = 12 \text{ V}$, $R_3 = 330 \text{ k}\Omega$, $R_4 = 680 \text{ k}\Omega$, $R_S = 3 \text{ k}\Omega$, $K_n = 500 \mu\text{A/V}^2$, $V_{TN} = 0.7 \text{ V}$ and $\lambda = 0.01 \text{ V}^{-1}$.

(40 marks/markah)

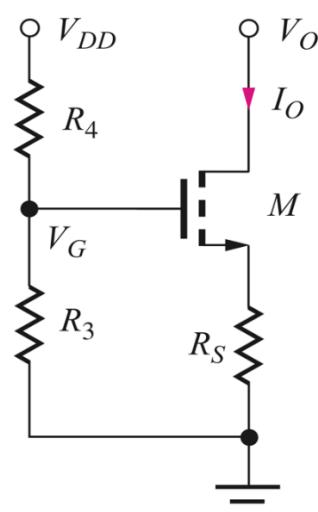


Figure 3 (b)

Rajah 3 (b)

...6/-

-6-

- (c) Derive G_m based on the Figure 3 (c).

Berdasarkan Rajah 3 (c), terbitkan G_m .

(40 marks/markah)

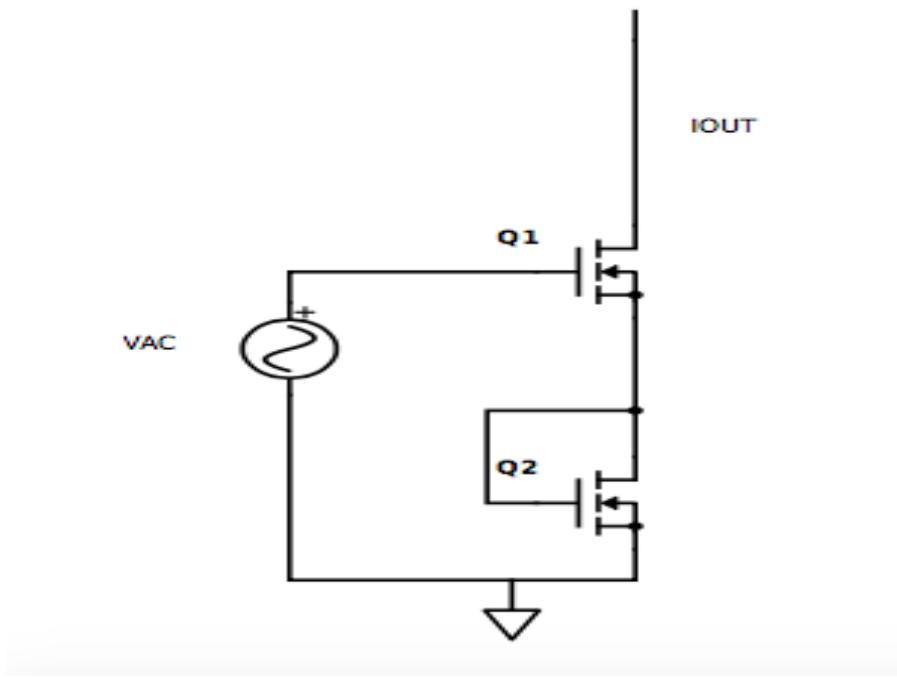


Figure 3(c)

Rajah 3(c)

4. For the circuit in Figure 4:

Bagi litar dalam Rajah 4:

- (a) Derive Miller C_C for dominant pole expression.

Hasilkan persamaan Miller C_C bagi kutub dominan.

(50 marks/markah)

- (b) Derive the expression of gain bandwidth.

Hasilkan persamaan gandaan jalur lebar.

(50 marks/markah)

-7-

Figure 4

Rajah 4

...8/

-8-

5. Figure 5 shows the folded cascode. If I_{REF} is 200 mA, lamda = 0.1:

Rajah 5 menunjukkan litar kaskod terlipat. Jika I_{REF} adalah 200 mA, lamda = 0.1:

- (a) Find the DC gain

Dapatkan gandaan DC

(80 marks/markah)

- (b) If CL at the out node is 1 pF, how much is the dominant frequency?

Jika CL di nod keluaran adalah 1 pF, berapakah frekuensi dominan?

(20 marks/markah)

Figure 5

Rajah 5

-oooOooo-

SULIT

APPENDIX A**LAMPIRAN A**

Course Outcomes (CO) – Programme Outcomes (PO) Mapping
Pemetaan Hasil Pembelajaran Kursus – Hasil Program

Questions Soalan	CO	PO
1	4	2
2	3	2
3	3	2
4	3	2
5	3	2