



Second Semester Examination
2018/2019 Academic Session

June 2019

EEE505 – Advanced Analog Integrated Circuit Design

Duration : 3 hours

Please check that this examination paper consists of SIX (6) pages and ONE (1) pages of printed appendix material before you begin the examination.

Instructions: This question paper consists of **SIX (6)** questions. Answer FIVE (5) questions. All questions carry the same marks.

Part A:

1. Investigate the cascode configuration of multi-transistor M_1 (common-source) and M_2 (common-gate) as shown in Figure 1 below.
 Given $I_{D1} = I_{D2} = 250 \mu\text{A}$, $W/L = 100$, $\lambda = 0.1 \text{ V}^{-1}$, $K'_n = \mu_n C_{ox} = 90 \mu\text{A/V}^2$, $V_t = 0.7 \text{ V}$
- (a) Derive the expression for output resistance, R_o . (10 marks)
- (b) Determine the values for small-signal parameters;
- (i) Transconductance, $G_M (\approx g_m)$. (4 marks)
- (ii) Output resistance, R_o . (4 marks)
- (iii) Open-circuit voltage gain, A_v . (2 marks)

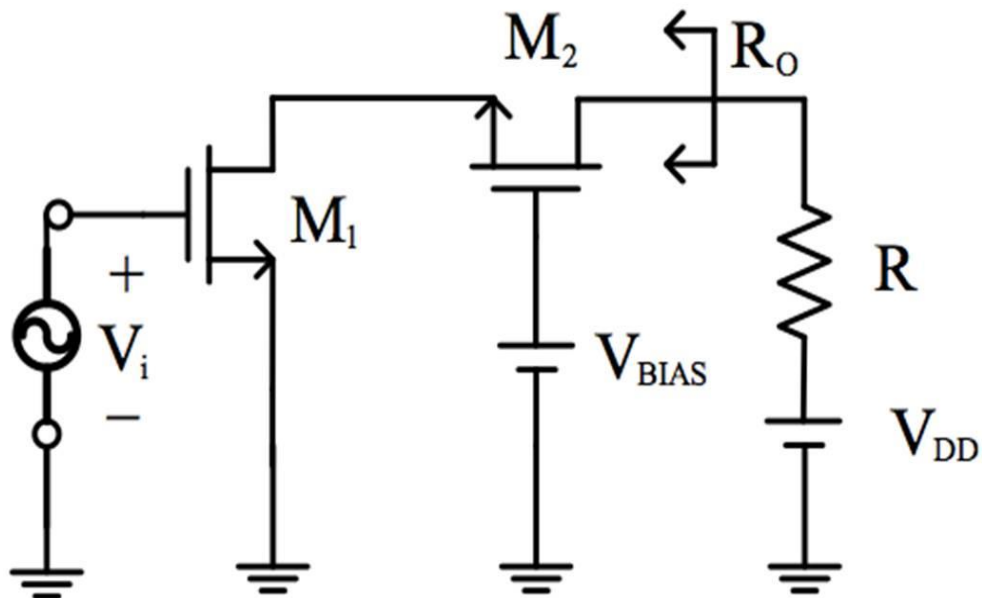


Figure 1.

2. For an active-loaded MOS differential amplifier shown in Figure 2, assume that for all transistors, $W/L = 7.2 \mu\text{m}/0.36 \mu\text{m}$, $\mu_n C_{ox} = 387 \mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 86 \mu\text{A}/\text{V}^2$, $|V'_{An}| = 5 \text{ V}/\mu\text{m}$, $|V'_{Ap}| = 6 \text{ V}/\mu\text{m}$, the bias current $I_{TAIL} = 0.2 \text{ mA}$ and $R_{ss} = 25 \text{ k}\Omega$.

- (a) Determine the value of differential-mode gain, A_{dm} .
(Note: No derivation needed)

(15 marks)

- (b) Given the common-mode gain, $A_{cm} = -1/(2.g_m.R_{ss})$, determine the CMRR.

(5 marks)

 


Figure 2.

3. Figure 3 refers to a current source design with all transistors are assumed to be operating in saturation region and both body-effect and channel-length modulation can be neglected.

- (a) Derive the expression for open-circuit voltage gain, A_v .

(5 marks)

...4/-

- (b) Derive the expression for output resistance, R_o .

(15 marks)

 


Figure 3

Part B:

4. (a) Figure 4 depicts the switched capacitor resistor circuit. By referring to the figure:
- (i) Derive the equivalent resistance between v_1 and v_2 of the circuit in Figure 4. (7 marks)
 - (ii) Calculate the resistance if the clock frequency is 0.5 MHz and C is 2 pF. (3 marks)

...5/-

- (b) What is the operation of MOSFET whereby the behaviour of V_{GS} is similar as V_{BE} of bandgap device? Together with switched capacitor resistor, design a PTAT current generator. The final equation must be included together with the design.

(10 marks)

 


Figure 4

5. (a) State a simplified 3-bit DAC mathematical model. The model is based on current steering-resistor string approach. Draw the schematic of the DAC. Explain the functions of all the components in the schematic. (12 marks)
- (b) Extend the model up to 8-bit. Explain your model. (8 marks)
6. (a) Figure 6 shows the biasing circuitries for a typical current steering DAC.
- (i) Explain the function of the operational amplifier. (2 marks)
- (ii) What is the value of resistance R, if I is 1 mA and $V_{REF} = 1.2$ V? (2 marks)
- (iii) Assuming $V_{DD} = 3.6$ V and M1 is in saturation, $W/L = 24/2$, $V_{tp} = -1$, $K_p = 40 \mu A/V^2$, calculate the required V_{SG} of M1. (6 marks)
- (b) Draw the basic 8-bit DAC which must include the biasing circuitries and the DAC resistor string.

(10 marks)

...6/-

 


Figure 6

-oooOooo-

APPENDIX

APPENDIX A

(b) NMOS Transistor Parameters

Quantity	Formula
Large-Signal Operation	
Drain current (active region)	$I_d = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{gs} - V_t)^2$
Drain current (triode region)	$I_d = \frac{\mu C_{ox}}{2} \frac{W}{L} [2(V_{gs} - V_t)V_{ds} - V_{ds}^2]$
Threshold voltage	$V_t = V_{t0} + \gamma [\sqrt{2\phi_f + V_{sb}} - \sqrt{2\phi_f}]$
Threshold voltage parameter	$\gamma = \frac{1}{C_{ox}} \sqrt{2q\epsilon N_A}$
Oxide capacitance	$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}} = 3.45 \text{ fF}/\mu\text{m}^2 \text{ for } t_{ox} = 100 \text{ \AA}$
Small-Signal Operation (Active Region)	
Top-gate transconductance	$g_m = \mu C_{ox} \frac{W}{L} (V_{GS} - V_t) = \sqrt{2I_D \mu C_{ox} \frac{W}{L}}$
Transconductance-to-current ratio	$\frac{g_m}{I_D} = \frac{2}{V_{GS} - V_t}$
Body-effect transconductance	$g_{mb} = \frac{\gamma}{2\sqrt{2\phi_f + V_{SB}}} g_m = \chi g_m$
Channel-length modulation parameter	$\lambda = \frac{1}{V_A} = \frac{1}{L_{eff}} \frac{dX_d}{dV_{DS}}$
Output resistance	$r_o = \frac{1}{\lambda I_D} = \frac{L_{eff}}{I_D} \left(\frac{dX_d}{dV_{DS}} \right)^{-1}$
Effective channel length	$L_{eff} = L_{drwn} - \frac{2L_d - X_d}{2}$
Maximum gain	$g_m r_o = \frac{1}{\lambda} \frac{2V_A}{V_{GS} - V_t} = \frac{2V_A}{V_{GS} - V_t}$
Source-body depletion capacitance	$C_{sb} = \frac{C_{sb0}}{\left(1 + \frac{V_{SB}}{\psi_0}\right)^{0.5}}$
Drain-body depletion capacitance	$C_{db} = \frac{C_{db0}}{\left(1 + \frac{V_{DB}}{\psi_0}\right)^{0.5}}$
Gate-source capacitance	$C_{gs} = \frac{2}{3} W L C_{ox}$
Transition frequency	$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd} + C_{gb})}$