

UNIVERSITI SAINS MALAYSIA

Second Semester Examination  
Academic Session 2006/2007

April 2007

**ZCT 106/3 - Electronic I**  
*[Elektronik II]*

Duration: 3 hours  
*[Masa : 3 jam]*

---

Please ensure that this examination paper contains **FIVE** printed pages before you begin the examination.

*[Sila pastikan bahawa kertas peperiksaan ini mengandungi **LIMA** muka surat yang bercetak sebelum anda memulakan peperiksaan ini.]*

**Instruction:** Answer all **FIVE** questions. Students are allowed to answer all questions in Bahasa Malaysia or in English.

**Arahan:** Jawab kesemua **LIMA** soalan. Pelajar dibenarkan menjawab semua soalan sama ada dalam Bahasa Malaysia atau Bahasa Inggeris.]

1. (a) (i) State Thevenin's Theorem.  
*[Nyatakan Teorem Thevenin.]*

(10/100)

- (ii) State Nortons's Theorem.  
*[Nyatakan Teorem Norton.]*

(10/100)

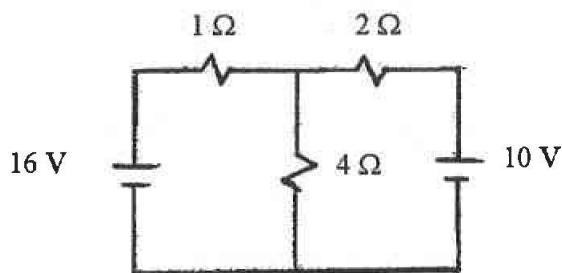


Figure 1(a)  
*[Gambarajah 1(a)]*

- (iii) In the circuit of Fig. 1(a), calculate the current flowing in the  $4\ \Omega$  resistor by using Thevenin's Theorem.

*[Dalam litar Rajah 1(a), hitungkan arus yang melalui perintang  $4\ \Omega$  dengan menggunakan Teorem Thevenin.]*

(40/100)

(b)

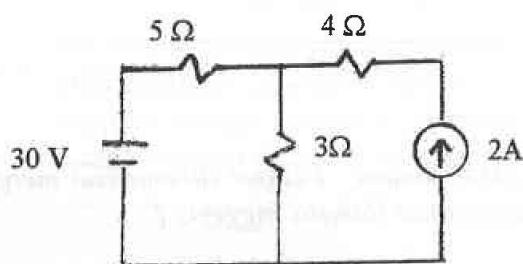


Figure 1 (b)  
*[Gambarajah 1(b)]*

- In circuit of Fig 1(b), calculate the voltage across the  $3\ \Omega$  resistor by using the Superposition Theorem.

*[Dalam litar bagi Rajah 1(b), hitungkan voltan yang melalui perintang  $3\ \Omega$  dengan menggunakan Teorem Superposisi.]*

(40/100)

2. (a) Describe the basic principle of the use of a diode and a capacitor as a clamping circuit. Sketch the circuit.

[Huraikan prinsip asas bagi penggunaan suatu diod dan suatu kapasitans sebagai litar pengapit. Lakarkan liter tersebut.]

(30/100)

- (b) Design a clamping circuit which clamps the maximum point of any periodic signal at + 3 V.

[Rekabentuk suatu litar pengapit yang mengapitkan titik maksimum sebarang isyarat berkala + 3 V.]

(30/100)

(c)

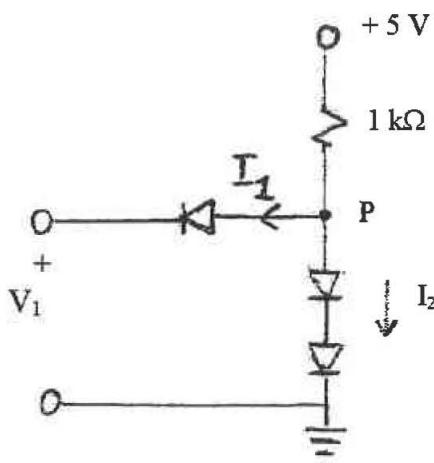


Figure 2(c)  
[Gambarajah 2(c)]

Three silicon diodes are connected as shown in Fig 2(c). Assume that each diode has a threshold voltage  $V_T = 0.7 \text{ V}$  and the ac resistance  $r_D = 0.0 \Omega$ .

[Tiga diod silikon disambung seperti ditunjukkan dalam Rajah 2(c). Anggapkan setiap diod mempunyai voltan ambang  $V_T = 0.7 \text{ V}$  dan rintangan ac  $r_D = 0.0 \Omega$ .]

- (i) Calculate the currents  $I_1$  and  $I_2$  (a) when  $V_1 = 0.69 \text{ V}$  (b) when  $V_1 = 0.7 \text{ V}$  (c) when  $V_1 = 0.71 \text{ V}$ .

[Hitungkan arus  $I_1$  dan  $I_2$  (a) apabila  $V_1 = 0.69 \text{ V}$  (b) apabila  $V_1 = 0.7 \text{ V}$  (c) apabila  $V_1 = 0.71 \text{ V}$ .]

(30/100)

- (iii) What is the important use of this behaviour?

[Apakah penggunaan yang penting bagi sifat ini?]

(10/100)

3. (a) Consider an elementary *npn* transistor amplifier connected in the common-emitter (CE) configuration. The collector battery  $V_{CC} = 15$  V. The biasing circuit is arranged so that the operating point  $Q$  is at  $I_B = 0.1$  mA and  $V_{CE} = 9$  V. The input current is

[Pertimbangkan suatu amplifier *npn* yang disambungkan dalam tatarajah pengeluar sepunya (CE). Bateri penggumpul  $V_{CC} = 15$  V. Litar pemincang adalah disusunkan supaya titik operasi  $Q$  adalah pada  $I_B = 0.1$  mA dan  $V_{CE} = 9$  V. Arus input adalah]

$$i_i = 0.05 \sin(\omega t) \text{ mA}$$

The value of the parameter  $\beta = 40$ .

[Nilai parameter  $\beta = 40$ .]

- (i) Sketch the amplifier circuit.

[Lakarkan litar amplifier.]

(15/100)

- (ii) Determine the dc load line and sketch it.

[Tentukan garis beban dc dan lakarkannya.]

(20/100)

- (iii) Calculate the value of the load resistance  $R_L$  which will give the operating point  $Q$  specified above.

[Hitungkan nilai rintangan beban  $R_L$  yang akan mengakibatkan titik operasi  $Q$  yang dispesifikasikan di atas.]

(20/100)

- (iv) Calculate the current gain.

[Hitungkan gandaan arus.]

(10/100)

- (v) Determine the output voltage.

[Tentukan voltan output.]

(15/100)

- (b) Explain the advantages of using a self-biasing circuit for a common-emitter (CE) *npn* transistor amplifier.

[Terangkan kelebihan litar pemincangan kendiri bagi suatu amplifier transistor *npn* yang dipasangkan pada tatarajah pemancar sepunya.]

(20/100)

4. (a) Sketch the circuits and state the functions of the following applications of op amps ( No need to derive the formulas. ).

[Lakarkan litar-litar dan nyatakan fungsi-fungsi bagi aplikasi op amp yang berikut. (Tak perlu terbitkan formula formula.) ]

- (i) an op amp inverting circuit.

[suatu litar op amp menyongsang.]

(15/100)

- (ii) an op amp summing circuit.

[suatu litar op amp yang menghasil tambah.]

(15/100)

- (iii) an op amp integrating circuit.

[suatu litar op amp yang mengkamir.]

(15/100)

- (iv) an op amp differentiating circuit.

[suatu litar op amp yang membezakan.]

(15/100)

- (b) Describe the basic principles of feedback in amplifier circuits. State the uses of (i) positive feedback (ii) negative feedback.

[Huraikan prinsip utama suap balik dalam litar amplifier. Nyatakan penggunaan (i) suap balik positif (ii) suap balik negatif.]

(40/100)

5. Answer any THREE (3) questions.

[Jawab mana-mana TIGA (3) soalan.]

- (a) Describe briefly the classification of power amplifiers as Class A, Class B and Class C.

[Huraikan secara ringkas pengelasan amplifier kuasa sebagai Kelas A, Kelas B dan Kelas C.]

- (b) Describe the use of an op amp together with a resistor and a capacitor in an active low pass filter circuit.

[Huraikan penggunaan suatu op amp dengan suatu perintang dan suatu kapasitor dalam suatu litar pemuras laluan rendah aktif.]

- (c) Describe the use of a transistor as a switch.

[Huraikan penggunaan suatu transistor sebagai suis.]

- (d) Describe the use of two (2) diodes and a center-tapped transformer as a full-wave rectifier.

[Huraikan penggunaan dua (2) diod dan suatu transformer "center-tapped" sebagai suatu rektifier gelombang sepenuh.]

(100/100)