

SULIT

---



Second Semester Examination  
2022/2023 Academic Session

July/August 2023

**EEE133 – Electronic Devices and Circuits**

Duration : 3 hours

---

Please check that this examination paper consists of **NINE (9)** pages of printed material including appendix before you begin the examination.

**Instructions** : This paper consists of **FOUR (4)** questions. Answer **ALL** questions.

...2/-

SULIT

1. a) Figure 1.1 illustrates the bonding diagram of a doped silicon. Si is silicon atom whereas B is the doped atom. Based on Figure 1.1, answer the followings:

 


Figure 1.1 Bonding diagram of a doped silicon.

- i. Sketch the energy band diagram of the doped silicon.
- ii. Redraw Table 1 and fill in the blanks.

Table 1. Doped silicon parameters

Doped Silicon Parameters	
Impurity type	
Majority carriers	
Minority carriers	
Type of fixed charges	

(20 marks)

- b) A silicon sample is doped with phosphorus with concentration of  $5 \times 10^{14} \text{ cm}^{-3}$ . At room temperature the intrinsic carrier concentration of silicon is  $9.65 \times 10^9 \text{ cm}^{-3}$ , electron and hole mobility,  $\mu_e = 1400 \text{ cm}^2/\text{Vs}$  and  $\mu_h = 450 \text{ cm}^2/\text{Vs}$  respectively. Find the conductivity of the doped material by

...3/-

taking into account both majority and minority carrier contributions. Based on your results, comment on the significance of minority carrier contributions as compared to majority carriers.

(30 marks)

- c) An abrupt silicon P-N junction with doping concentrations of  $N_A = 3.5 \times 10^{16} \text{ cm}^{-3}$  and  $N_D = 4.5 \times 10^{16} \text{ cm}^{-3}$  respectively is biased at  $V = 0.7 \text{ V}$ . Determine the ideal forward current assuming that the N-type region is much smaller than the minority carrier diffusion length with a length of  $l_n = 1 \text{ }\mu\text{m}$  and assuming a "long" P-type region, sufficiently enough for the minority carriers to diffuse in. Use carrier mobility values of  $\mu_e = 1350 \text{ cm}^2/\text{Vs}$  and  $\mu_h = 550 \text{ cm}^2/\text{Vs}$  for electron and hole, respectively, in your calculation. The minority carrier lifetime in P-type is given as  $60 \text{ }\mu\text{s}$  and the height of the structure = width of the structure =  $100 \text{ }\mu\text{m}$ . Intrinsic carrier density is  $1 \times 10^{10} \text{ cm}^{-3}$ . Discuss what happens to the forward current when the voltage is increased even further under same temperature environment. Will the saturation current change?

(50 marks)

2. a) Assuming that the diodes are identical, determine  $I$ ,  $I_{D1}$ ,  $I_{D2}$  and  $V_{out}$  in Figure 2.1 under the following conditions:

- i. The diodes are assumed to be ideal;
- ii. The potential barrier,  $V_0$  of the diodes are considered (where  $V_0 = 0.7 \text{ V}$ );
- iii. The potential barrier,  $V_0$  and the internal resistance,  $r_d$  of the diodes are considered (where  $V_0 = 0.7 \text{ V}$  and  $r_d = 10 \text{ }\Omega$ ).

(60 marks)

...4/-

 


Figure 2.1

- b) Figure 2.2 shows the full wave voltage rectification from the output of the transformer using bridge configuration. Assuming that the diodes are identical and they all have a potential barrier,  $V_o = 0.7\text{ V}$ , determine:

 


Figure 2.2

- i. The value of turns, n required to give a voltage of amplitude 5 V at V<sub>2</sub> (n should be rounded to an integer).
- ii. The peak voltage at the output, V<sub>out</sub> for V<sub>2</sub> = 5 V.
- iii. The peak current flowing through any of the diodes.

(25 marks)

- c) By referring to Figure 2.3, state;

...5/-

- i. The name of the circuit;
- ii. The function of the circuit;
- iii. The main application of the circuit.

 


Figure 2.3

(15 marks)

3. Figure 3.1 shows the npn transistor circuit with  $\beta = 100$ . Given  $V_{CC} = 10\text{ V}$ ,  $R_C = 2\text{ k}\Omega$ ,  $V_{BE} = 0.7\text{ V}$ ,  $V_{BE(\text{sat})} = 0.8\text{ V}$ , and  $V_{CE(\text{sat})} = 0.2\text{ V}$ ,

 


Figure 3.1

...6/-

-6-

- a) Determine the region of operation (i.e., active or saturation) and the values of  $I_B$ ,  $I_C$ , and  $V_{CE}$  for:
- $R_B = 500 \text{ k}\Omega$   
(25 marks)
  - $R_B = 120 \text{ k}\Omega$   
(30 marks)
- b) Consider the circuit of Figure 3.1 with  $R_B = 500 \text{ k}\Omega$ , sketch the DC load line and determine its operating point ( $Q$ -point). Then, calculate the new operating point if  $\beta$  is changed to 150.  
(25 marks)
- c) You are to bias an NPN transistor to function as an amplifier. The requirement is for the the NPN to be maintained or stable in the forward active region throughout its operation. Sketch and label the circuit of the two biasing techniques that you know which can fulfill this application.  
(20 marks)
4. a) Compare and list four differences between BJT and FET.  
(20 marks)
- b) An N-channel JFET fixed-bias amplifier circuit as shown in Figure 4.1 has a voltage supply  $V_{GG} = 2 \text{ V}$  and  $V_{DD} = 10 \text{ V}$ . Given  $R_D = 1 \text{ k}\Omega$ ,  $R_G = 1 \text{ M}\Omega$ ,  $I_{DSS} = 8 \text{ mA}$  and  $V_{GS(off)} = -5 \text{ V}$ , determine the values of  $I_D$  and  $V_{DS}$ .  
(30 marks)
- c) Calculate the values of  $V_{GS}$ ,  $K$ ,  $I_{D1}$ , and  $V_{DS}$  for the E-MOSFET circuit shown in Figure 4.2. Given that  $I_{D(on)} = 3 \text{ mA}$ ,  $V_{GS} = 4 \text{ V}$ ,  $V_{GS(th)} = 2 \text{ V}$ , and  $V_{DD} = 10 \text{ V}$ .  
(50 marks)

...7/-

 


Figure 4.1

 


Figure 4.2

-oooOooo-

## APPENDIX I

Electronic charge,  $q = 1.6 \times 10^{-19} \text{C}$

Room temperature,  $27^\circ\text{C} = 300\text{K}$

Thermal voltage,  $V_T = \frac{kT}{q} \approx 26\text{mV}$

Carrier velocity,  $u = \mu E$

Conductivity of material,  $\sigma = nq\mu_e + pq\mu_h$

Current density,  $J = (nq\mu_e + pq\mu_h)E$

\*Hole current in n-type semiconductor,  $I_{pn} = \frac{AqD_p p_n}{L_p} \left( e^{\frac{V}{V_T}} - 1 \right)$

\*Electron current in p-type semiconductor,  $I_{np} = \frac{AqD_n n_p}{L_n} \left( e^{\frac{V}{V_T}} - 1 \right)$

Diode current,  $I = I_S \left( e^{\frac{V}{V_T}} - 1 \right)$

\*Note: the expressions are for the assumption that the minority carrier diffusion length is shorter than the length of the substrate.



APPENDIX II

<b>Question</b>	<b>Course Outcome (CO)</b>	<b>Programme Outcome (PO)</b>
1	1	PO1
2	2	PO2
3	3	PO1
4	4	PO2