

SULIT



Second Semester Examination
2022/2023 Academic Session

July / August 2023

EEE270 – Analogue Electronics II

Duration : 3 hours

Please check that this examination paper consists of **EIGHT (8)** pages of printed material including appendix before you begin the examination.

Instructions : This paper consists of **FIVE (5)** questions. Answer **ALL** questions. All questions carry the same marks.

...2/-

SULIT

-2-

1. Design a differential amplifier as shown in Figure 1. The gain, A_{DM} for the amplifier should be around 26 dB, and differential-mode output resistance, R_{od} of 20 k Ω . Given a value for $V_{DD} = V_{SS} = 10$ V. Assume $V_{TN} = 1$ V and $K_n = 25$ mA/V². Then, find:

- Transconductance, g_m (20 marks)
- Resistance, R_D and R_{SS} (45 marks)
- Current, I_D (20 marks)
- Estimation value of CMRR (dB) for this circuit (15 marks)

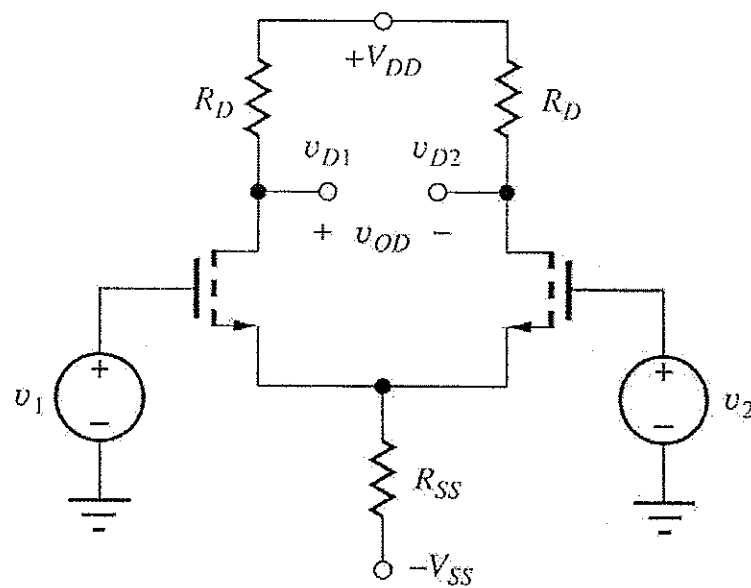


Figure 1

...3/-

-3-

2. Analyze the circuit in Figure 2 below. Given values are: $V_{DD} = V_{SS} = 10\text{ V}$, $I_1 = 750\ \mu\text{A}$, $I_2 = 2\ \text{mA}$, $I_3 = 5\ \text{mA}$. Assume $V_{TN} = 0.7\ \text{V}$, $\lambda_n = 0.02\ \text{V}^{-1}$, $K_n = 5\ \text{mA/V}^2$, $V_{TP} = -0.7\ \text{V}$, $\lambda_p = 0.015\ \text{V}^{-1}$, $K_p = 2\ \text{mA/V}^2$, $R_L = 2\ \text{k}\Omega$. Based on the given values, find:

- Q-points (30 marks)
- Differential mode voltage gain, A_{dm} (50 marks)
- Output resistance, R_{out} (10 marks)
- CMRR (resistance of current source I_1 , $R_1 = 1.5\ \text{M}\Omega$) (10 marks)

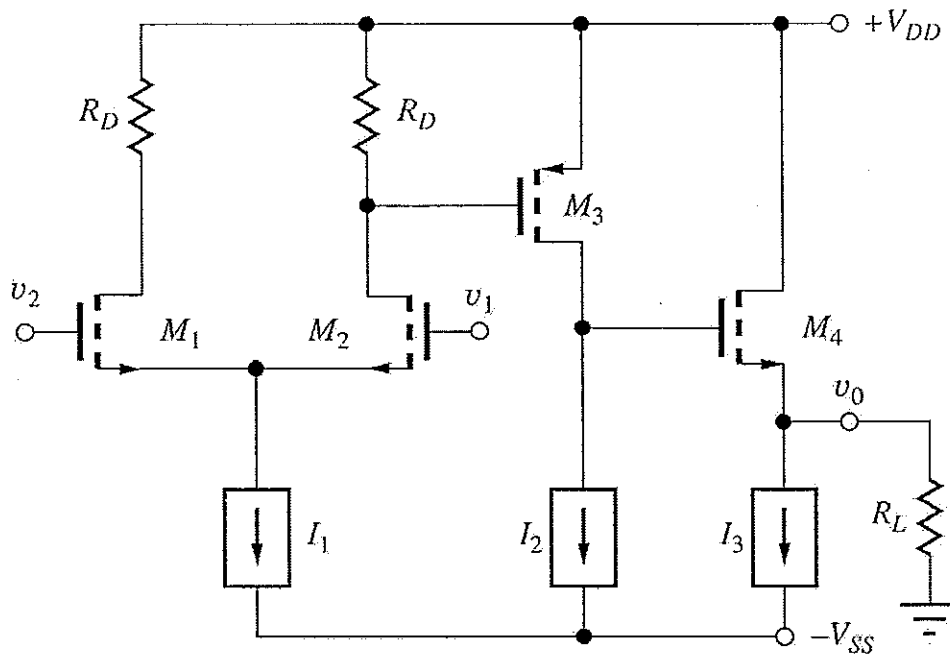


Figure 2

...4/-

3. a) Find the output current, I_o and output resistance, R_{out} of the current source in Figure 3 (a) if $V_{CC} = 12\text{ V}$, $R_1 = 100\text{ k}\Omega$, $R_2 = 200\text{ k}\Omega$, $R_E = 47\text{ k}\Omega$, $\beta_o = 75$, and Early Voltage, $V_A = 50\text{ V}$.

(50 marks)

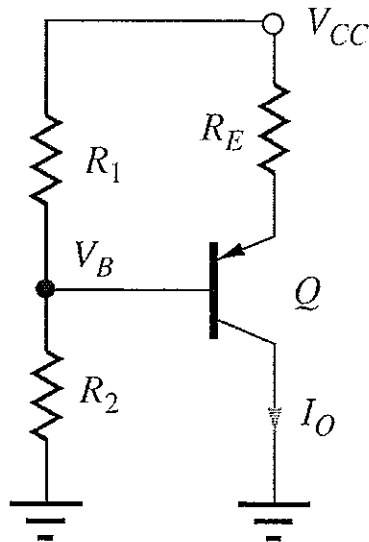


Figure 3 (a)

- b) An amplifier with a dc gain of 60 dB has a single pole, high-frequency response with a 3-dB frequency of 100 kHz.
- Give an expression for the gain function $A_v(s)$ (5 marks)
 - Sketch Bode diagrams for the gain magnitude (10 marks)
 - What is the gain-bandwidth product? (5 marks)

...5/-

- c) Find the midband gain, poles and zeros, and cut-off frequency for $A_H(s)$ transfer function below.

(30 marks)

$$A_H(s) = 50 \frac{\left(1 + \frac{s}{10^9}\right)}{\left(1 + \frac{s}{10^6}\right) \left(1 + \frac{s}{10^8}\right)}$$

4. a) For the common-source amplifier in Figure 4, draw,

- i. ac small-signal circuit, and
- ii. circuits for determining the time constant of each C_1 , C_2 and C_3 .

(44 marks)

- b) Find the short circuit time constants for the amplifier.

(24 marks)

- c) What is the lowest cut-off frequency of the amplifier if $I_D = 1.5$ mA and $V_{GS} - V_T = 0.5$ V. Assume $\lambda = 0.015/V$.

(32 marks)

...6/-

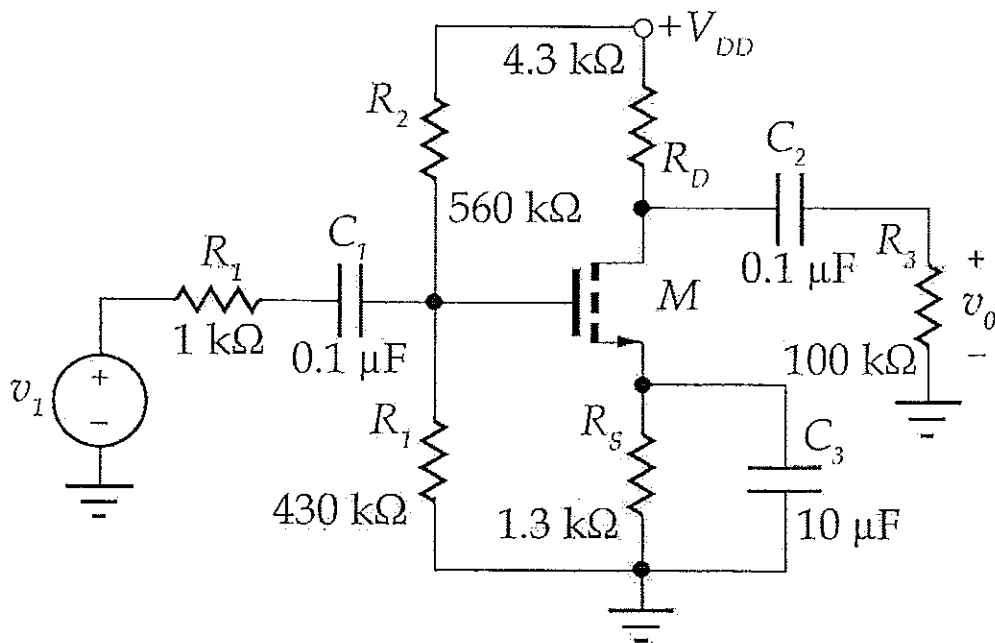


Figure 4

5. a)

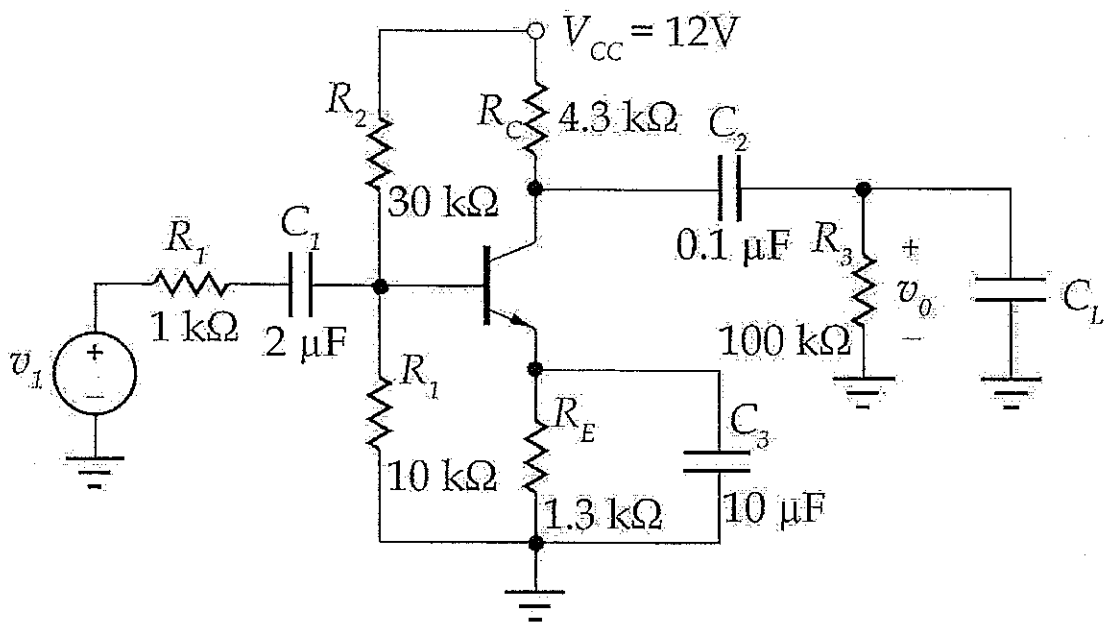


Figure 5 (a)

- i. Find the midband gain and upper-cutoff frequency of the common-emitter amplifier shown in Figure 5 (a). Assuming $\beta_0 = 100$, $f_T = 500$ MHz, $C_{\mu} = 0.5$ pF, $r_x = 250$ Ω , $g_m = 64.0$ mS and a Q-point of 1.60, 3.00 V.

(30 marks)

- ii. Find additional poles and zeros of the common-emitter amplifier. Assume $C_L = 0$, $C_1 = C_3 = 3.9$ μ F, $C_2 = 0.082$ μ F.

(20 marks)

- b) Figure 5 (b) shows an ideal voltage amplifier having a gain of -100 V/V with an impedance Z connected between its output and input terminals. Find the Miller equivalent circuit when Z is a 1 M Ω resistance. And use the equivalent circuit to determine V_0 / V_{sig} .

(50 marks)

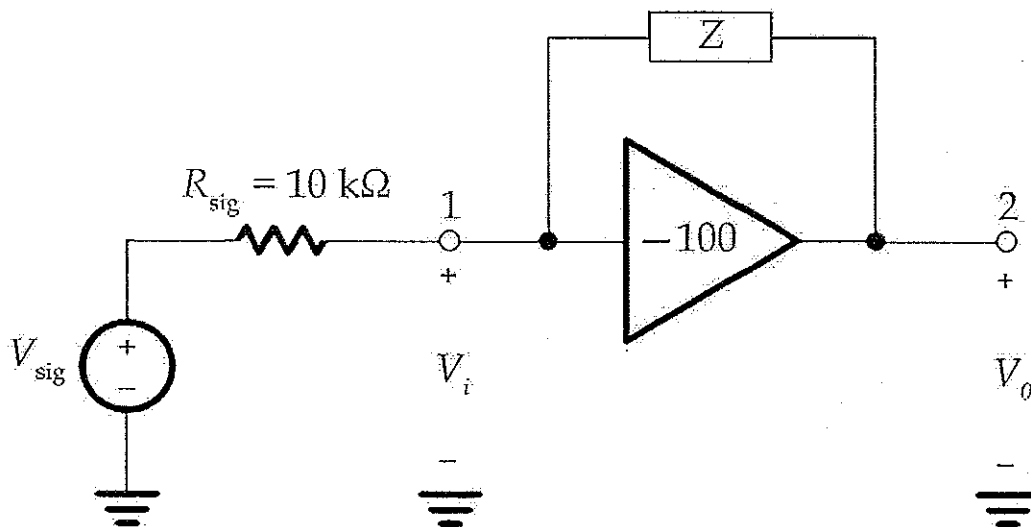


Figure 5 (b)

-oooOooo-

...8/-

APPENDIX

Question	Course Outcome (CO)	Programme Outcome (PO)
1	1	2
2	1	2
3	1	2
4	1	2
5	1	2