



Second Semester Examination  
2022/2023 Academic Session

July/August 2023

**EEK372 –POWER SYSTEM ANALYSIS**

**Duration: 3 hours**

---

Please ensure that this examination paper consists of SIX (6) pages including appendix material before you begin the examination.

**Instructions:** This question paper consists of **FOUR (4)** questions. Answer **ALL** questions. All questions carry the same marks.

1. (a) The single-line diagram of a three-phase power system is shown in Figure 1. The length of transmission line has is 64 km with series reactance of 0.5 ohm/km. The ratings of the components are given in Table 1. Using the common base  $S_b = 300$  MVA and  $V_b = 20$  kV at the generator, draw the reactance diagram in per unit.

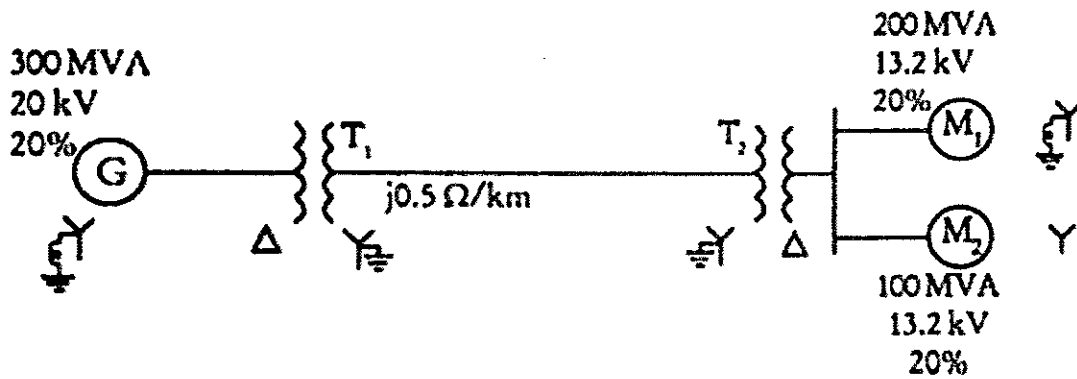


Figure 1

Table 1

Component	Power (S)	Voltage (V)	Reactance X
Generator G	300 MVA	20.0 kV	20%
Transformer T <sub>1</sub>	350 MVA	230/20 kV	10%
Transformer T <sub>2</sub>	300 MVA	220/13.2 kV	10%
Motor M1	200 MVA	13.2 kV	20%
Motor M2	100 MVA	13.2 kV	20%

(55 marks)

- (b) A three-phase line with an impedance of  $(0.2 + j1.0)$  ohm/phase feeds three balanced three-phase loads connected in parallel.  
 Load 1: absorbs a total of 150 kW and 120 kvar  
 Load 2: delta connected with an impedance of  $(150 - j48)$  ohm/phase  
 Load 3: 120 kVA at 0.6 power factor leading  
 If the line-to-neutral voltage at the load end of the line is 2000 V (rms), calculate the magnitude of the line-to-line voltage at the source end of the line.

(45 marks)

...3/-

-3-

2. (a) A three-phase overhead transmission line is designed to deliver 15 MW, power factor 0.8 lagging at 132 kV at its receiving end. The transmission line loss is 5 % of the delivered power. The transmission line has resistance  $0.572 \Omega$  per km. Given the resistivity of the conductor material to be  $2.84 \times 10^{-8}$  ohm-m, determine the length of the line and conductor diameter. Neglect power losses due to insulator leakage currents and corona.
- (35 marks)

- (b) Assuming that there are 4 sub-conductors arranged symmetrically in a circle of radius  $R$ . These sub-conductors are equal in size with a diameter of 6 cm. Determine the radius of the circle,  $R$  if the geometric mean radius of this bundle conductor is 12 cm.
- (25 marks)

- (c) A single-phase transmission line has two conductors, each of 10 mm radius. The distance between them is 1 m. It is then converted to a three-phase transmission line by introducing a third conductor of the same radius. This new conductor is fixed at an equal distance,  $D$  from the two single-phase conductors. The three-phase lines is fully transposed. The inductance per phase of the three-phase system is 5 % more than that of the inductance per conductor of the single-phase system. Calculate the distance,  $D$ . Determine the ratio of the capacitance per phase of the three-phase system to the line-to-neutral capacitance of the single-phase system.
- (40 marks)

...4/-

3. The one-line diagram of a simple three-bus power system and its data are shown in Figure 3 and Table 3. The neutral of each generator is grounded through an impedance of 0.25 per unit on a 100-MVA base. The generators are running on the no-load condition at rated voltage and frequency with their EMF in phase.

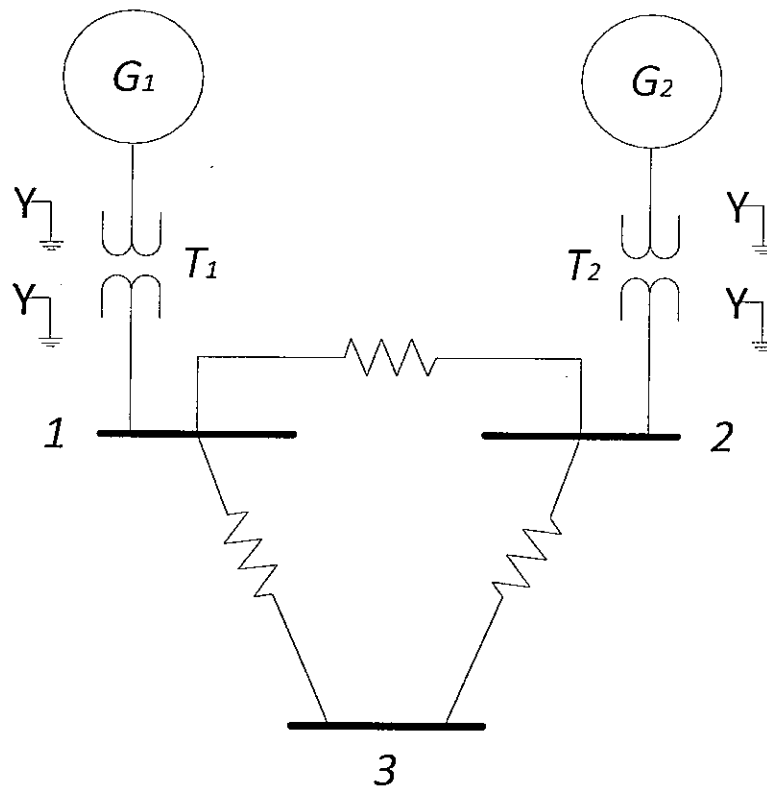


Figure 3: Three-bus power system

Table 3: List of Data

Item	Base MVA	Voltage Rating (kV)	$X^1$	$X^2$	$X^3$
$G_1$	100	20	0.15	0.15	0.05
$G_2$	100	20	0.15	0.15	0.05
$T_1$	100	20/220	0.10	0.10	0.10
$T_2$	100	20/220	0.10	0.10	0.10
$L_{12}$	100	220	0.125	0.125	0.30
$L_{13}$	100	220	0.15	0.15	0.35
$L_{23}$	100	220	0.25	0.25	0.7125

-5-

Determine the followings:

- (a) The positive, negative and zero sequence Thevenin impedance seen from bus 3.

(60 marks)

- (b) Fault current when a single line-to-ground fault occurred at bus 3 with  $Z_f = 0.1j$  per unit.

(40 marks)

4. Based on Question Three (Q3), determine:

- (a) Fault current when a line-to-line fault occur at bus 3 with  $Z_f = 0.1j$  per unit.

(50 marks)

- (b) Fault current when a double line-to-ground fault occur at Bus 3 with  $Z_f = 0.1j$  per unit.

(50 marks)

-oooOooo-

...6/-

APPENDIX A

QUESTION NUMBER	CO	PO
1	1	2
2	1	2
3	3	2
4	3	3