

**SULIT**

---



Second Semester Examination  
2022/2023 Academic Session

July/August 2023

**EEU 104- ELECTRICAL TECHNOLOGY**

Duration : 3 hours

---

Please check that this examination paper consists of **TWELVE (12)** pages of printed material including appendix before you begin the examination.

**Instructions** : This paper consists of **THREE (3)** questions. Answer **ALL** questions.

-2-

1. a) Find the equivalent resistance at terminal a-b for the following network in Figure 1(a) and 1(b):

(i).

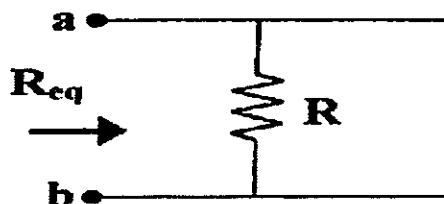


Figure 1(a)

(10 marks)

(ii).

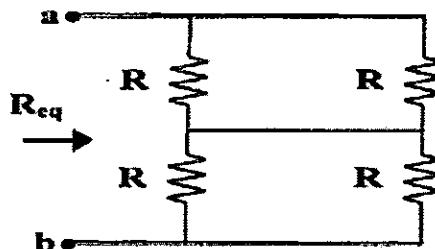


Figure 1(b)

(10 marks)

- b) By using Thevenin Theorem, solve the current,  $i$  in Figure 1(c).

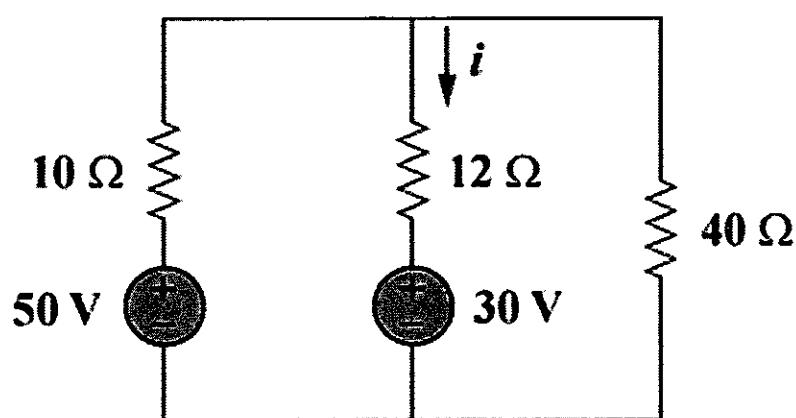


Figure 1(c)

(30 marks)

...3/-

-3-

- c) Find the Norton equivalent circuit for network in Figure 1(d).

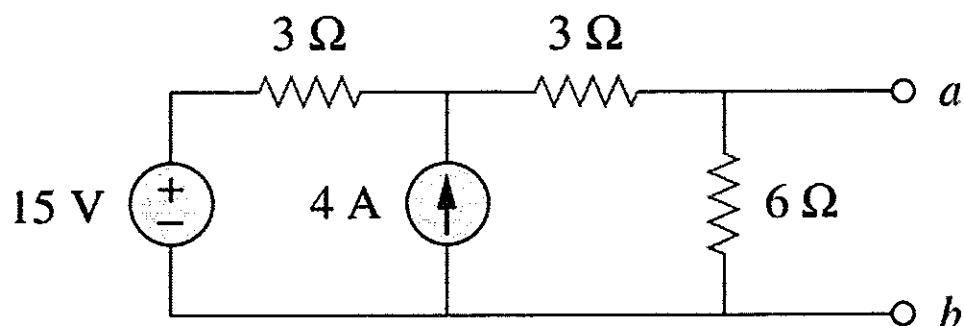


Figure 1(d)

(30 marks)

- d) Use nodal analysis to obtain  $v_o$  in the circuit in Figure 1(e).

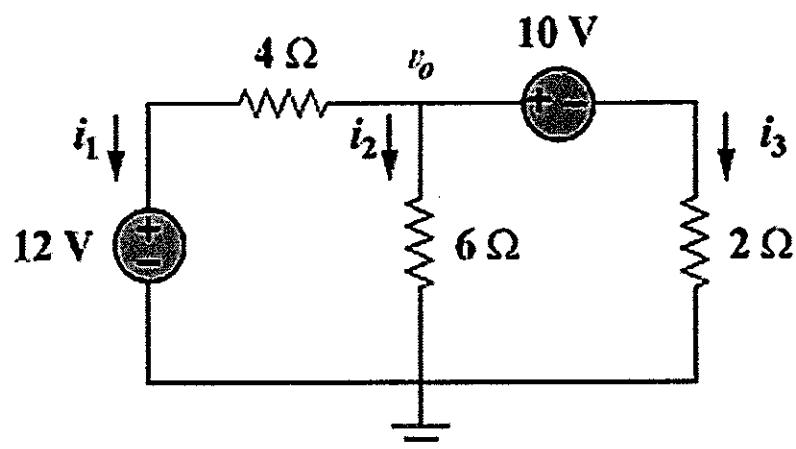


Figure 1(e)

(20 marks)

-4-

2. a) For the circuit in Figure 2(a),  $i(t) = 4(2 - e^{-10t})$  mA. If  $i_2(0) = -1$  mA,

Find:

- (i).  $i_1(0)$
- (ii).  $v_1(t)$  and  $v_2(t)$
- (iii).  $i_1(t)$  and  $i_2(t)$

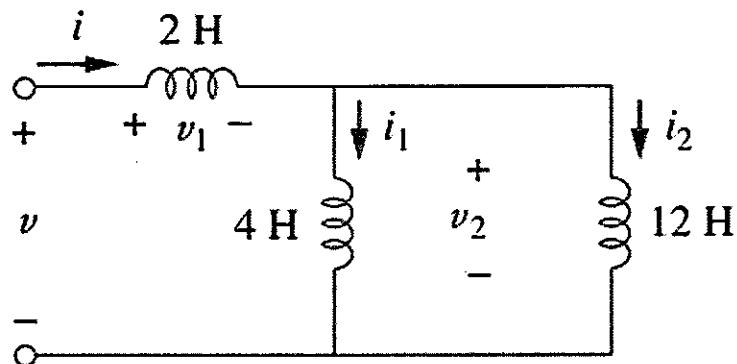


Figure 2(a)

(30 marks)

- b) The initial voltages on capacitors in the circuit shown in Figure 2(b) have been established by sources not shown. The switch is closed at  $t=0$ . Find:
- (i).  $v(t)$  for  $t \geq 0$
  - (ii).  $i(t)$  for  $t \geq 0$
  - (iii).  $v_1(t)$  for  $t \geq 0$ .
  - (iv).  $v_2(t)$  for  $t \geq 0$
  - (v). Calculate the initial energy stored in the Capacitors C1 and C2.
  - (vi). Determine how much energy is stored in the capacitors at  $t \rightarrow \infty$ .

...5/-

-5-

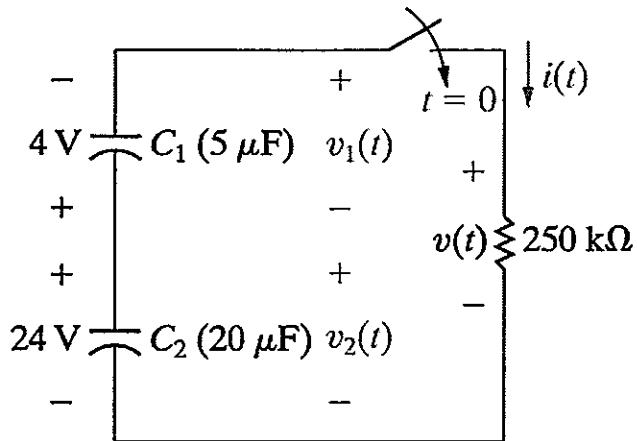


Figure 2(b)

(50 marks)

- c) The switch in the circuit shown in Figure 2(c) has been open for a long time. The initial charge on the capacitor is zero. At  $t = 0$ , the switch is closed. Find the expression for:
- $i(t)$  for  $t > 0$
  - $v(t)$  when  $t \geq 0$

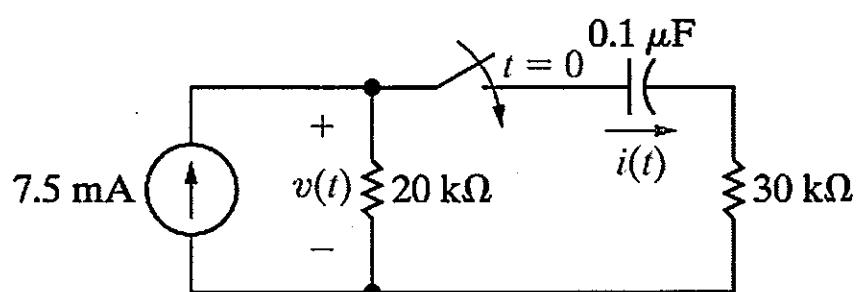


Figure 2(c)

(20 marks)

...6/-

-6-

3. a) Briefly explain the comparison between AC voltage and DC voltage. May add related figure/s in your answers.
- (20 marks)
- b) Determine the total current in the circuit of Figure 3(a). Also, find the power consumed and the power factor.

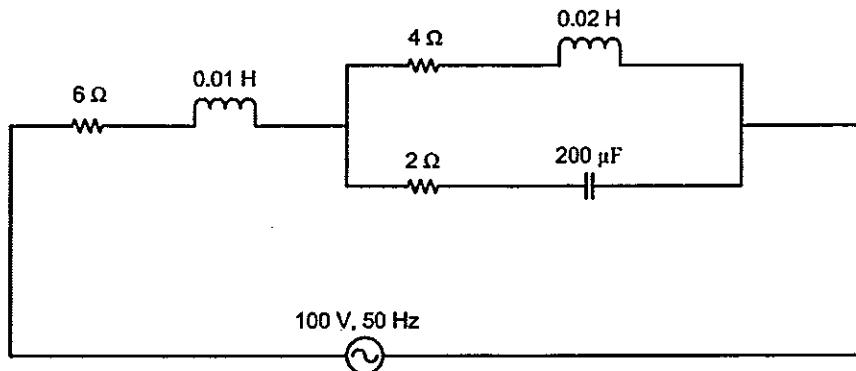


Figure 3(a)

(40 marks)

- c) A three-phase network, 200kW, 50Hz, delta-connected induction motor is supplied from a three-phase, 440V, 50Hz supply system. The efficiency and power factor of the three-phase induction motor is 91% and 0.86 respectively. Calculate:
- (i). Line currents
  - (ii). Currents in each phase of the motor
  - (iii). Active and reactive components of phase current

(40 marks)

-ooooOooo-

...7/-

-7-

**APPENDIX**

<b>Question</b>	<b>Course Outcome (CO)</b>	<b>Programme Outcome (PO)</b>
1	2	PO2
2	2	PO3
3	3	PO4

**Mathematical Formulas**

This appendix – by no means exhaustive – serves as a handy reference. It does contain all the formulas needed to solve circuit problems in this examination book.

**Quadratic Formula**

The roots of the quadratic equation  $ax^2 + bx + c = 0$  are

$$x_1, x_2 = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

**Trigonometric Identities**

$$\sin(-x) = -\sin x$$

$$\cos(-x) = \cos x$$

$$\sec x = \frac{1}{\cos x}, \csc x = \frac{1}{\sin x}$$

$$\tan x = \frac{\sin x}{\cos x}, \cot x = \frac{1}{\tan x}$$

$$\sin(x \pm 90^\circ) = \pm \cos x$$

$$\cos(x \pm 90^\circ) = \mp \sin x$$

$$\sin(x \pm 180^\circ) = -\sin x$$

$$\cos(x \pm 180^\circ) = -\cos x$$

$$\cos^2 x + \sin^2 x = 1$$

$$\frac{a}{\sin A} = \frac{b}{\sin B} = \frac{c}{\sin C} \quad (\text{law of sines})$$

$$a^2 = b^2 + c^2 - 2bc \cos A \quad (\text{law of cosines})$$

$$\frac{\tan \frac{1}{2}(A-B)}{\tan \frac{1}{2}(A+B)} = \frac{a-b}{a+b} \quad (\text{law of tangents})$$

$$\sin(x \pm y) = \sin x \cos y \pm \cos x \sin y$$

$$\cos(x \pm y) = \cos x \cos y \mp \sin x \sin y$$

$$\tan(x \pm y) = \frac{\tan x \pm \tan y}{1 \mp \tan x \tan y}$$

$$2 \sin x \sin y = \cos(x-y) - \cos(x+y)$$

$$2 \sin x \cos y = \sin(x+y) + \sin(x-y)$$

$$2 \cos x \cos y = \cos(x+y) + \cos(x-y)$$

$$\sin 2x = 2 \sin x \cos x$$

$$\cos 2x = \cos^2 x - \sin^2 x = 2 \cos^2 x - 1 = 1 - 2 \sin^2 x$$

-9-

$$\tan 2x = \frac{2 \tan x}{1 - \tan^2 x}$$

$$\sin^2 x = \frac{1}{2}(1 - \cos 2x)$$

$$\cos^2 x = \frac{1}{2}(1 + \cos 2x)$$

$$K_1 \cos x + K_2 \sin x = \sqrt{K_1^2 + K_2^2} \cos\left(x + \tan^{-1} - \frac{K_2}{K_1}\right)$$

$$e^{\pm jx} = \cos x \pm j \sin x \quad (\text{Euler's identity})$$

$$\cos x = \frac{e^{jx} + e^{-jx}}{2}$$

$$\sin x = \frac{e^{jx} - e^{-jx}}{2j}$$

$$1 \text{ rad} = 57.296^\circ$$

### Hyperbolic Functions

$$\sinh x = \frac{1}{2}(e^x - e^{-x})$$

$$\cosh x = \frac{1}{2}(e^x + e^{-x})$$

$$\tanh x = \frac{\sinh x}{\cosh x}$$

$$\coth x = \frac{1}{\tanh x}$$

$$\operatorname{csch} x = \frac{1}{\sinh x}$$

$$\operatorname{sech} x = \frac{1}{\cosh x}$$

$$\sinh(x \pm y) = \sinh x \cosh y \pm \cosh x \sinh y$$

$$\cosh(x \pm y) = \cosh x \cosh y \pm \sinh x \sinh y$$

### Derivatives

If  $U = U(x)$ ,  $V = V(x)$ , and  $a = \text{constant}$ ,

$$\frac{d}{dx}(aU) = a \frac{dU}{dx}$$

$$\frac{d}{dx}(UV) = U \frac{dV}{dx} + V \frac{dU}{dx}$$

$$\frac{d}{dx}\left(\frac{U}{V}\right) = \frac{\left(V \frac{dU}{dx} - U \frac{dV}{dx}\right)}{V^2}$$

-10-

$$\frac{d}{dx}(aU^n) = naU^{n-1}$$

$$\frac{d}{dx}(a^U) = a^U \ln a \frac{dU}{dx}$$

$$\frac{d}{dx}(e^U) = e^U \frac{dU}{dx}$$

$$\frac{d}{dx}(\sin U) = \cos U \frac{dU}{dx}$$

$$\frac{d}{dx}(\cos U) = -\sin U \frac{dU}{dx}$$

Indefinite Integrals

If  $U = U(x)$ ,  $V = V(x)$ , and  $a = \text{constant}$ ,

$$\int a \, dx = ax + C$$

$$\int U \, dV = UV - \int V \, dU \quad (\text{integration by parts})$$

$$\int U^n \, dU = \frac{U^{n+1}}{n+1} + C, \quad n \neq 1$$

$$\int \frac{dU}{U} = \ln U + C$$

$$\int a^U \, dU = \frac{a^U}{\ln a} + C, \quad a > 0, a \neq 1$$

$$\int e^{ax} \, dx = \frac{1}{a} e^{ax} + C$$

$$\int xe^{ax} \, dx = \frac{e^{ax}}{a^2} (ax - 1) + C$$

$$\int x^2 e^{ax} \, dx = \frac{e^{ax}}{a^3} (a^2 x^2 - 2ax + 2) + C$$

$$\int \ln x \, dx = x \ln x - x + C$$

$$\int \sin ax \, dx = -\frac{1}{a} \cos ax + C$$

$$\int \cos ax \, dx = \frac{1}{a} \sin ax + C$$

$$\int \sin^2 ax \, dx = \frac{x}{2} - \frac{\sin 2ax}{4a} + C$$

$$\int \cos^2 ax \, dx = \frac{x}{2} + \frac{\sin 2ax}{4a} + C$$

$$\int x \sin ax \, dx = \frac{1}{a^2} (\sin ax - ax \cos ax) + C$$

...11/-

-11-

$$\int x \cos ax dx = \frac{1}{a^2} (\cos ax + ax \sin ax) + C$$

$$\int x^2 \sin ax dx = \frac{1}{a^3} (2ax \sin ax + 2 \cos ax - a^2 x^2 \cos ax) + C$$

$$\int x^2 \cos ax dx = \frac{1}{a^3} (2ax \cos ax - 2 \sin ax + a^2 x^2 \sin ax) + C$$

$$\int e^{ax} \sin bx dx = \frac{e^{ax}}{a^2 + b^2} (a \sin bx - b \cos bx) + C$$

$$\int e^{ax} \cos bx dx = \frac{e^{ax}}{a^2 + b^2} (a \cos bx + b \sin bx) + C$$

$$\int \sin ax \sin bx dx = \frac{\sin(a-b)x}{2(a-b)} - \frac{\sin(a+b)x}{2(a+b)} + C, \quad a^2 \neq b^2$$

$$\int \sin ax \cos bx dx = -\frac{\cos(a-b)x}{2(a-b)} - \frac{\cos(a+b)x}{2(a+b)} + C, \quad a^2 \neq b^2$$

$$\int \cos ax \cos bx dx = \frac{\sin(a-b)x}{2(a-b)} + \frac{\sin(a+b)x}{2(a+b)} + C, \quad a^2 \neq b^2$$


$$\int \frac{dx}{a^2 + x^2} = \frac{1}{a} \tan^{-1} \frac{x}{a} + C$$

$$\int \frac{x^2 dx}{a^2 + x^2} = x - a \tan^{-1} \frac{x}{a} + C$$

$$\int \frac{dx}{(a^2 + x^2)^2} = \frac{1}{2a^2} \left( \frac{x}{x^2 + a^2} + \frac{1}{a} \tan^{-1} \frac{x}{a} \right) + C$$

### Phasor & Complex Number

Imaginary axis

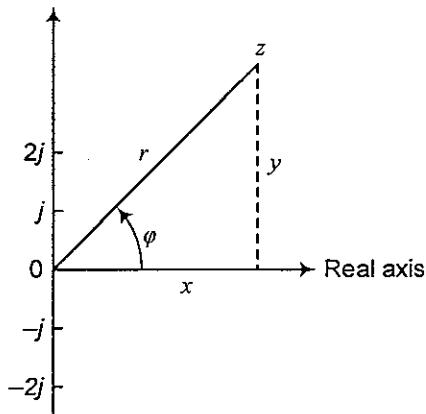

Complex number in rectangular form:

$$z = x + jy$$

$$r = \sqrt{x^2 + y^2}$$

$$\varphi = \tan^{-1} \frac{y}{x}$$

...12-

-12-

$$z = r(\cos \varphi + j \sin \varphi)$$

$$\frac{1}{j} = -j \text{ and } j = 1 \angle 90^\circ$$

Complex number in polar form:

$$z = r \angle \varphi$$

Complex number in exponential form:

$$z = r e^{j\varphi}$$

Sinusoid  $\leftrightarrow$  phasor transformation:

$$V_m \cos(\omega t + \varphi) \leftrightarrow V_m \angle \varphi$$

$$V_m \sin(\omega t + \varphi) \leftrightarrow V_m \angle (\varphi - 90^\circ)$$

$$I_m \cos(\omega t + \theta) \leftrightarrow I_m \angle \theta$$

$$I_m \sin(\omega t + \theta) \leftrightarrow I_m \angle (\theta - 90^\circ)$$

Mathematic operation of complex number:

$$\text{Addition } z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$\text{Subtraction } z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$$


$$\text{Multiplication } z_1 z_2 = r_1 r_2 \angle (\varphi_1 + \varphi_2)$$

$$\text{Division } \frac{z_1}{z_2} = \frac{r_1}{r_2} \angle (\varphi_1 - \varphi_2)$$

$$\text{Reciprocal } \frac{1}{z} = \frac{1}{r} \angle -\varphi$$

$$\text{Square-root } \sqrt{z} = \sqrt{r} \angle (\varphi/2)$$
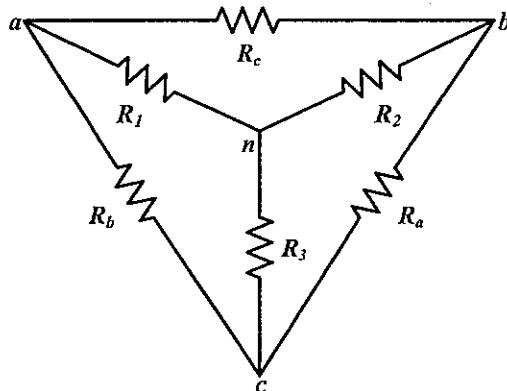
$$\text{Complex conjugate } z^* = x - jy = r \angle -\varphi = r e^{-j\varphi}$$



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$